

~~I was on page 849~~

Electric Circuits

SI units

m - meter

A - ampere (s)

kg - kilograms

K - Kelvin

s - seconds

cd - candela

symbols Electrical Engineers USE

Quantity

Symbol

Unit

Time $\rightarrow t$

s

Frequency $\rightarrow f$

s^{-1}

Radian frequency $\rightarrow \omega = 2\pi f$

$rads^{-1}$

Energy $\rightarrow W$

J

Power $\rightarrow P$

(J/s)

charge $\rightarrow q$

C

2

Voltage $\rightarrow V$ V

Current

$$q(t) = C$$

unit for current $\sim A \left(\frac{C}{s}\right)$

How do we find current from the charge expression?

Recall from Physics I,


$$\frac{m(t)}{V} ?$$

$$V = \frac{m}{s} = \frac{d}{dt} m(t)$$

$$q = \frac{d^2}{dt^2} m(t) = \frac{m}{s^2}$$

$$\underline{i = \frac{d}{dt} q(t)}$$

$$1 \text{ C} = 1 \text{ A}$$

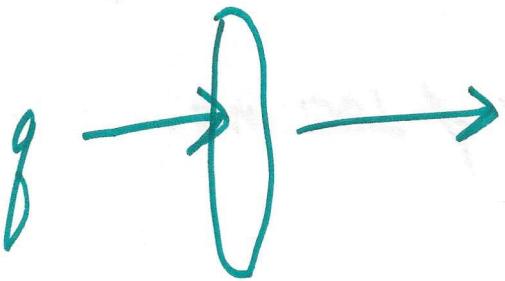

$$V = \frac{d}{dt} W(q) = \text{J/C}$$

$$1 \text{ J/C} = 1 \text{ V} \quad \text{work done per charge unit}$$

power:

$$P = \frac{d}{dt} W(t) = \frac{dW}{dq} \frac{dq}{dt} = (V)(i)$$

$$W_T = \sum_{t=0}^{t_f} P dt$$

4

Example

The current thru a circuit element is 50mA .
 find the total charge and the number of electrons transferred during a period of 100 ns .

$$\bar{i} = \frac{dq}{dt} q(t)$$

$$q_T = \int_0^{10^{-7}} 50 \times 10^{-3} dt = 50 \times 10^{-10} C = 5\text{nC}$$

$$q_{e^-} = \cancel{6.25 \times 10^{18}} C$$


$$\rightarrow 5 \times 10^{-9} (6.25 \times 10^{18}) = 31.25 \times 10^8 e^-$$

$$q_{e^-} = \underline{\quad} C$$

$$\frac{5\text{nC}}{q_{e^-}} = 5\text{nC} \left[\frac{1}{q_{e^-}} \right]$$

Passive Sign Convention

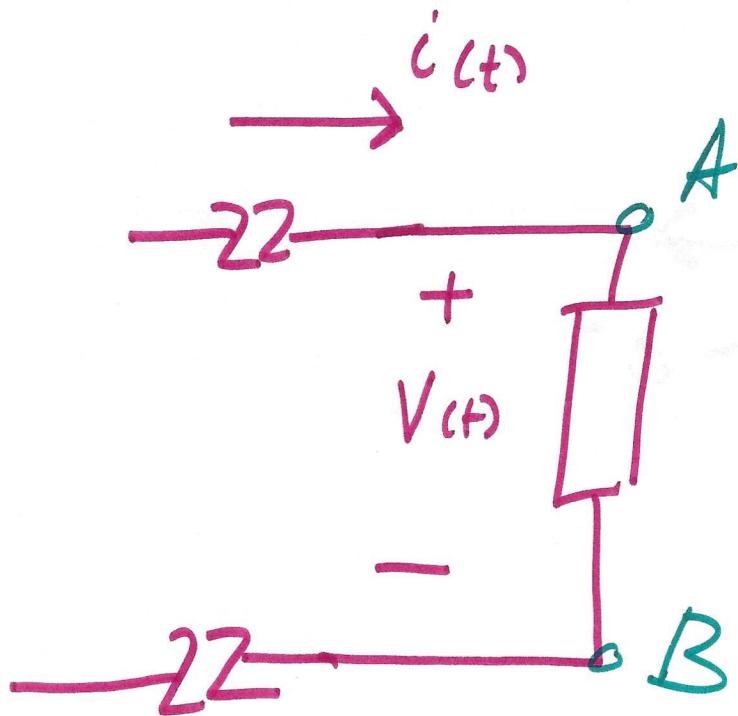We usually don't deal with charge and energy but voltage, current, and power





We define this
to be passive sign
convention!

The physical phenomena happens regardless of
the assigned polarity

If $i > 0$, i flows into A from Left to Right

If $i < 0$, i flows from A, from Right to Left

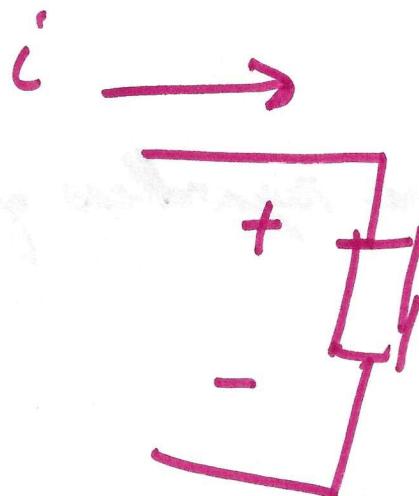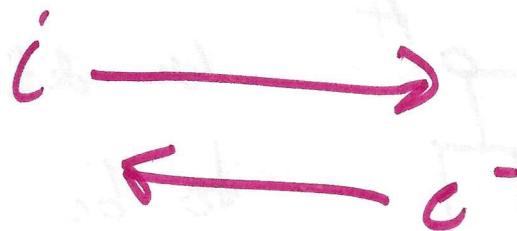In summary, the algebraic signs of the answer together with arbitrarily assigned reference marks tell us the actual direction of a voltage or current variable.



Passive sign convention

$P(+)>0$ when the device absorbs power

$P(+)<0$ device delivers power


For battery S

$P(t) > 0$, battery is being charged


$P(t) < 0$, battery is being discharged.

Ground

- Common voltage reference point

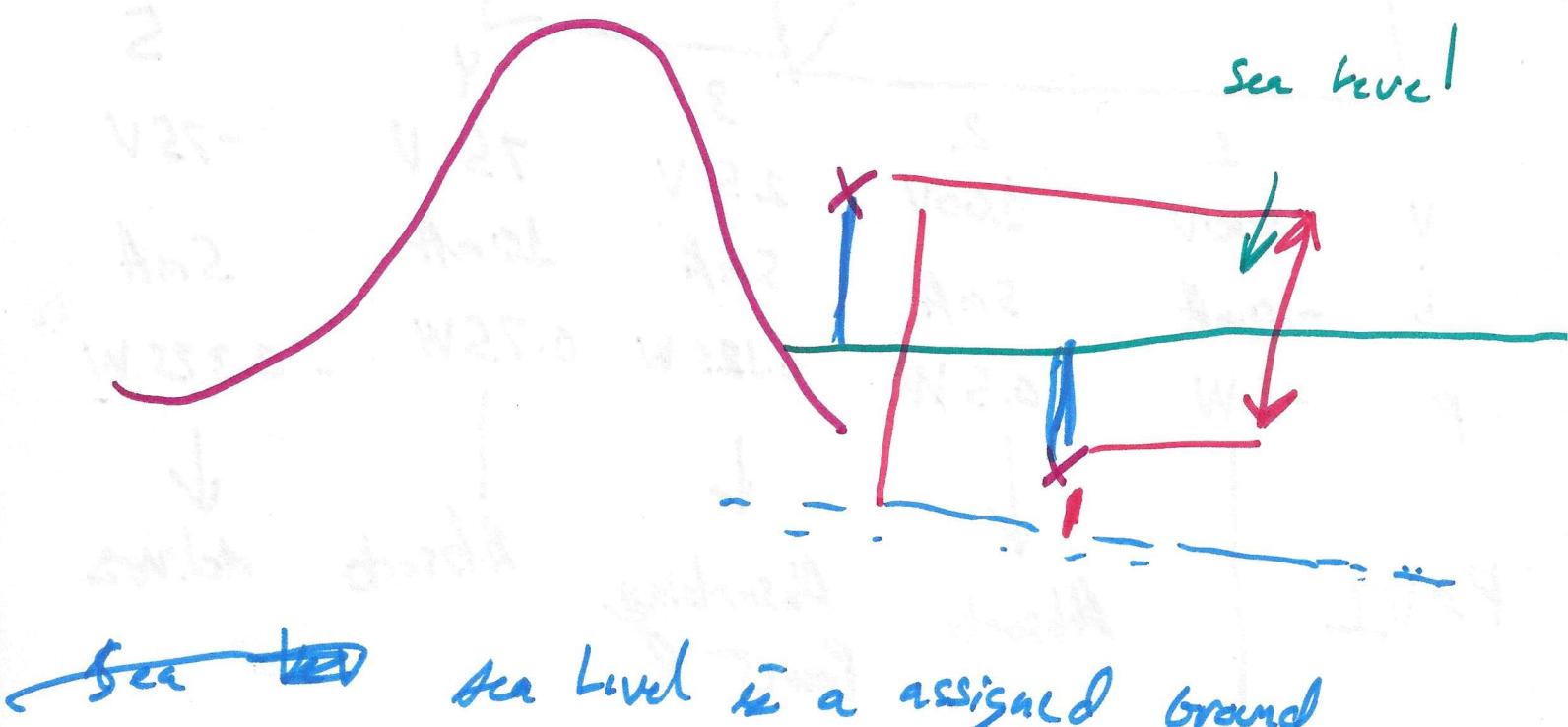

7

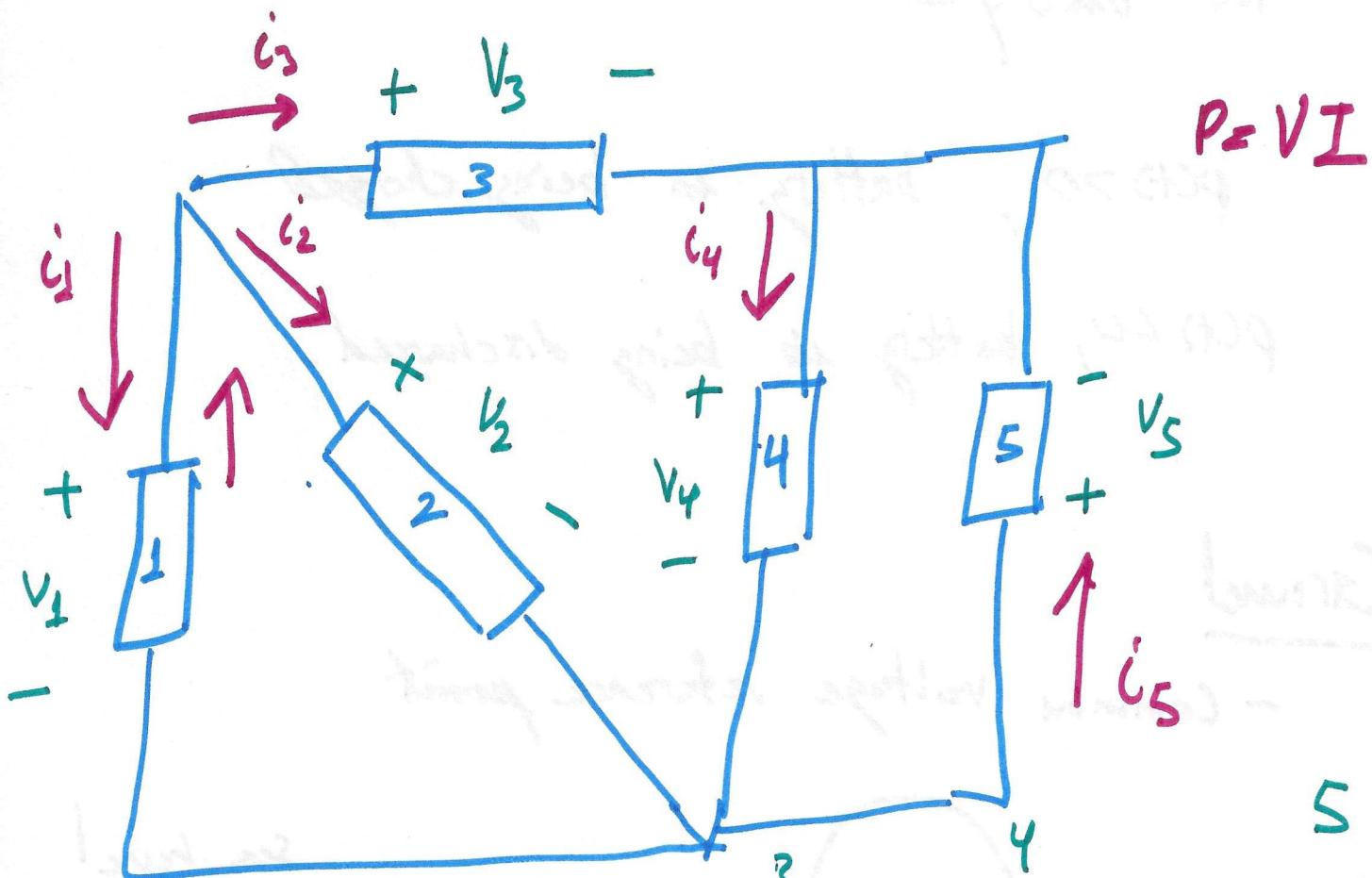

	1	2	3	4	5
V	100V	100V	25V	75V	-75V
i	-10mA	5mA	5mA	10mA	5mA
P	-1W	0.5W	0.125W	0.75W	-0.375W
$P = VI$					
	Absorb	Absorb	Absorb	Absorb	delivers
		Absorbing Power			

As you can see, total power is zero!

For Linear Circuits Total Power will
Always be zero!

2-1 Element Constraints!

A two terminal device is described by an
i-V characteristic



→ The relationship between Voltage and
current in the device

A circuit element is a model of a real world
device!

10

The Linear Resistor

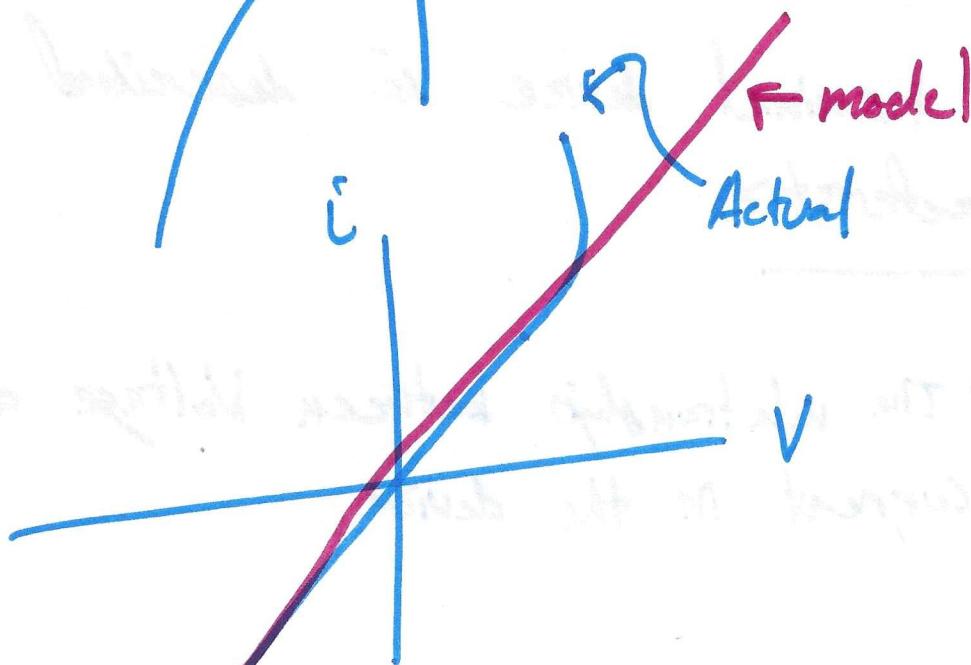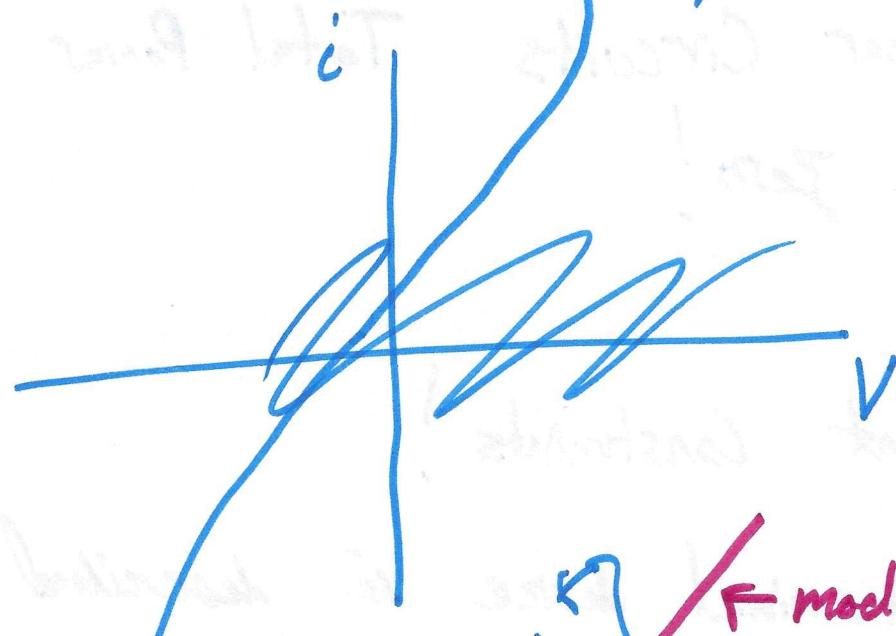The actual I-V characteristic of a resistor



even resistors have power ratings
that tell us the linear range of its
operating characteristics

$$V = iR \quad \text{or} \quad i = GV \quad \text{Ohm's}$$

$$G = \frac{1}{R} \quad R - \text{resistance} \quad \Omega$$


$$G - \text{conductance} \quad \Omega^{-1} = S$$

mho Ω^{-1}

Siemens

Ohm's Law presumes that the passive sign convention is used to assign the reference marks to Voltage and Current.

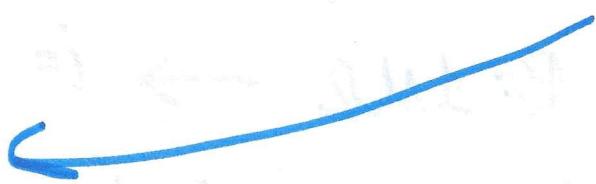I-V characteristic for the Ohm's Law model says the circuit current is Linear and Bilateral




i-V curve has odd symmetry about the origin

J2


→ A curve $i = f(v)$ has odd symmetry if
 $f(-v) = -f(v)$

Limiting Cases of the Resistor

→ Open and short Circuits

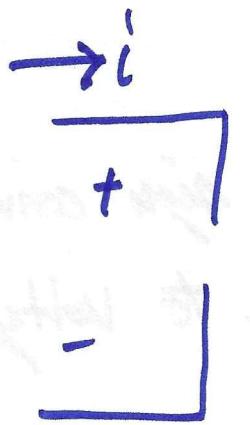

$$R = \infty \Omega$$

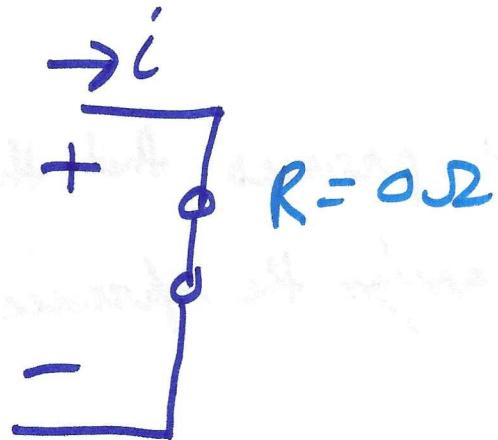

$$R = 0 \Omega$$

$$V = 10V \quad R = 1\Omega \rightarrow i = 10A$$

$$V = 10V \quad R = 100\Omega \rightarrow i = 0.1A$$


$$V = 10V \quad R = 1M\Omega \rightarrow i = 10\mu A$$

$$R = \infty \Omega \rightarrow i = 0A$$

What happens to the current and Voltage
when $R \rightarrow 0$

will $V \rightarrow 0$, $V = IR$

for

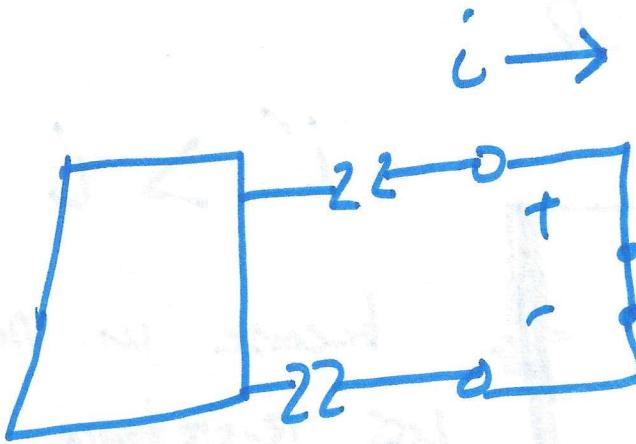


The current i_1 is supplied by the rest of the circuit,

If we get go from R to 0Ω ,


the current is no longer delivering Power (Energy)
to the Resistor as there is no Resistor anymore

14

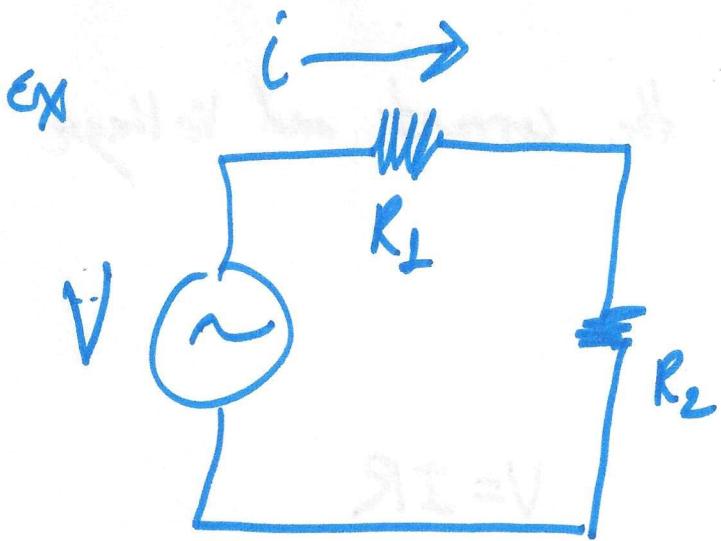

i' goes thru
both R_L and
 R_2

Let $R_2 \rightarrow 0 \Omega$

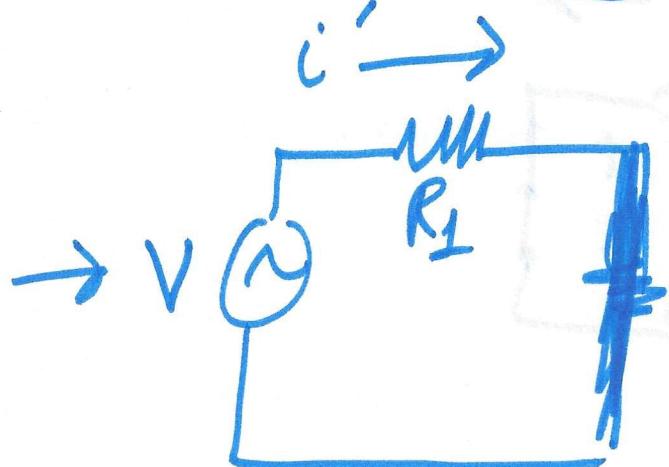

$i' > i$

because we now have
less resistance.

$$V = IR \rightarrow$$

In the first case

Power delivered is $P = VI = I^2(R_L + R_2)$

Second case (Less Power delivered)

Power delivered is $P = I^2(R_L + 0)$