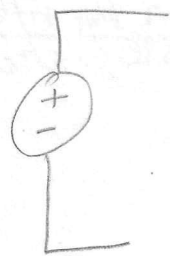


Review Notes for Stream


Make Lecture Notes After Reviewing

→ Use Mystery Persuasion while writing Notes


Chapter 2 Ideal Sources




Time Varying

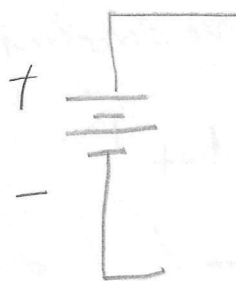


Constant

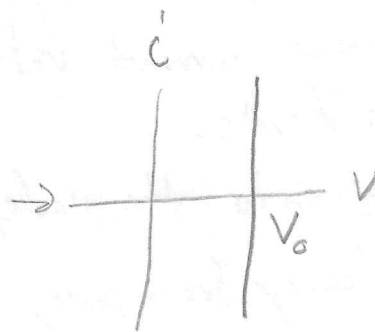

i-v plot for constant

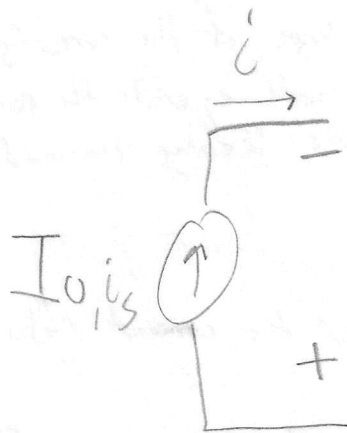

Time-varying or
constant source

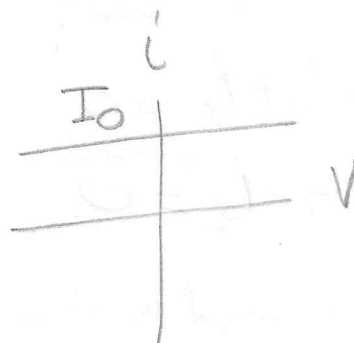

constant source i-v characteristics

→ Forcing function, driving function

→ represents an input that causes a circuit response

For Analysis & Design of Linear circuits → DC: V , AC: $V(t)$
for Circuit Analysis and Design → DC: V , AC: v

(2)

Kirchhoff's current Law (KCL)

→ the algebraic sum of the currents entering a node is zero at every instant

↓
an equipotential

$$\sum_{n=1}^N i_n = 0 \quad (\text{KCL})$$

$N = \text{total \# of branches connected to the node}$
 i_n is the rth current associated

— we must know current reference direction with each device.

— if current is into the node, '+'

" away from node, '-'

$$A: -i_1 - i_2 = 0$$

$$i_1 - i_3 - i_4 + i_5 = 0$$

$$i_2 + i_3 + i_4 - i_5 = 0$$

The sum of the currents entering a node equals the sum of the currents leaving the node

→ '+' or '-' determined by the orientation of the current reference direction relative to a node

→ when equations are solved, we have the actual direction of the current relative to the reference direction

for $i_1 = 4 \text{ A}$, $i_3 = 1 \text{ A}$, $i_4 = 2 \text{ A}$ $i_2?$ $i_5?$

$$-i_1 - i_2 = 0 \rightarrow i_2 = -4 \text{ A} \quad i_2 \text{ is actually going into (A)}$$

$$i_1 - i_3 - i_4 + i_5 = 0 \rightarrow i_5 = i_4 + i_3 - i_1$$

$$= 2 + 1 - 4$$

$$= -1 \rightarrow i_5 = -1 \text{ A, comes out of (B)}$$

Note $i_2 + i_3 + i_4 - i_5 = 0$ is from

$$-i_1 - i_2$$

+

$$i_1 - i_3 - i_4 + i_5$$

$$\underline{-i_2 - i_3 - i_4 + i_5 = 0}$$

$$-(A+B) = C$$

C is not independent of A, B

→ In a circuit containing a total of N nodes, there are only $N-1$ independent KCL connection equations

→ So select one node as ground (reference) then get KCL equations from $(N-1)$ nodes

[Self Q, does Ulaby mention this?]

[Does Nilsson mention this?]

Kirchoff's Voltage Law based on conservation of Energy

The algebraic sum of all the voltages around a Loop is zero at every instant

$$\sum_{n=1}^N V_n = 0$$

N = Total number of branches in the loop
 V_n is n th voltage across the n th branch

p 24, Figure 2-13 - In writing the algebraic sum of voltages, we must account for the assigned reference marks
 → Positive for $+$ → $-$
 → Negative for $-$ → $+$

④

cf 2-10

$$L1: V_2 + V_5 - V_1 = 0$$

$$L2: V_4 + V_5 - V_3 = 0$$

$$L3: V_2 + V_4 + V_5 - V_1 = 0$$

if a voltage is positive,
Then it agrees with the reference.
Polarity wise

Solve KVL for $V_1 = 5V$, $V_2 = -3V$, $V_4 = 10V$

$V_3?$, $V_5?$

$$V_3 = V_1 - V_2 = 8V$$

$$V_5 = V_3 - V_4 = -2V$$

We found using KVL constraints

Loop 3 is valid eq but has no new info cuz $L1 + L2 = L3$

$L3$ is not independent of $L1$ or $L2$

In a circuit containing a total of E two-terminal elements and N nodes, there are only $E - N + 1$ independent KVL connection equations

→ A sufficient condition for a Loop to be different is that each contains at least one element that is not contained in any other Loop nodes

$$E - N + 1 = 2$$

$$E - N = 1$$

$$N = 4 \quad E = 5$$

for 2-13 devices

p26 Parallel and Series Connections

(5)

p28 Combined constraints

We want to know V and I at various places in the circuit

element constraints are based on the models of the specific devices connected in the circuit

- based on Kirchhoff's Laws and circuit connection.

So we know:

$$i_x = i_o$$


$$V_o = R i_o$$

$$E = 2 \text{ element}$$

$$N = 2 \text{ nodes}$$

$$\text{so } E - N + 1 = 1 \text{ KVL}$$

$$N - 1 = 1 \text{ KCL}$$

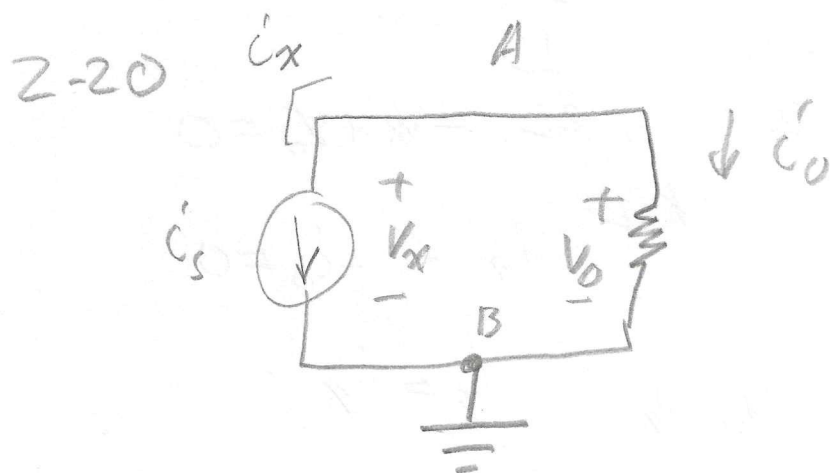

combined restraint circuit

(at A) KCL: $-i_x - i_o = 0$

KVL: $-V_x + V_o = 0$

$$i_o = -i_x = -i_s$$

$$\rightarrow V_o = -R i_s$$

[if i_s is '+' then V_o is '-']
Not $i-v$ relationship
 \rightarrow input-output relationship

⑥

$$i_s = +2 \text{ mA} \quad R = 2 \text{ k}\Omega$$

$$i_x, v_x, i_o, v_o?$$

$$v_o = v_x = -(2 \times 10^{-3})(2 \times 10^{-3}) = -4 \text{ V}$$


$$i_o = -2 \text{ mA}$$

$$i_s = -2 \text{ mA}$$

$$i_x = -2 \text{ mA}$$

$$v_o = v_x = 4 \text{ V}$$

$$i_o = -i_x = 2 \text{ mA}$$

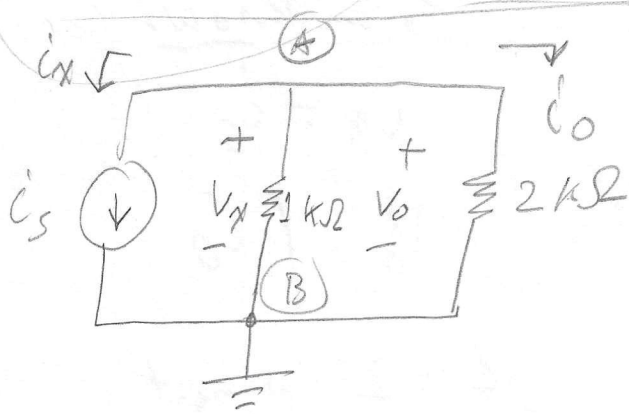

$$\text{KVL } 3 - 2 + 1 = 2$$

$$1L$$

$$2L: -v_x + v_o = 0$$

$$\text{KCL}$$

$$-i_x - i - i_o = 0$$

$$i_x, v_x, i_o, v_o$$

$$v_o = v_x \quad i_s = i_x$$

$$v_o = 2 \times 10^3 (i_o)$$

$$-i_x - \frac{v_x}{1 \text{ k}\Omega} - \frac{v_o}{2 \text{ k}\Omega} = i_x$$

$$-2i_o - i_o = -3i_o = i_x$$

$$V = IR$$


$$v_x = 2 \text{ k}\Omega i_o$$

$$\frac{V}{R}$$

$$I = \frac{2 \text{ k}\Omega}{1 \text{ k}\Omega} i_o = 2i_o$$

$$\rightarrow -i_x - i - i_o = 0$$

$$3i_o - 2i_o - i_o$$

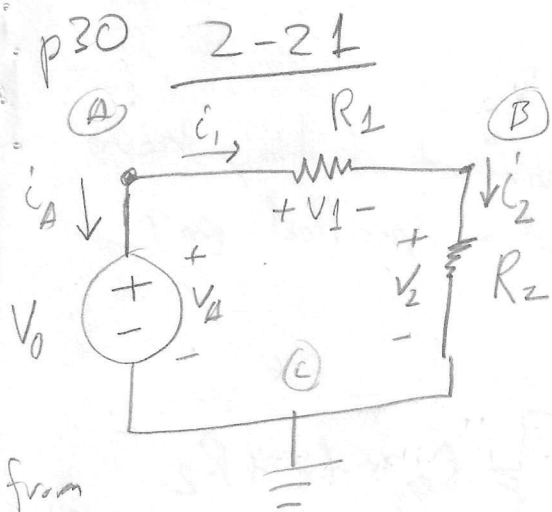

from
Ohm's
Law

Elemental equations
KCL equations
KVL equations

$$V_A = V_0$$

$$V_1 = i_1 R_1$$

$$V_2 = i_2 R_2$$

KCL (7)

$$A: -i_A - i_1 = 0$$

$$B: -i_2 + i_1 = 0$$

KVL

$$L1: V_1 + V_2 - V_A = 0$$

$E = \# \text{ of Element}$
 $N = \# \text{ of nodes (incl. GND)}$

$$\frac{E - N + 1}{2E} \leftarrow \text{Total Equations}$$


$$i_1 R_1 + i_2 R_2 - V_0 = 0$$

$$i_1 R_1 + i_1 R_2 - V_0 = 0 \rightarrow V_0 = i_1 (R_1 + R_2)$$

$$i_1 = \frac{V_0}{R_1 + R_2} = \frac{10}{2k\Omega + 3k\Omega} = \frac{1}{500} = 2 \text{ mA} = i_2 = i_1$$

$$-i_A = i_1 = -2 \text{ mA}$$

p32 2-23

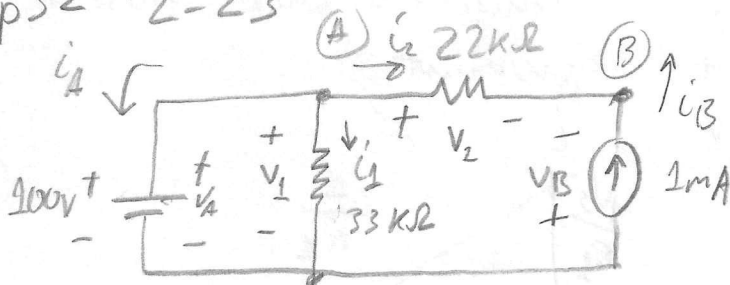

$$A: -i_A - i_2 - i_1 = 0$$

$$B: i_2 + i_B = 0$$


$$V_1 - V_A = 0$$

$$V_2 - V_B - V_1 = 0$$

Ohm's Law assumes that the passive sign convention is used to assign the voltage and current reference marks to a device. p34, 35

Equivalent circuits p36

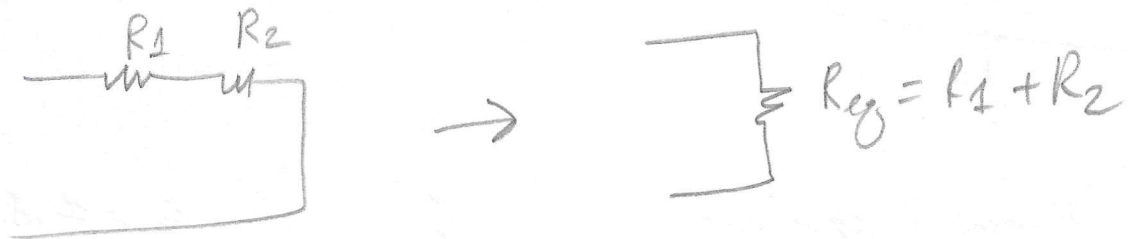
→ Two circuits are said to be equivalent if they have identical i-v characteristics at a specified pair of terminals




$$R_1 || R_2 = R_{eq} = \frac{1}{G_{eq}} = \frac{1}{G_1 + G_2} = \frac{1}{R_1^{-1} + R_2^{-1}} = \frac{R_1 R_2}{R_1 + R_2}$$

Equivalent sources p39

Practical source models


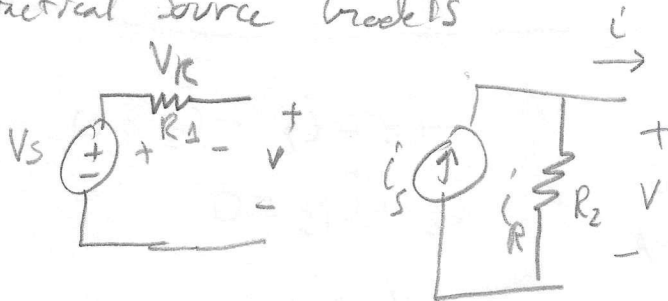


A
KVL

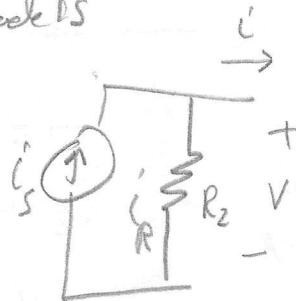

B
KCL

conditions where these are equivalent

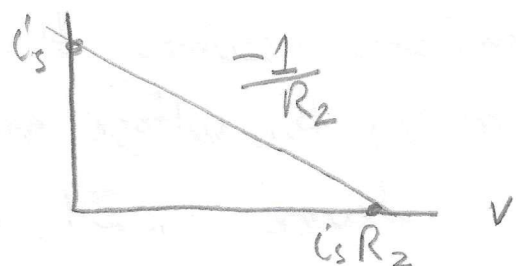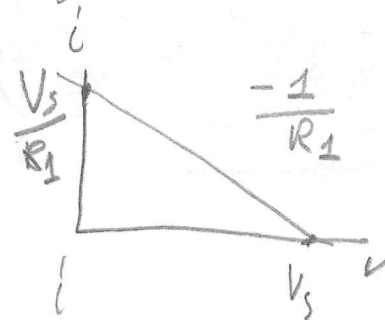

$$V_R = V_s - V \quad V_s = V_R + V$$

$$V_R = R_1 i$$

$$i = \frac{V_s}{R_1} - \frac{V}{R_1}$$

$$I_s = I_R + i$$

$$V_R = \frac{V}{R_2}$$

$$i = I_s - \frac{V}{R_2}$$

we need

$$V_s = i_s R_2, \quad i_s = \frac{V_s}{R_1}$$

$$\text{So } R_1 = R_2 = R \rightarrow V_s = i_s R$$

$$\begin{matrix} A & B \\ i = -\frac{V}{R} + \frac{V_s}{R} & i = -\frac{V}{R} + \frac{V_s}{R} \end{matrix} \quad i_s$$

Exchanging one practical source model for an equivalent model is called source transformation

→ either models will deliver the same voltage and current to the rest of the circuit


→ Do not have same internal power loss (p 40)

Summary p 42

Voltage and Current Division

p 44

Voltage division

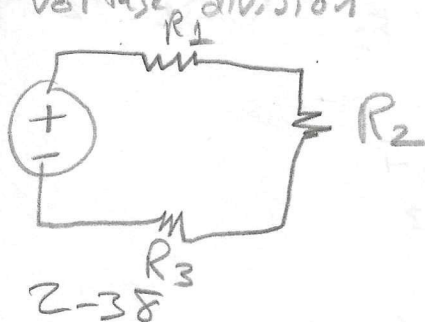

$$\begin{aligned} V_s &= V_1 + V_2 + V_3 \\ &= R_1 i + R_2 i + R_3 i \end{aligned}$$

$$\rightarrow i = \frac{V_s}{R_1 + R_2 + R_3}$$

Voltage across each resistor

$$V_1 = R_1 i = \left(\frac{R_1}{R_1 + R_2 + R_3} \right) V_s$$


$$V_2 = R_2 i = \left(\frac{R_2}{R_1 + R_2 + R_3} \right) V_s$$

$$V_3 = R_3 i = \left(\frac{R_3}{R_1 + R_2 + R_3} \right) V_s$$

(20) So write voltage division rule

$$V_K = \left(\frac{R_K}{R_{eq}} \right) V_{Total} \quad (2-31)$$

ex) p 45

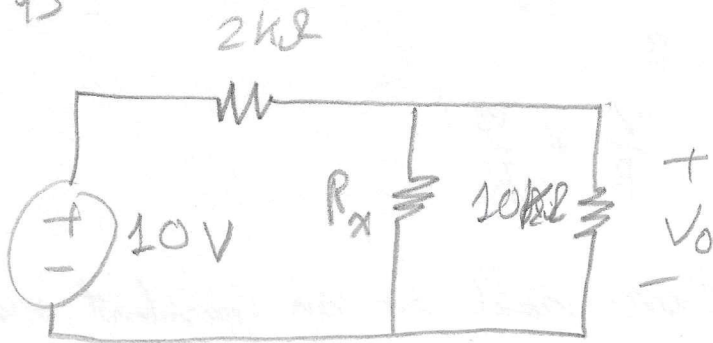


$$V_O = 8V$$

$$\rightarrow V_O = \left(\frac{R_{eq}}{R_{eq} + 2k} \right) 10V$$

$$R_{eq} = 8k\Omega$$

$$R_{eq} = \frac{R_K(10k)}{R_K + 10k} \rightarrow R_K = 40k\Omega$$

Current Division p 47-48

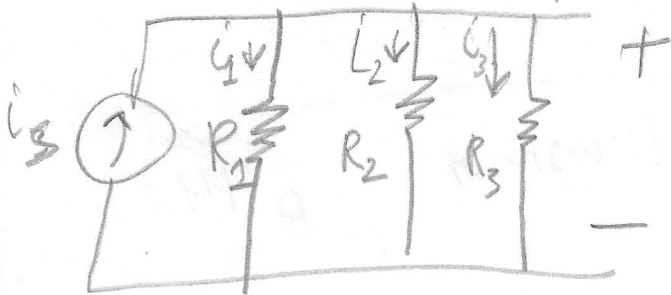

KCL

$$I_S = I_1 + I_2 + I_3$$

$$I_S = \frac{V}{R_1} + \frac{V}{R_2} + \frac{V}{R_3} = V(R_1^{-1} + R_2^{-1} + R_3^{-1})$$

$$V = \frac{I_S}{R_1^{-1} + R_2^{-1} + R_3^{-1}}$$

$$I_1 = \frac{V}{R_1} = \frac{I_S}{R_1(R_1^{-1} + R_2^{-1} + R_3^{-1})}$$

$$I_2 = \frac{V}{R_2} = \frac{I_S}{R_2(R_1^{-1} + R_2^{-1} + R_3^{-1})}$$

$$I_3 = \frac{I_S}{R_3(R_1^{-1} + R_2^{-1} + R_3^{-1})}$$

$$\text{So } I_K = \left(\frac{G_K}{G_{eq}} \right) I_{Total}$$