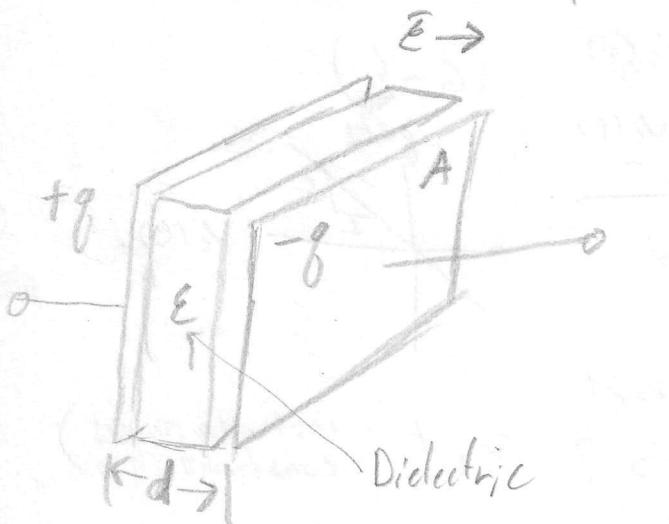


(1)

Chapter 6 Capacitance and Inductance

6-1 The Capacitor

a dynamic element involving the time variation of an electric field



We have a uniform electric field exist across the plates when there's a voltage across the capacitor.

We have charge separation, equal and opposite across the plates

$$\text{We have } \bar{E}(t) = \frac{q(t)}{\epsilon A}$$

ϵ - permittivity of Dielectric

A - area of the plates

$q(t)$ - magnitude of charge on each plate

\bar{E} field $\frac{N}{C}$ or V/m

Note, the \bar{E} field can be written in terms of Voltage across the cap

$$\bar{E} = \frac{V_c(t)}{d} \quad \text{From Physics II and Fields and Waves}$$

$$\text{So we can write: } \frac{q(t)}{\epsilon A} = \frac{V_c(t)}{d} \rightarrow q(t) = \frac{\epsilon A}{d} V_c(t) \quad (6-3)$$

We know from Physics II and Fields and Waves

$$C = \frac{\epsilon A}{d} F \quad (6-4) \quad \text{This is capacitance (Farads)}$$

$$\text{So we may write: } q(t) = C V_c(t) \quad C \quad (6-5)$$



② I-V Relationship

To express the desired constraint in terms of voltage and current, recall we know current is charge/second so differentiate

$$\frac{d}{dt} q(t) = \frac{d}{dt} C V_C(t)$$

We have $i_C(t) = C \frac{d}{dt} V_C(t)$ (6-6)

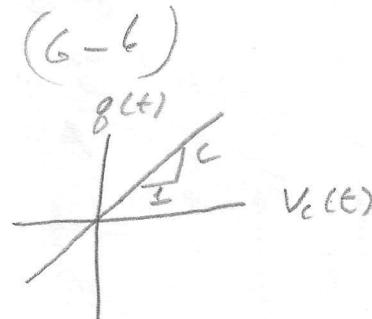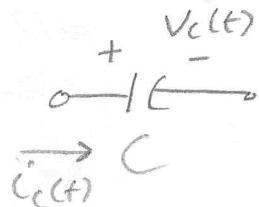We assume the reference marks for current and voltage follow the passive sign convention



so $i_C(t) = 0$, for $V_C(t) = \text{constant}$

and current is constant when $V_C = 0$? Yes! (instantaneous constant)

The capacitor is a dynamic element because the current is 0 unless the voltage is changing

→ discontinuous change in ^{voltage} current would require an infinite current

→ so V_C must be a continuous function of time

To express Voltage in terms of current, we are allowed to write

$$\int \left(C \frac{d}{dt} V_C(t) \right) = \int i_C(t) dt \quad \begin{pmatrix} \text{we multiplied both sides} \\ \text{by } dt \text{ and then integrate} \end{pmatrix}$$

$$\int dV_C(t) = \frac{1}{C} \int i_C(t) dt$$

we assume at some time t_0 the voltage across the cap $V_C(t_0)$ is known so voltage at a later time $t > t_0$

$$\rightarrow \int_{V_C(t_0)}^{V_C(t)} \frac{dV_C}{dt} = \frac{1}{C} \int_{t_0}^t i_C(x) dx$$

$$\text{or } \int_{V_C(t_0)}^{V_C(t)} \frac{dV_C}{V_C(t)} = \frac{1}{C} \int_{t_0}^t i_C(x) dx$$

(3)

Further

$$V_C(t) - V_C(t_0) = \frac{1}{C} \int_{t_0}^t i_C(x) dx$$

$$\rightarrow V_C(t) = V_C(t_0) + \frac{1}{C} \int_{t_0}^t i_C(x) dx \quad (6-7)$$

time to

In practice, t_0 is established by a physical event (closing switch)
(start of a particular clock pulse)

Let's define $t_0 = 0$

$$V_C(t) = V_C(0) + \frac{1}{C} \int_0^t i_C(x) dx \quad (6-8)$$

Power and Energy considering passive sign convention

$$P_C(t) = i_C(t) V_C(t) \quad (6-9)$$

we write

$$P = \frac{d}{dt} W \quad P_C(t) = C V_C(t) \frac{d}{dt} V_C(t) = \frac{d}{dt} \left[\frac{1}{2} C V_C^2(t) \right] \quad (6-10)$$

(we may write this)

 \rightarrow Power can be '+' or '-'

absorbs Power	delivers power
------------------	----------------

 \rightarrow As the cap can deliver power, it can store it (Power)Power is J/S (time rate change of energy)we can infer that $W_C(t) = \frac{1}{2} C V_C^2(t) + \text{constant } J$ Constant refers to stored energy at instant t (time), when $V_C(t) = 0$ $\rightarrow \bar{E}$ is 0 so stored energy is 0

$$\rightarrow W_C(t) = \frac{1}{2} C V_C^2(t) \quad (6-11)$$

(proportional to square so energy can't be negative)

④ Capacitor stores power by absorbing
then returns power from stored energy

→ abrupt change in voltage → discontinuous charge or energy

$$\rightarrow \text{Power} = \frac{d}{dt} w, \text{ if } w \text{ is discontinuous}$$


$$\rightarrow \text{Power} \rightarrow \infty$$

voltage

(Not Possible)

Capacitor is a state variable because it determines the energy state of the element.

Example 6-1 p 283

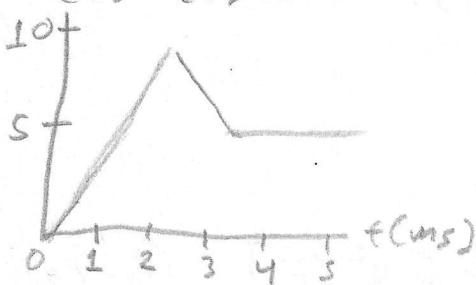

C = 0.5 μF Find current through capacitor

$$\text{we know } i = C \frac{d}{dt} V_c(t)$$

$$\text{for } 0 \leq t \leq 2 \text{ ms}, C \frac{d}{dt} V_c(t) = \frac{10}{2 \times 10^{-3}} = 0.5 \times 10^6 \text{ A}$$

$$\rightarrow i_c(t) = C \frac{d}{dt} V_c(t) = 2.5 \text{ mA}$$

$$\text{for } 2 \leq t \leq 3, \frac{d}{dt} V_c(t) = -5000 \text{ V/s}$$

$$\therefore i_c(t) = (-5000)(0.5 \mu\text{F}) = -2.5 \text{ mA}$$


$$\text{for } 3 \text{ ms} \leq t \quad i_c(t) = 0$$

Example 6-2 $i_c(t) = I_o (e^{-t/T_c}) u(t) \text{ A}$

what's V_c if $V_c(0) = 0 \text{ V}$ (initial condition)

$$\frac{I_o}{C} T_c (V) \text{ recall } V_c(t) = V_c(0) + \frac{1}{T_c} \int_0^t i_c(x) dx = \frac{I_o}{C} \int_0^t e^{-x/T_c} dx$$

$$= \frac{I_o T_c}{C} \left(-1/e^{-t/T_c} - 1 \right) \text{ V}$$

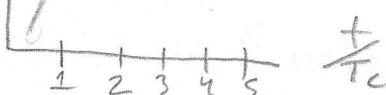


Example 6-4, Find power and energy

(5)

$$\begin{aligned}
 P_C(t) &= i_C(t) V_C(t) \\
 &= I_0(e^{-t/\tau_C}) \frac{I_0 \tau_C}{C} (1 - e^{-t/\tau_C}) \\
 &= \frac{I_0^2 \tau_C}{C} (e^{-t/\tau_C} - e^{-2t/\tau_C}) \text{ W}
 \end{aligned}$$


$$W_C(t) = \frac{1}{2} C V_C^2(t) = \frac{1}{2} C \left[\frac{I_0 \tau_C}{C} (1 - e^{-t/\tau_C}) \right]^2$$

$P_C(t)$ (W)

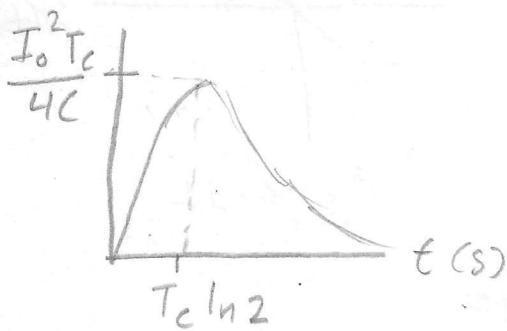

Voltage grows
and $i_C \rightarrow 0$ as $t \rightarrow \infty$

$W_C(t)$ (J)

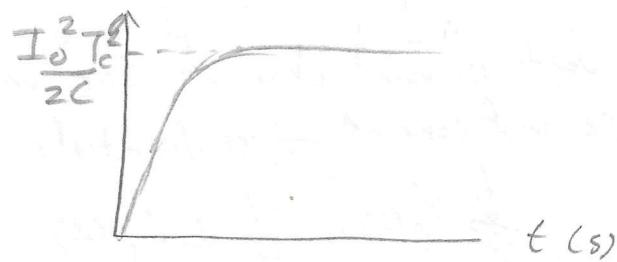

Capacitor stores energy

6-2 The Inductor

$$\bar{H} = \frac{A}{m}, \bar{B} = \frac{N}{m}$$

dynamic circuit element involving the time variation of the magnetic (\bar{B}) field produced by a current

Magnetostatics shows that as magnetic flux ϕ surrounds a wire carrying an electric current, when the wire is wound into a coil, the lines of flux concentrate along the axis of the coil



$$\phi(t) = K_1 N i_L(t) \text{ Wb (V-s)}$$

K_1 = a constant of proportionality

$$\lambda(t) = N \phi(t) \text{ flux linkage (Wb)}$$

N = # of turns (6-13)

$$\text{so } \lambda(t) = [K_1 N^2] i_L(t) \quad (6-14)$$

(6)

We have the Inductance L of the coil

$$\rightarrow L = k_1 N^2 \text{ (H) } (6-15)$$

Henrys

$$\rightarrow \lambda(t) = L i_L(t) \quad (6-16)$$

Inductor's element constraint
Inductor is a Linear element

I-V relationship

We want element characteristic in terms of voltage and current \rightarrow differentiate

$$\frac{d}{dt} \lambda(t) = \frac{d}{dt} L i_L(t) \quad 6-17$$

Faraday's Law, voltage across the Inductor is equal to time rate of change of flux Linkage

$$\rightarrow V_L(t) = L \frac{d}{dt} i_L(t) \quad (6-18)$$

\rightarrow Voltage across the Inductor is zero unless the current is time varying, DC excitation, $i = \text{constant}$, $V_L = 0$

Inductor is a Dynamic element because only changing current produces a nonzero voltage

\rightarrow discontinuous change in current \rightarrow infinite Voltage

$\rightarrow i_L(t)$ must be a continuous function of time t

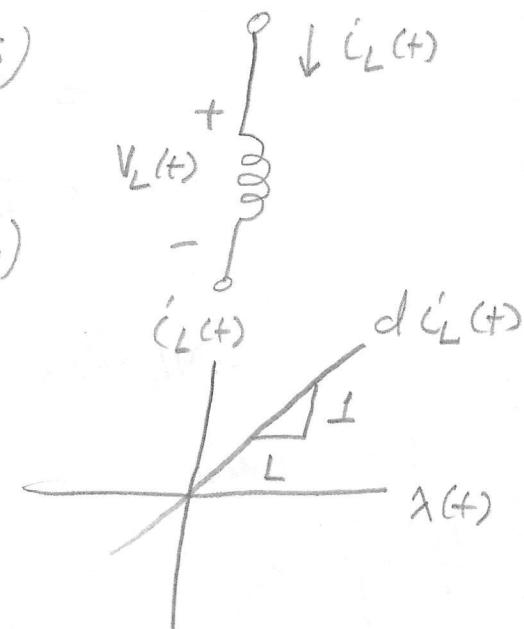


Fig 6-12

to express $i_L(t)$ in terms of $V_L(t)$

(7)

We can write

$$\int L \frac{di_L(t)}{dt} dt = \int V_L(t) dt \quad (6-19)$$

assume $i_L(t_0)$ is known at time t_0 ,
or $\left(\int di_L(t) = \frac{1}{L} \int V_L(t) dt \right)$ (we multiplied by dt and then integrate)

$$\int_{i_L(t_0)}^{i_L(t)} di_L(t) = \frac{1}{L} \int_{t_0}^t V_L(x) dx \quad (6-20)$$

$$i_L(t) - i_L(t_0) = \frac{1}{L} \int_{t_0}^t V_L(x) dx \quad (6-21)$$

$$\rightarrow i_L(t) = i_L(t_0) + \frac{1}{L} \int_{t_0}^t V_L(x) dx$$

t_0 may indicate the flip of a switch, we may write $t_0=0$

$$i_L(t) = i_L(0) + \frac{1}{L} \int_{t_0}^t V_L(x) dx \quad (6-22)$$

$\rightarrow i_L$ and V_L follow passive sign convention

Power and Energy

noting passive sign convention

$$P_L(t) = i_L(t) V_L(t) \text{ W} \quad (6-23)$$

We may write (we can do this)

$$P_L(t) = (i_L(t)) \left[L \frac{d}{dt} i_L(t) \right] = \frac{d}{dt} \left[\frac{1}{2} L i_L^2(t) \right] \quad (6-24)$$

\rightarrow Power can be positive or negative inductor current
and time derivative can have opposite signs

\rightarrow can absorb and deliver Power

\rightarrow can store energy

⑧ To Find the stored Energy

Power is the time rate of change of energy (J/s)

$(P = \frac{dW}{dt})$ The quantity $\left[\frac{1}{2}L i_L^2(t)\right]$ represents the stored energy in the magnetic field of the inductor.

$$\text{energy at time } t, W_L(t) = \frac{1}{2} L i_L^2(t) + \text{constant } J$$

Constant = 0 because energy stored at instant t at which $i_L(t) = 0$, so we have

$$W_L(t) = \frac{1}{2} L i_L^2(t) \quad (6-25)$$

Energy stored is never negative

Inductor returns stored energy when delivering power

(6-25) implies. Inductor current is a continuous function of time because an abrupt change in current causes a discontinuity in energy. \rightarrow which would mean infinite Power

\rightarrow Current is called the state variable of the inductor because it determines the energy state of the element

Example 6-6 p290

$$L = 2 \text{ mH} \quad i_L(t) = 4 \sin 1000t + 1 \sin 3000t \text{ A}$$


$$V_L(t)? \quad V_L(t) = L \frac{di_L}{dt}(t)$$

$$= 0.002 [4(1000) \cos 1000t + 3000 \cos 3000t]$$

$$= 8 \cos 1000t + 6 \cos 3000t \text{ V}$$

There are two sinusoids at different f_s
~~1 Krad~~ AC component is $4X$ bigger than ~~3 Krad~~

AC responses of energy storage elements depend on frequency \sim we can create frequency-selective filters

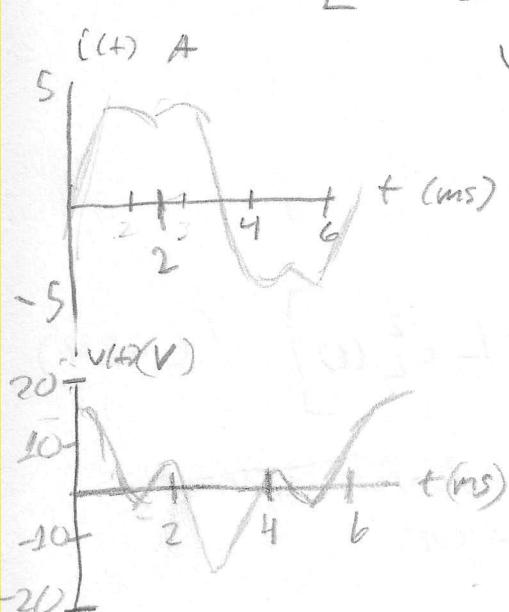

Exercise 6-6, for $t > 0$, $V_L(t) = 20e^{-2000t}$ V, $i_L(0) = 0$ (9)
 $L = 4 \text{ mH}$

(a) current for $t > 0$?

$$\begin{aligned} i_L(t) &= \frac{1}{L} \int_{t_0}^t V_L(x) dx \\ &= \frac{1}{L} \int_{t_0}^t 20e^{-2000x} dx = \frac{1}{L} \cdot \frac{20}{2000} (-1) [e^{-2000x}] \Big|_0^t \\ &= -\frac{20}{2000L} [e^{-2000t} - 1] \\ &= 2.5[1 - e^{-2000t}] \text{ A} \end{aligned}$$

(b) power $t > 0$?

$$\begin{aligned} P_L(t) &= \frac{d}{dt} \left(\frac{1}{2} L i_L^2(t) \right) = \frac{L}{2} \frac{d}{dt} \left((2.5)(1 - e^{-2000t}) \right)^2 \\ &= \frac{L}{2} (2.5)^2 \frac{d}{dt} [1 - e^{-2000t} - e^{-4000t} + e^{-4000t}] \\ &= \frac{L}{2} (2.5)^2 \frac{d}{dt} [1 - 2e^{-2000t} + e^{-4000t}] \\ &= \frac{L}{2} (2.5)^2 [4000e^{-2000t} - 4000e^{-4000t}] \\ &= 50 [e^{-2000t} - e^{-4000t}] \text{ W} \end{aligned}$$

(c) Energy $t > 0$?

$$\begin{aligned} W_L(t) &= \frac{1}{2} L i_L^2(t) \text{ J} \\ &= \frac{L}{2} [1 - 2e^{-2000t} + e^{-4000t}] \text{ J} \end{aligned}$$

(10)

Principle of Duality

KVL	KCL
LOOP	Node
Resistance	Conductance
Voltage Source	Current Source
Thevenin	Norton
Short circuit	Open circuit
Series	Parallel
Capacitance	Inductance
Flux Linkage	charge

if every electrical term in a correct statement about circuit behavior is replaced by its dual, then the result is another correct statement.

Capacitor

1.) $i_C = 0$ unless v_C is changing
Cap acts like open circuit for DC excitations

2.) $v_C(t)$ is continuous
if v_C is discontinuous
 $P_C \rightarrow \infty, i_C \rightarrow \infty$

3.) Cap absorbs Power when charging (storing Energy), releases Energy when delivering Power

Inductor

1.) $v_L = 0$ unless i_L is changing
Coil acts like short circuit for DC excitations


2.) $i_L(t)$ is a continuous function of time, if i_L is discontinuous,
 $P_L \rightarrow \infty, v_L \rightarrow \infty$

3.) Coil absorbs power from the circuit when storing energy.
Then delivers power to the circuit and releases the energy

Energy is conserved

both are passive elements

6-3 Dynamic OP AMP Circuits

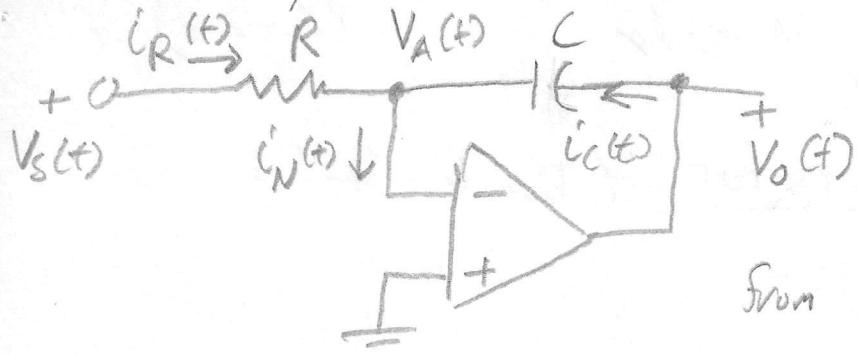


What's the input-output?

KCL at node A

$$i_R(t) + i_C(t) = i_N(t)$$

from element constraints
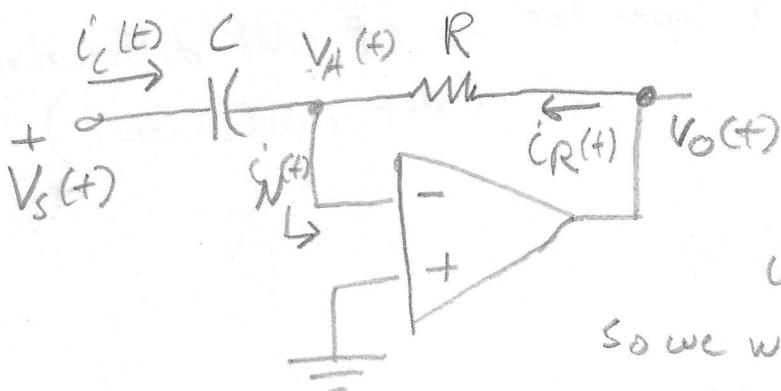
$$i_C(t) = C \frac{d}{dt} [V_o(t) - V_A(t)]$$



$$i_R(t) = \frac{1}{R} [V_s(t) - V_A(t)]$$

Ideal OP AMP constraints

$$i_N(t) = 0, V_A(t) = 0$$

so we write

$$\frac{V_s(t)}{R} + C \frac{d}{dt} V_o(t) = 0$$

rearrange

$$\frac{d}{dt} V_o(t) = -\frac{1}{RC} V_s(t)$$

(It's egregious, but we can (for some reason) multiply by dt and then integrate
→ just like cap and inductor

$$\rightarrow \int dV_o(t) = -\frac{1}{RC} \int V_s(t) dt$$

Assume we know $V_o(t)$ at $t_0 = 0$,

$$\text{Note, } V_A(t) = V_R(t) + V_s(t)$$

$$\text{KVL, } V_o(t) = V_C(t) + V_A(t) \rightarrow V_o(t) = V_C(t)$$

$$\int_{V_o(0)}^{V_o(t)} dV_o(t) = -\frac{1}{RC} \int_0^t V_s(x) dx$$

$$\rightarrow V_o(t) = V_o(0) - \frac{1}{RC} \int_0^t V_s(x) dx$$

$$\text{as } V_o(t) = V_C(t) \rightarrow V_C(0) = 0$$

(12) $\int_0^t V_s(x) dx$ (6-26)

$$V_o(t) = -\frac{1}{RC} \int_0^t V_s(x) dx$$

\rightarrow Inverting integrator (Due to ' $-$ ')

$$\frac{1}{RC} = s^{-1}$$

p294 Interchanging resistor and capacitor \rightarrow OP AMP differentiator
(Not differential)

KCL at A

$$i_R(t) + i_C(+) = i_N(t)$$

Element constraints

$$i_C(+) = C \frac{d}{dt} [V_s(t) - V_A(+)]$$

$$i_R(+) = \frac{1}{R} [V_o(t) - V_A(+)]$$


Ideal OP AMP constraints: $i_N(+) = 0, V_A(+) = 0$

So we write, $\frac{V_o(t)}{R} + C \frac{d}{dt} V_s(t) = 0$

$$\rightarrow V_o(t) = -RL \frac{d}{dt} V_s(t) \quad 6-27$$

$RC = \text{Seconds}$


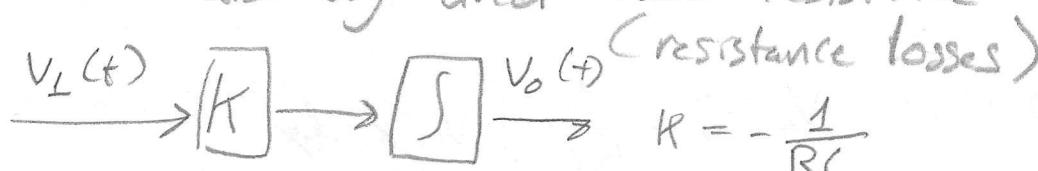
Note, Inductor versions aren't interesting because coils are big and have resistance



p295

Example 6-9

(13)

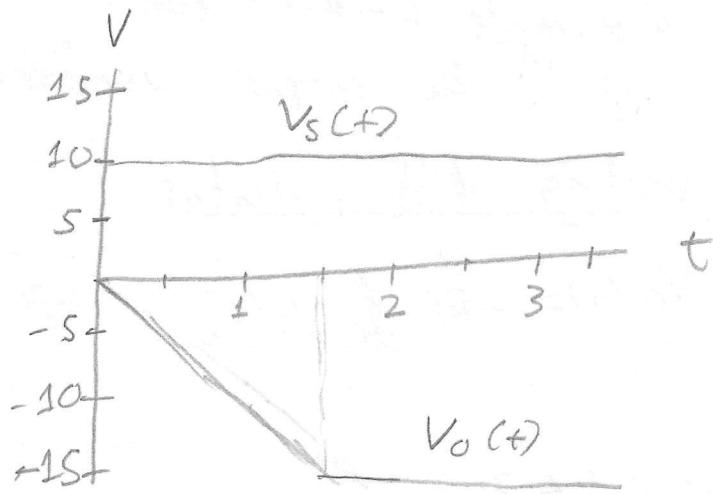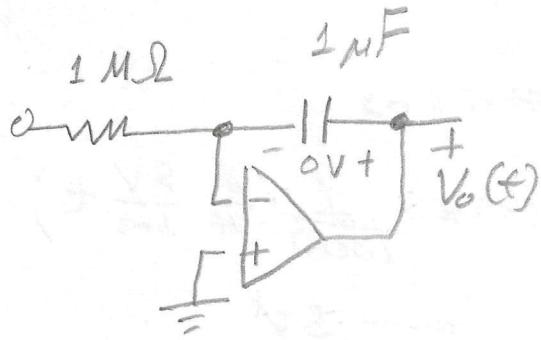

$$V_{CC} = 15V, -V_{CC}$$

$$V_s(t) = 10u(t) \text{ V} \quad V_o(t) ?$$

$$V_o(t) = V_o(0) - \frac{1}{RC} \int_0^t V_s(x) dx = 0 - \frac{1}{RC} \int_0^t 10 dx$$

$$= - \int_0^t 10 dx = -10t \text{ V} \quad t > 0 \quad R \cdot C = 1 \text{ s}$$

slope = $-10 \frac{\text{V}}{\text{s}}$ total Integrator

output is unbounded until $-V_{CC}$ if $-V_{CC} = -15$

$t = 1.5 \text{ seconds}$ till saturate

Example 6-10 p296


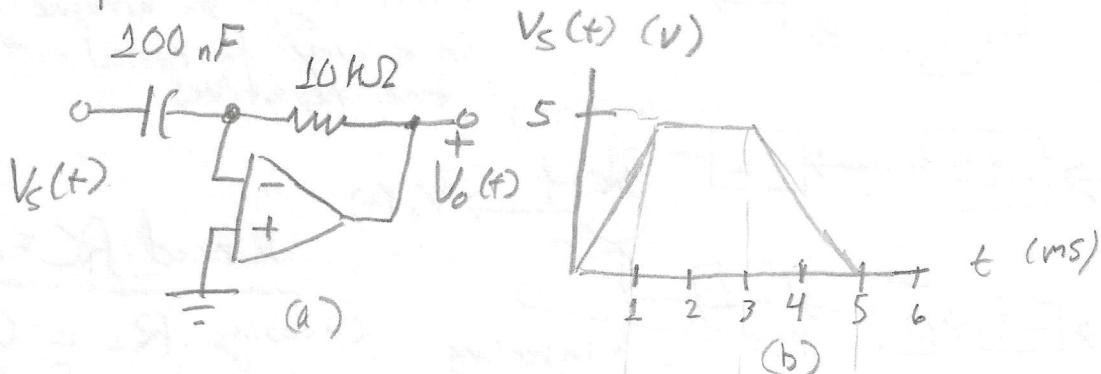


Fig 6-19(a)

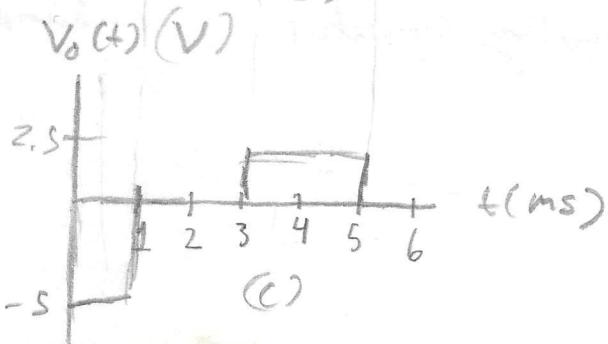

(14)

Example 6-40 continued
What's the output waveform

Inverting Differentiator

$0 \leq t < 1 \text{ ms}$

$$V_o(t) = -RC \frac{d}{dt} V_s(t) \rightarrow V_o(t) = -\frac{1}{1000} \left(\frac{d}{dt} \frac{5V}{1\text{ms}} t \right) \\ = -5V$$

$1 \text{ ms} < t < 3 \text{ ms}$

$$V_o(t) = -\frac{1}{1000} \frac{d}{dt}(5) = 0 \text{ V}, \quad V_o(t) = -\frac{1}{1000} \frac{d}{dt} \frac{-5t}{(3-3)\text{ms}} \\ = +2.5 \text{ V}$$

$t > 5 \text{ ms}, V_o(t) = 0$


Design Example 6-11

Design op amp circuit to implement

$$V_o(t) = 10 V_s(t) + \int_0^t V_s(\tau) d\tau$$

Solution is not unique

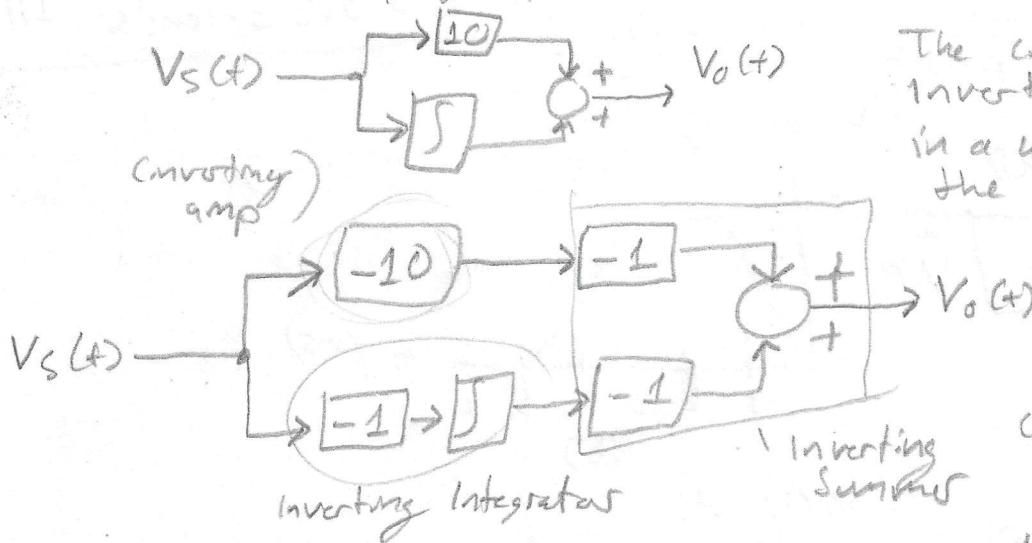Draw block diagram, gain, integrator, summer




The circuits we know are inverting, so arrange it in a way to cancel out the negatives

We need $RC = 1$

choosing R_s or C depends on factors

Like accuracy,
internal resistance of source, output load

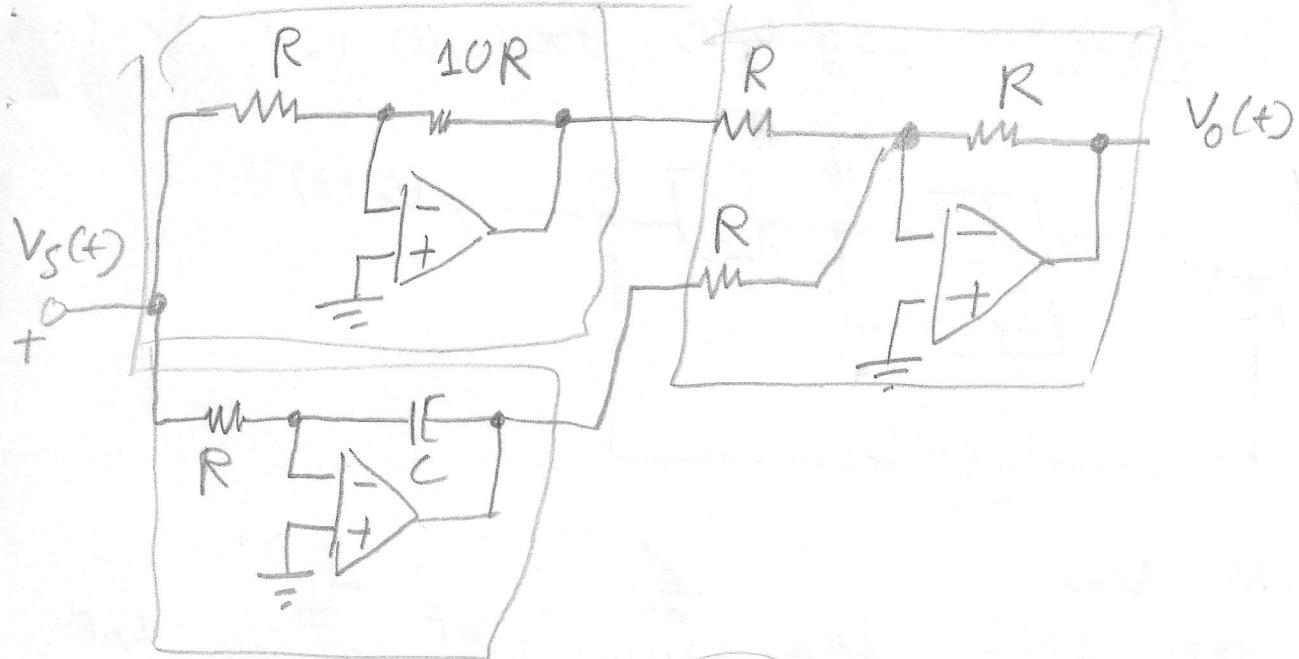

Design 6-42

p298

Differential, integral, and integro-differential equations can be solved using dynamic circuits.

→ Second order system

$$5 \frac{d^2}{dt^2} V_o(t) + 100 \frac{d}{dt} V_o(t) + 5000 V_o(t) = 250 \text{ V}$$

Develop a block-diagram representation of the eq and then design a circuit to solve the equation. [design a circuit w/ output $V_o(t)$]

Highest order derivative, coefficient of 1

$$\frac{d^2}{dt^2} V_o(t) = -20 \frac{d}{dt} V_o(t) - 1000 V_o(t) + 50 \text{ V}$$

Highest order derivative is sum of the 3 inputs

Strategy


$$\int \frac{d^2}{dt^2} V_o(t) = \frac{d}{dt} V_o(t) \quad (1)$$

$$\int \frac{d}{dt} V_o(t) = V_o(t) \quad (2)$$


outputs of Integrators → scale them → Feed back into summer

16

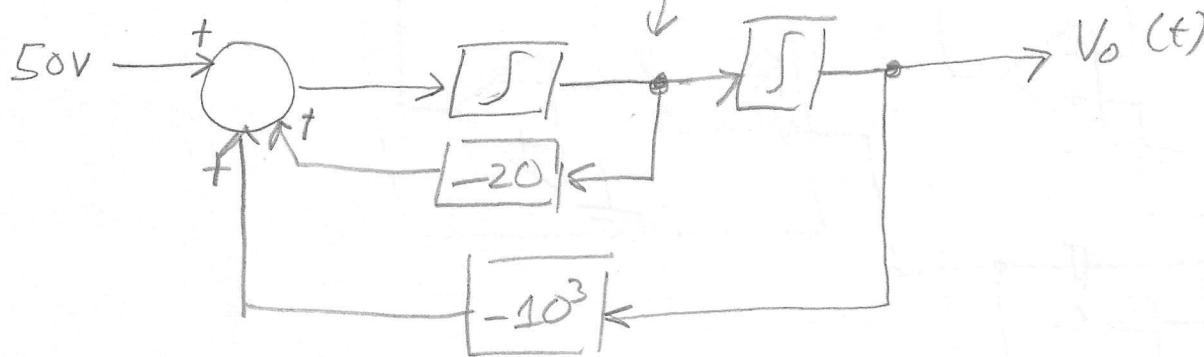
$$\frac{d^2}{dt^2} V_o(t) = -20 \frac{d}{dt} V_o(t) - 1000 V_o(t) + 50 \quad V$$



One possible design

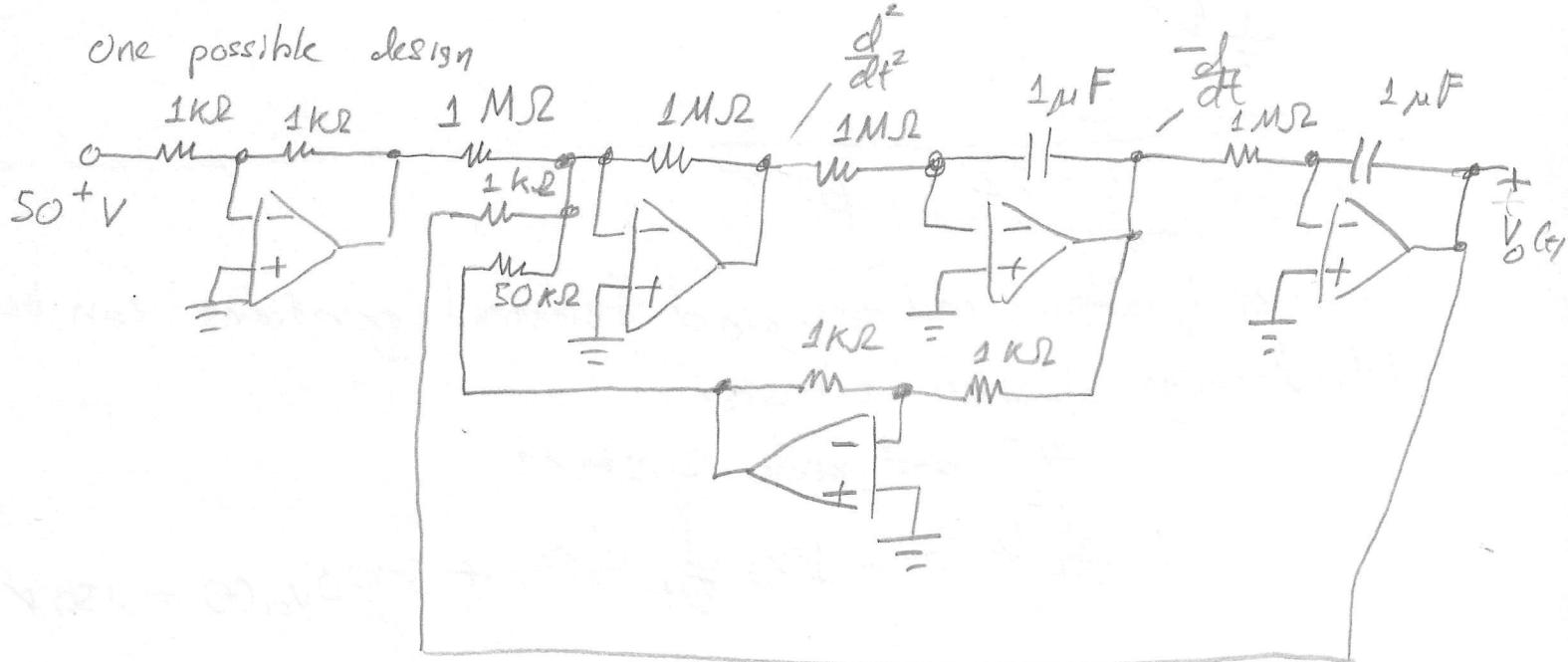

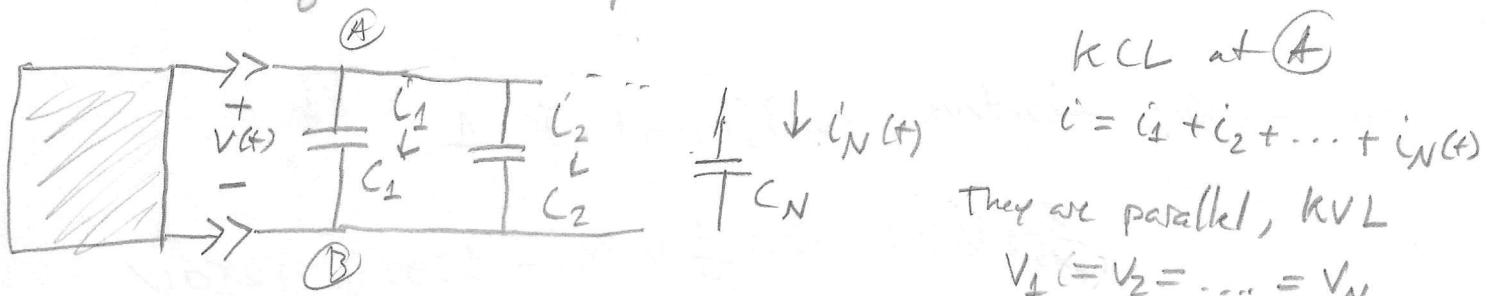6-4 Equivalent Capacitance and Inductance



So then

$$i_K(t) = C_K \frac{d}{dt} V(t)$$

$$\text{and Now KCL: } i(t) = C_1 \frac{d}{dt} V(t) + C_2 \frac{d}{dt} V(t) + \dots + C_N \frac{d}{dt} V(t)$$


$$= (C_1 + C_2 + \dots + C_N) \frac{d}{dt} V(t)$$

$$We \text{ see } C_{eq} = C_1 + C_2 + \dots + C_N \quad (6-28) \quad (17)$$

(for parallel caps)

initial voltage $V(0)$ is the same across the caps

For

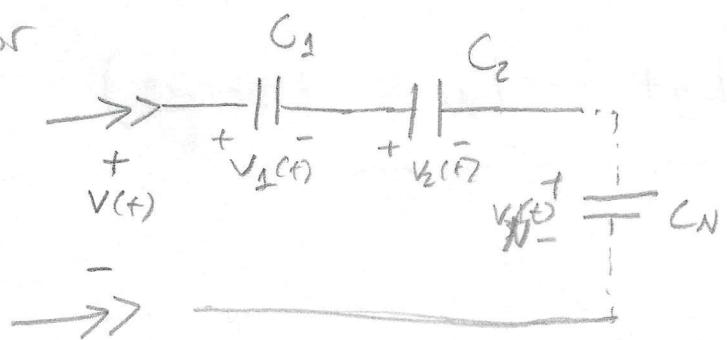

KVL

$$V(t) = V_1(t) + V_2(t) + \dots + V_N(t)$$

We know,

$$i_1 = i_2 = i_3 = \dots = i_N = i(t)$$

So we know $i-V$ relationship

$$V_n(t) = V_n(0) + \frac{1}{C_n} \int_0^t i(x) dx$$

Substitute into KVL,

$$V(t) = V_1(0) + \frac{1}{C_1} \int_0^t i_1(x) dx + V_2(0) + \frac{1}{C_2} \int_0^t i_2(x) dx$$

$$+ \dots + V_N(0) + \frac{1}{C_N} \int_0^t i_N(x) dx$$

$$\rightarrow V(t) = [V_1(0) + V_2(0) + \dots + V_N(0)] + \left(\frac{1}{C_1} + \frac{1}{C_2} + \dots + \frac{1}{C_N} \right) \int_0^t i(x) dx$$

From observation

$$\frac{1}{C_{eq}} = \frac{1}{C_1} + \frac{1}{C_2} + \dots + \frac{1}{C_N} \quad (\text{series})$$

The initial voltage on C_{eq} is the sum of the initial voltages on each of the original N caps

18

if we replace cap for coils

$$\text{KVL } V(t) = L_1 \frac{di_1(t)}{dt} + L_2 \frac{di_2(t)}{dt} + \dots + L_N \frac{di_N(t)}{dt}$$

$$= (L_1 + L_2 + \dots + L_N) \frac{di(t)}{dt}$$

So

$$L_{eq} = L_1 + L_2 + \dots + L_N \quad (\text{series})$$

for Parallel,

$$\text{KCL } i(t) = i_1 + i_2 + \dots + i_N$$


$$= i_1(0) + \frac{1}{L_1} \int_0^t v(x) dx + i_2(0) + \frac{1}{L_2} \int_0^t v(x) dx$$

$$+ \dots + i_N(0) + \frac{1}{L_N} \int_0^t v(x) dx$$

$$= [i_1(0) + i_2(0) + \dots + i_N(0)] + \left(\frac{1}{L_1} + \frac{1}{L_2} + \dots + \frac{1}{L_N} \right) \int_0^t v(x) dx$$

$$\text{So } \frac{1}{L_{eq}} = \frac{1}{L_1} + \frac{1}{L_2} + \dots + \frac{1}{L_N} \quad (\text{parallel})$$

A note about DC responses

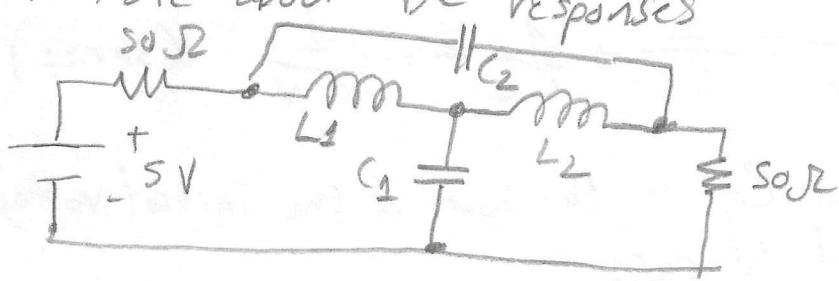

This gives us initial operating points (ICs) under conditions for transient responses that begin at $t=0$

