

I Skipped the rest of Chp 2

(11)

3-1 Node-Voltage Analysis p74

From 2-3, circuit behavior is based on constraints of
2 types

- 1) connection constraints Kirchhoff's Laws
- 2) Power constraints, element i-v relationships


→ A circuit with 6 devices gives us 12 equations
with 12 unknowns

We want to reduce the number of equations
that must be solved simultaneously

→ Using node voltages instead of element voltages as circuit
variables can reduce the number of equations that must
be solved simultaneously

→ To define a set of node voltages, we first select
a reference node.

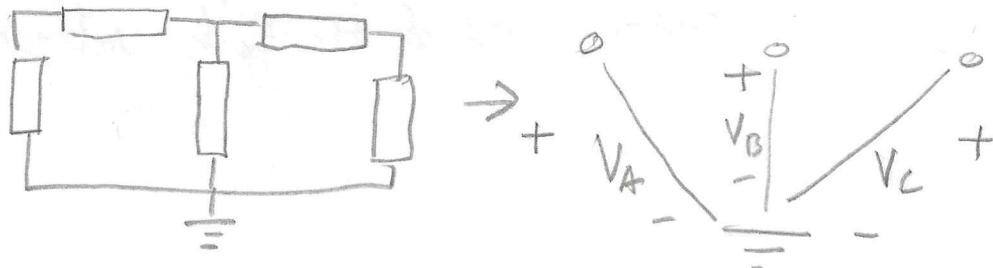Node voltages: voltages between the remaining nodes
and the selected reference node



(12)

If the k th two-terminal element is connected between nodes X and Y , then the element voltage can be expressed in terms of the two node voltages as


$$V_k = V_x - V_y \quad (3-1)$$

where X is the node connected to the positive reference for element voltage V_k

$$\text{if } V_y = 0 \rightarrow V_k = V_x$$

$$\text{if } V_x = 0 \rightarrow V_k = -V_y$$

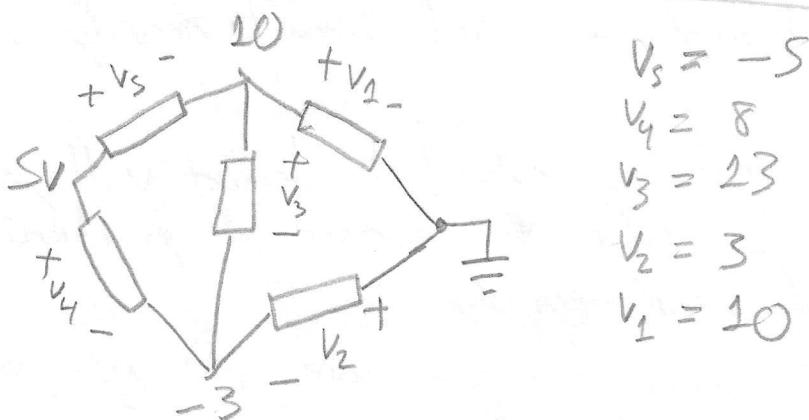
Voltage across an element can be expressed as the difference of two node voltages, one may be zero



Formulating Node-Voltage Equations p 75

circuit description using node voltages

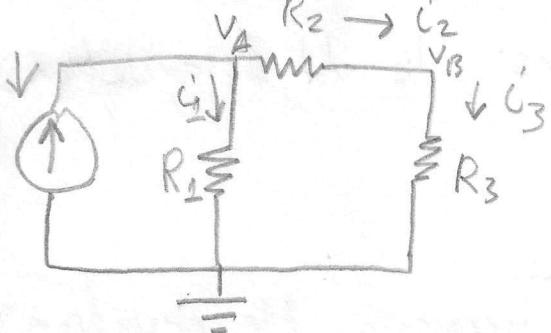→ use node analysis to express the element voltages in terms of the node voltages



KCL

A: $-i_0 - i_1 - i_2 = 0$

B: $i_2 - i_3 = 0$

(3-2)

3-5 Use Node analysis, so Look at Node A

Then $i_1 = \frac{V_A}{R_1}$

$i_2 = \frac{1}{R_2} (V_A - V_B) \quad (3-3)$

$i_3 = \frac{V_B}{R_3}, \quad i_0 = -i_1$

We have 4 i_s and 2 node voltages, substitute device constraints into KCL connection constraints gets

A: $i_s - \frac{V_A}{R_1} - \frac{1}{R_2} (V_A - V_B) = 0$

B: $\frac{1}{R_2} (V_A - V_B) - \frac{V_B}{R_3} = 0$

Rewrite

A: $V_A \left(\frac{1}{R_1} + \frac{1}{R_2} \right) - V_B \left(\frac{1}{R_2} \right) = i_2 \quad (3-4)$

$-V_A \frac{1}{R_2} + V_B \left(\frac{1}{R_2} + \frac{1}{R_3} \right) = 0$

We have eliminated the currents, we have reduced the circuit description to two linear equations. We used KCL, and implicitly used KVL.

[4 Step Process on p 76]

- 1) Pick a reference, then identify Node Voltages
- 2) KCL at nodes

- 3) I-V relationships of elements to express i in terms of V

4) Insert (3) into KCL

(14)

We went from $2E$ equations to $N-1$ equations
~~elements~~

→ We have several examples of arranging the equations as a matrix arrangement, which is great for organization p77 - p78

$$i = \frac{1}{R} (V_A - 0)$$

$$i = \frac{1}{R} (V_A - V_B)$$

The pattern for node equation follows from these observations.
 The sum of the currents leaving any node A via resistance is

- 1.) V_A times the sum of conductances connected to node A
- 2.) minus V_B times the sum of conductances connected between nodes A and B
- 3.) minus similar terms for all other nodes connected to node A by conductances


KCL, sum of currents leaving node A via R_S plus sum of currents directed away from node A by ind. current sources must equal zero

→ We can write Node-Voltage equations by inspection
 [No KCL constraints, or element equations, or labeling currents]

p79 example

3-8

p79

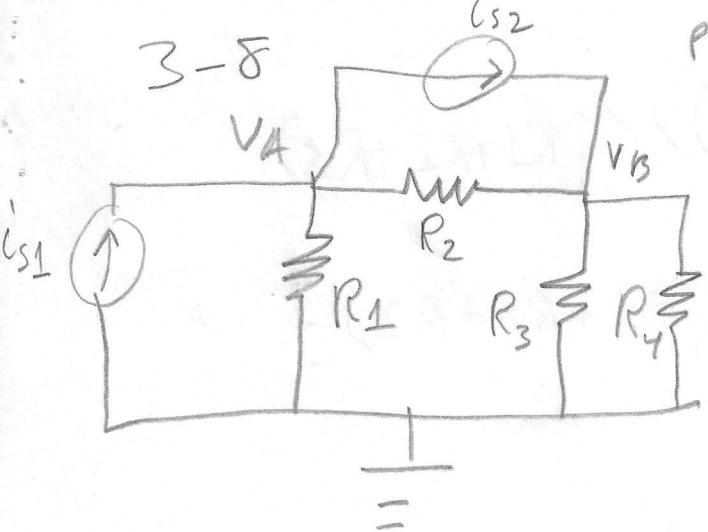

Start w/ A, sum of conductances, G_1 , connected to A

minus V_B (conductance between A and B)

balances currents into A

$$\Rightarrow (R_1^{-1} + R_2^{-1})V_A - (R_2^{-1})V_B - i_{S1} + i_{S2} = 0$$

$$B \rightarrow (R_2^{-1} + R_3^{-1} + R_4^{-1})V_B - (R_2^{-1})V_A - i_{S2} = 0$$

So we have

$$(R_1^{-1} + R_2^{-1})V_A - (R_2^{-1})V_B = i_{S1} - i_{S2}$$

$$-(R_2^{-1})V_A + (R_2^{-1} + R_3^{-1} + R_4^{-1})V_B = i_{S2}$$

→ Symmetrical matrix

Solving Linear Algebraic Equations p80-p81

In MatLab, to solve

$$(R_1^{-1} + R_2^{-1})V_A - R_2^{-1}V_B = i_{S1}$$

$$-R_2^{-1}V_A + (R_2^{-1} + R_3^{-1})V_B = i_{S2}$$

First, define symbolic parameters

syms R1 R2 R3 iS real

$$A = [(1/R1 + 1/R2) - 1/R2; -1/R2 (1/R2 + 1/R3)];$$

$$B = [iS; 0];$$

$$X = A \setminus B;$$

46

$$X(1) = (R_1 * i_S * (R_2 + R_3)) / (R_1 + R_2 + R_3)$$

$$V_A = X(1)$$

$$X(2) = (R_1 * R_3 * i_S) / (R_1 + R_2 + R_3)$$

$$V_B = X(2)$$

now we have

$$V_1 = V_A \quad V_2 = V_A - V_B \quad V_3 = V_B$$

Do the
MatLab

$$i_1 = \frac{V_A}{R_1} \quad i_2 = \frac{V_A - V_B}{R_2} \quad i_3 = \frac{V_B}{R_3}$$

Node Analysis w/ Voltage Sources p84

→ Adding voltage sources to circuits modifies node analysis procedures because current thru a voltage source is not directly related to the voltage across it

Method 1 Source transformation

Method 2, don't need a resistor in series

make node B the reference $\rightarrow V_A = V_S$, we know voltage A

N-2 remaining equations, V_A is known

Method 3: A or B can't be reference, V_S has no R in series \rightarrow Combine A and B into Super Node


N-3 node equations and 1 super node equation

Do all the examples for these methods and PSPICE later [p85-91]

Examples for Node Analysis of Voltage Sources


16.1

3-14

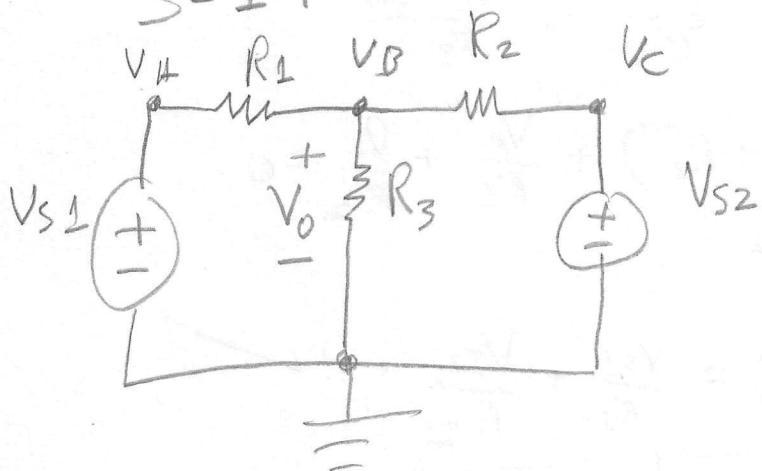


Use node-voltage analysis to find V_o in 3-14

→ use method 1
source transformation

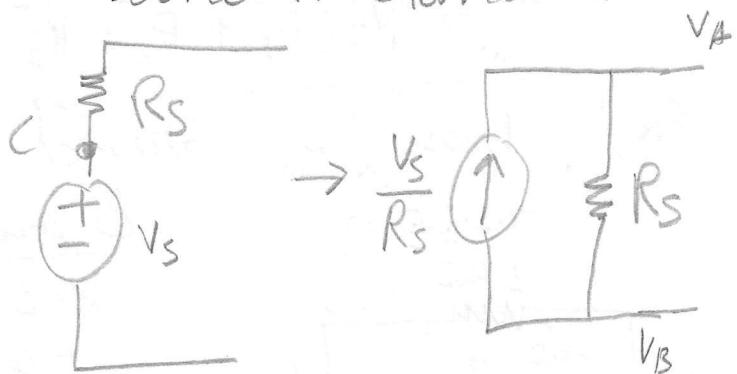

So now we have

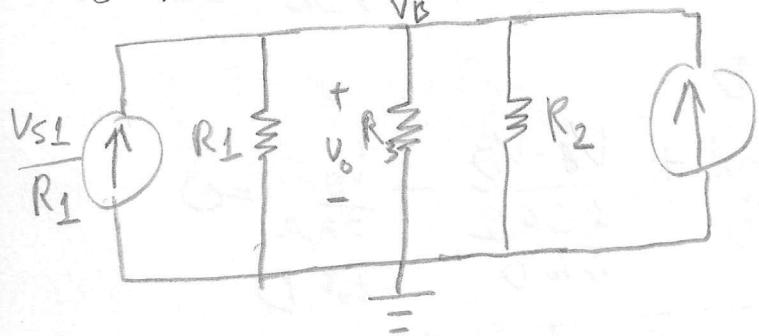

So from observation

$$0 = V_B(R_1 + R_2 + R_3) - \frac{V_{S1}}{R_1} - \frac{V_{S2}}{R_2}$$


$$\frac{V_{S1}}{R_1} = V_B$$

$$So \quad V_o = \frac{\frac{V_{S1}}{R_1} + \frac{V_{S2}}{R_2}}{(R_1 + R_2 + R_3)}$$


Method 2, make B the reference

Super Node


Recall the Methods

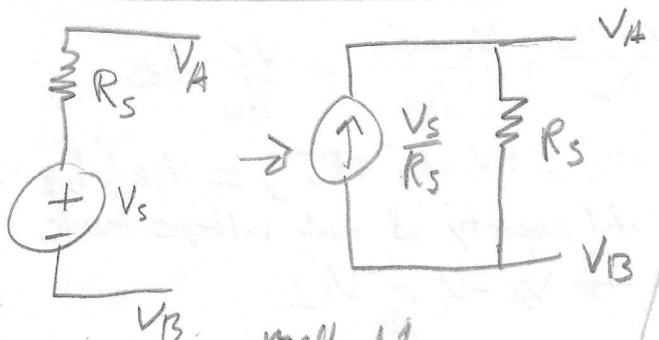

V_B method 1

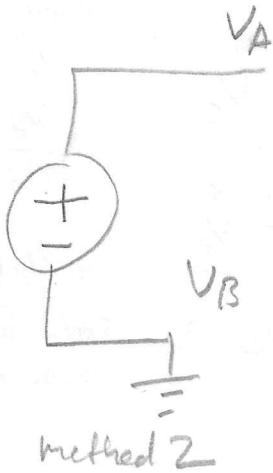

method 2

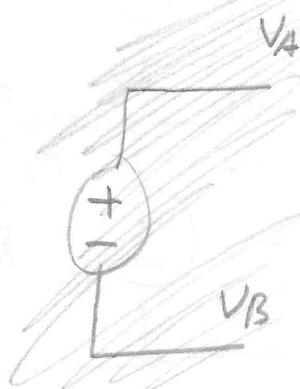


method 3

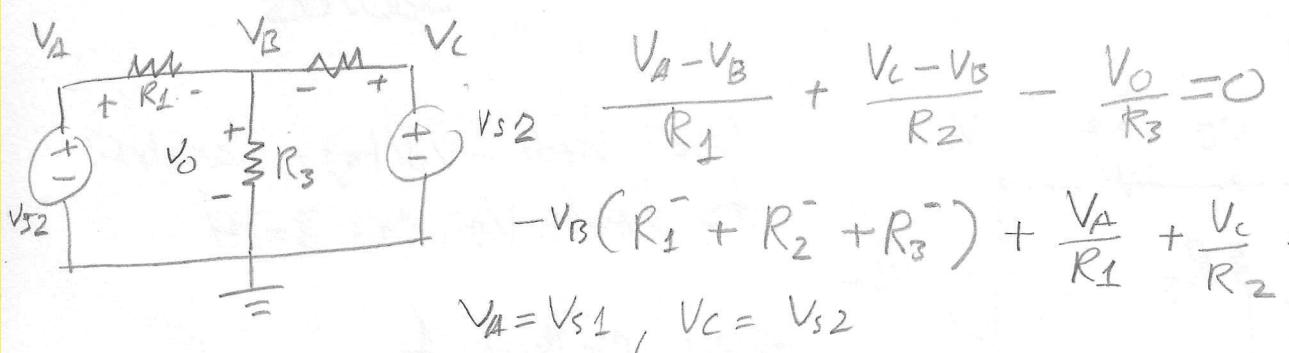16.2

Use Method 2


KCL at B $\rightarrow i_1 + i_2 - i_3 = 0$



$$\therefore V_B(R_1 + R_2 + R_3) = \frac{V_{S1}}{R_1} + \frac{V_{S2}}{R_2} \quad \checkmark$$

(Ex) choose a Ground wisely

3-15

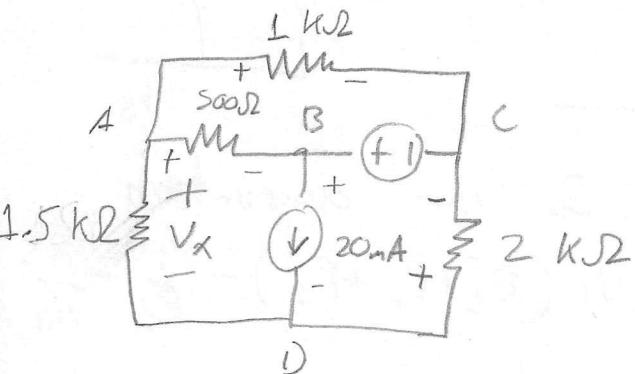

C should be ground

KCL at A

$$-(i_4 - i_1) - i_2 = 0$$

$$-\left(\frac{V_A - V_D}{1.5k\Omega}\right) - \frac{V_A - V_B}{500} - \frac{V_A - V_C}{1k\Omega} = 0$$


KCL at D

$$+20mA + \frac{V_A - V_D}{1.5k\Omega} - \frac{V_D}{2k\Omega} = 0$$

into D into D at D

3-17

V_{S1}

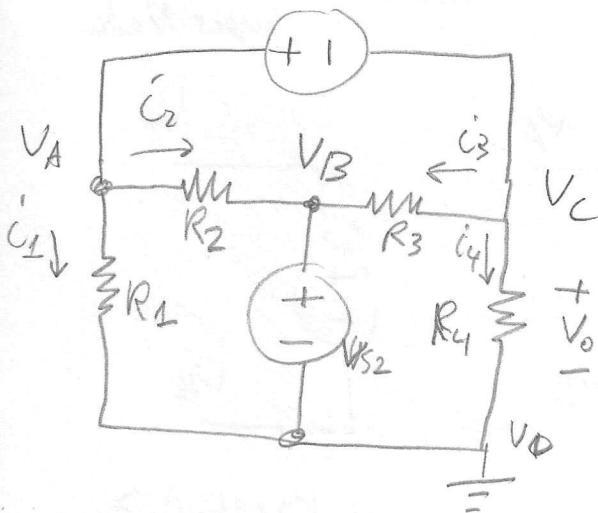

Node-Voltage Equations

Method 3, 3

needed, we used 2 already

make a supernode boundary

Supernode equation KCL

$$i_1 + i_2 + i_3 + i_4 = 0$$

$$\frac{V_A}{R_1} + \frac{V_A - V_S2}{R_2} + \frac{V_C - V_S2}{R_3} + \frac{V_C}{R_4} = 0$$

$$\rightarrow V_A(R_1 + R_2) + V_C(R_3 + R_4) = V_S2(R_2 + R_3)$$

Apply fundamental property of node voltages inside supernode $\rightarrow V_A - V_C = V_{S1}$

→ ungrounded voltage source constrains the difference between the two unknown node voltages inside the supernode, so now we need 2 equations and 2 unknowns

$$\text{so } V_A(R_1^- + R_2^-) + V_c(R_3^- + R_4^-) = V_{S2}(R_2^- + R_3^-)$$

$$\text{and } V_A - V_c = V_{S1} \rightarrow V_A = V_{S1} + V_c$$

done

p92

3.2 Mesh - Current Analysis

mesh currents are analysis variables that are useful in circuits containing many elements connected in series

Loop

closed path formed by passing through an ordered sequence of nodes w/o passing thru any node more than once

mesh

A loop not enclosing an element

mesh current restricted to planar circuit

(No cross overs)
(window pane)
circuit

→ To define a set of variables, associate a mesh current with each window pane and assign a reference direction

All mesh are taken clockwise

Mesh currents are variables not representing actual physics phenomenon

→ Elements around the perimeter are contained in only one mesh, interior elements are in two meshes

→ Element with two meshes, two meshes circulate in opposite direction (the mesh currents)

KCL: net current thru element is the difference of the two mesh currents

∴ If the k th two-terminal element is contained in meshes X and Y , then the element current can be expressed in terms of the two mesh currents as

$$i_k = i_X - i_Y \quad 3-9$$

(18)

where X is the mesh whose reference direction agrees with the reference direction of i_K

3-9 is a KCL constraint at the element level
if the element is in only 1 mesh, then


$$i_K = i_X \text{ or } i_K = -i_X$$

depending on whether the reference direction for the element current agrees or disagrees with the reference direction of the mesh current

$\rightarrow i_K$ can be expressed in terms of no more than two mesh currents

Ex p 93

3-20

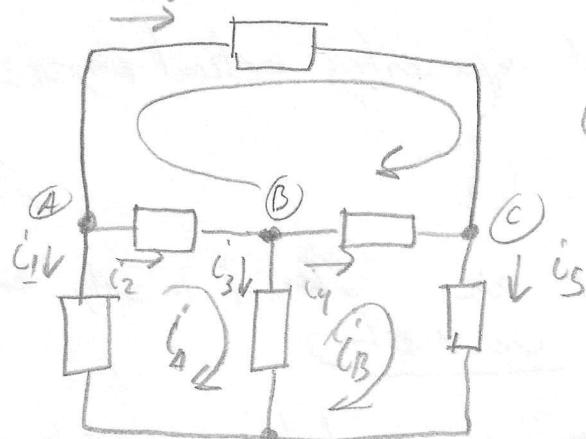

$$i_A = 10 \text{ A}$$

$$i_B = 5 \text{ A}$$

$$i_C = -3 \text{ A}$$

$$i_1 = -10$$

$$i_2 = 13$$

$$i_3 = 5$$

$$i_4 = 8$$

$$i_5 = 5$$

$$i_6 = -3$$

KCL A

$$-i_1 - i_2 - i_6 = 0$$

KCL B

$$i_2 - i_3 - i_4 = 0$$

KCL C


$$i_6 + i_4 - i_5 = 0$$

Strategy

Want to use mesh currents to formulate circuit equations

\rightarrow use elements and connection constraints, except KCL constraints are not explicitly written

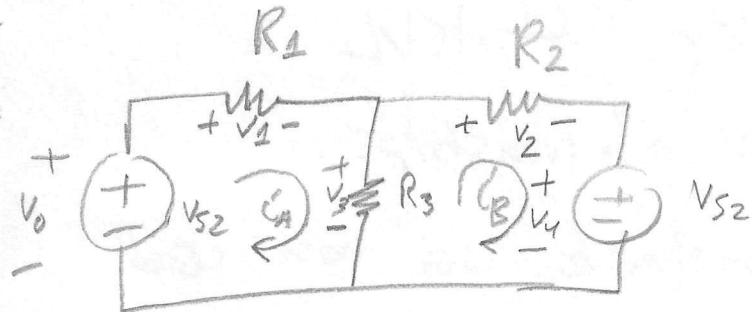\rightarrow use fundamental property of mesh currents to express the element voltages in terms of the mesh currents



If we express element voltages in terms of mesh currents

We can avoid using the element currents and work only with element voltages and mesh currents

We write KVL constraints around each mesh

$$\text{Mesh A: } -V_0 + V_1 + V_3 = 0$$

$$\text{Mesh B: } V_2 + V_4 - V_3 = 0$$

Use fundamental property of mesh currents, write element voltages in terms of the mesh currents and input voltages

$$V_1 = R_1 i_A$$

$$V_0 = V_{S1}$$

$$V_2 = R_2 i_B$$

$$V_4 = V_{S2}$$

$$V_3 = R_3 (i_A - i_B)$$

So rewrite KVL equations

$$-V_{S1} + R_1 i_A + R_3 (i_A - i_B) = 0$$

$$R_2 i_B + V_{S2} - R_3 (i_A - i_B) = 0$$

$$V_{S1} = i_A (R_1 + R_3) - R_3 i_B$$

$$V_{S2} = i_A R_3 - i_B (R_3 + R_2)$$

(3-12)

(20) every method must satisfy KCL, KVL
and element I-V relationships.

To write the element constraints we have used

$$\text{KCL} \rightarrow i_1 = i_A, i_2 = i_B, i_3 = i_A - i_B$$

\rightarrow mesh current analysis implicitly satisfies KCL when element constraints are expressed in terms of the mesh currents

\rightarrow fundamental property of mesh currents ensures that KCL constraints are satisfied

[We already did fundamental property of node voltages.]

$$(3-4) : V_A(R_1 + R_2) - V_B R_2 = i_S \\ - R_2 V_A + V_B (R_2 + R_3) = 0$$

Mesh Current Summary

- 1.) Identify a mesh current with every mesh and a voltage across every circuit element
- 2.) Write KVL connection constraints in terms of element voltages around every mesh
- 3.) Use KCL and the I-V relationships of the elements to express the element voltages in terms of the mesh currents
- 4.) Substitute the element constraints from step 3 into step 2 connection constraints \rightarrow then arrange result equations to standard form

recall,

elements nodes

$$\# \text{ of KVL constraints} \leq E - N + 1$$

Window panes in a planar circuit generate $E - N + 1$ independent mesh currents

→ Mesh analysis is for circuit w/ many elements

(E large) connected in series (also N large)

p94 Writing Mesh-Current Equations by Inspection

from equations (3-12), there is a similar coefficient

symmetry observed in node equations

$$(3-12) \quad \begin{aligned} (R_1 + R_3)i_A - R_3 i_B &= V_{S1} \\ -R_3 i_A + (R_2 + R_3)i_B &= -V_{S2} \end{aligned}$$

$$\begin{aligned} (R_1 + R_2)v_A - R_2 v_B &= i_S \\ -R_2 v_A + (R_2 + R_3)v_B &= 0 \end{aligned}$$

→ We can see R_3 is in both meshes

→ $(R_1 + R_3)i_A$ and $(R_2 + R_3)i_B$

Sum of R_S
in mesh A

Sum of R_S'
in mesh B

This occurs in planar circuits containing R_S and independent voltage sources

consider R_1 it contained in mesh A only

$$\rightarrow V = R(C_A - 0) = R C_A$$

or R_1 contained in A and adjacent B

$$V = R(C_A - C_B)$$

② Following conclusions


Voltage across R_5 in mesh A involves

- 1.) i_A times sum at R_5 in mesh A
- 2.) minus i_B times sum at R_5 common to mesh A and mesh B
- 3.) minus similar terms for any other mesh adjacent to mesh A with a common resistance

KVL must be satisfied

Ex 3-22 V_{S1}

From inspection

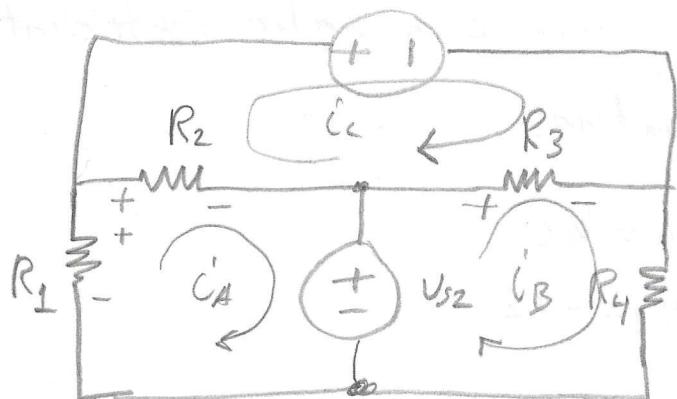

$$A: i_A(R_1 + R_2) - i_C(R_2) + V_{S2} = 0$$

$$B: i_B(R_3 + R_4) - i_C(R_3) - V_{S2} = 0$$

$$C: i_C(R_2 + R_3) - i_A(R_2) - i_B(R_3) + V_{S1} = 0$$

$$\rightarrow \begin{bmatrix} R_1 + R_2 & 0 & -R_2 \\ 0 & R_3 + R_4 & -R_3 \\ -R_2 & -R_3 & R_2 + R_3 \end{bmatrix} \begin{bmatrix} i_A \\ i_B \\ i_C \end{bmatrix} = \begin{bmatrix} -V_{S2} \\ +V_{S2} \\ -V_{S1} \end{bmatrix}$$

Symmetrical

P97

Mesh Equations with Current Sources

Voltage across current sources is not related to its current.

→ To deal with Voltage sources (Methods)

- 1) if the current source B is parallel with a resistor → equivalent source transform
→ eliminates a mesh and reduces # of equations by 1
- 2) if the current source is contained in only 1 mesh, then that mesh current B determined by the source current
→ Move known mesh to source side in final step
then proceed as normal
→ 1 less equation than # of meshes
- 3) if the current source is not in parallel with a resistor, or in 2 meshes, create a Supernode by excluding the current source and any elements connected in series with it
→ write a mesh equation around the supernode using i_A and i_B
→ Proceed as normal
we have 1 equation short coz A and B are included in the supernode

→ Fundamental Property of mesh currents says


$$i_A - i_B = i_S$$

This is one extra relationship needed


(24)

3-23 Super mesh


Super mesh

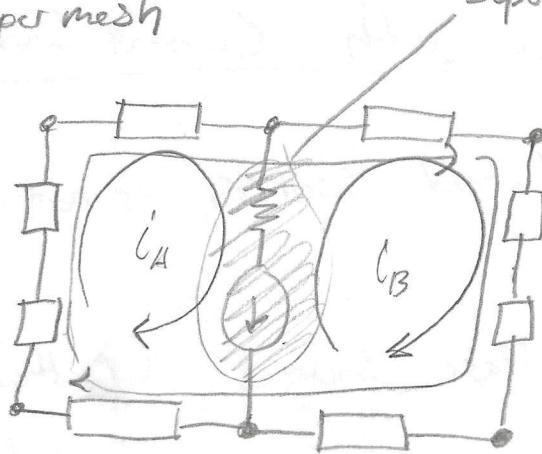

Ex

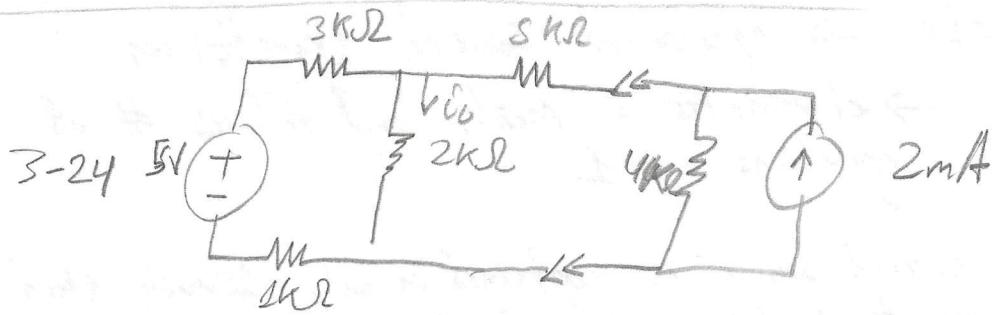

Method 1 → Source Transformations

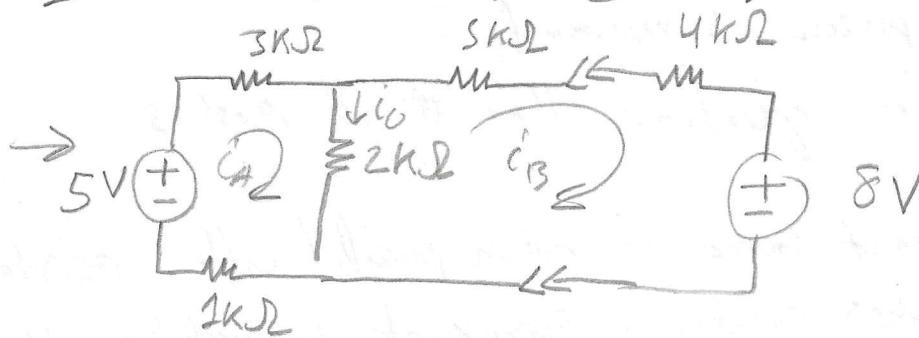

$$\rightarrow A: i_A(6k) - i_B(2k) = 5V$$

$$i_B(11k) - i_A(2k) = -8$$

$$\epsilon_0 = i_A - i_B$$

Ex (3-10)

3-25

method 3: Supermesh

(25)


Voltages around supermesh

$$i_c(R_3 + R_4) + i_b(R_1 + R_2) - i_s_1(R_1 + R_3) = 0$$

for supermesh, when forming KVL use i_c and i_b

method 2 don't forget
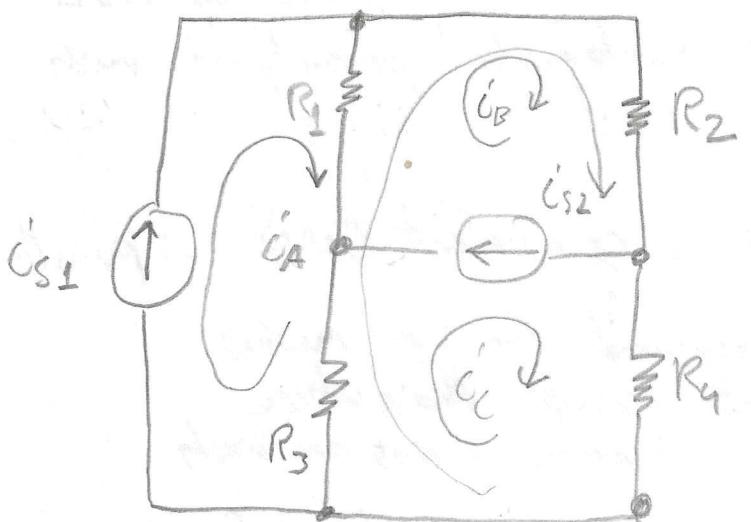
$$i_A = i_{s1} \quad i_{s2} = i_b - i_c$$




$$i_c(R_3 + R_4) + (i_{s2} + i_c)(R_1 + R_2) - i_{s1}(R_1 + R_3) = 0$$

$$i_c(R_3 + R_4 + R_1 + R_2) = i_{s1}(R_1 + R_3) - i_{s2}(R_1 + R_2)$$

$$V_0 = R_4 i_c$$

Ex 3-19

(3-27)

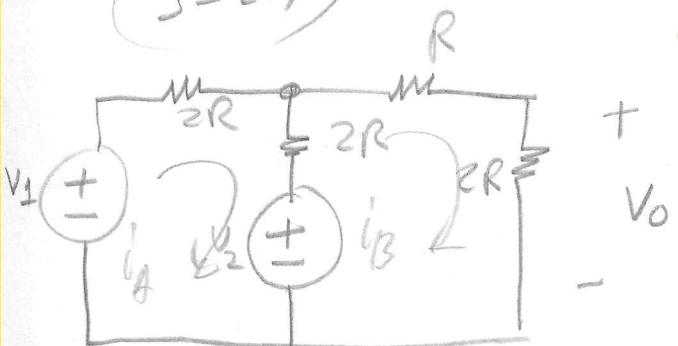

A: KVL

$$-v_1 + i_A(2R) + (2R)(i_A - i_B)$$

by inspection!

$$i_A(2R + 2R) - i_B(2R) - v_1 + v_2 = 0$$

$$i_B(R + 2R + 2R) - i_A(2R) - v_2 = 0$$

- (26) Summary of Mesh-Current Analysis p100
- Mesh-current equations can always be formed by KVL + element constraints + fundamental property of mesh currents
- 1.) Simplify the circuit \rightarrow equivalent series or parallel
 - 2.) Mesh equations required for super meshes and all other meshes except those where current sources are contained in only one mesh
 - 3.) Use KVL to write mesh equations for the meshes identified in (2), express element voltages in terms of mesh currents or voltage produced by independent voltage sources
 - 4.) Write expressions relating the mesh currents to the currents produced by independent current sources
 - 5.) Substitute expressions from (4) into mesh equations from (3), make equation in standard form
 - 6.) Solve

3-3 Linearity Properties

A circuit is linear if it can adequately be modeled using only linear elements and independent sources.

→ Outputs are linear functions of inputs

Circuit inputs are signals produced by external sources

→ A function is said to be linear if it has two properties

1.) Homogeneity, output is proportional to input

$$f(kx) = kf(x) \quad (3-16)$$

2.) Additivity, output of two (or more) inputs is equivalent to the addition of each signal applied individually.

$$f(x+y) = f(x) + f(y) \quad (3-17)$$

For circuit analysis

homogeneity is called proportionality

additivity is called superposition


② p 101 the proportionality Property

→ applies to circuits w/ 1 input


linear resistive circuits

Input-output relationship

$$y = kx$$

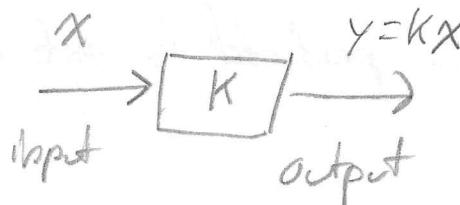


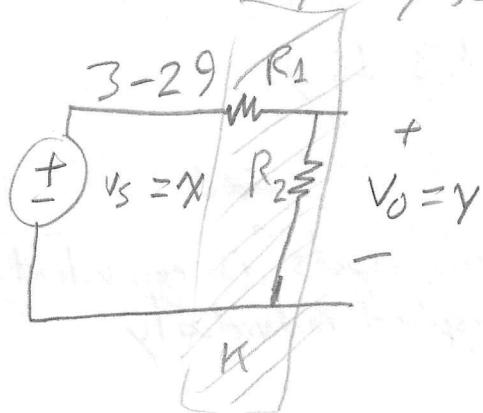
→ ratio of output and input dominates much of circuit design and analysis, for now we are restricted to $K \leq 1$



Proportionality only applies when input/output are current or voltage

→ Not apply to output power as $P = IV$

→ not linearly related to input I or V

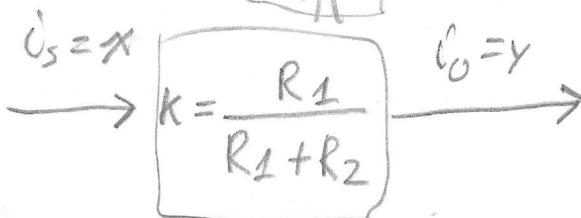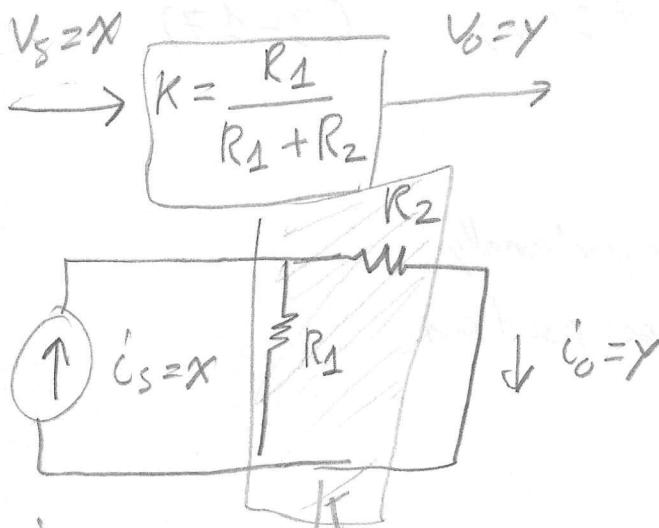

$$\text{Voltage division} \rightarrow V_o = \left(\frac{R_2}{R_1 + R_2} \right) V_s$$

$$\begin{aligned} x &= V_s \\ y &= V_o \end{aligned}$$

Current division

$$i_o = \left(\frac{R_1}{R_1 + R_2} \right) i_s$$

$$x = i_s, y = i_o \quad k = \frac{R_1}{R_1 + R_2}$$

Ex

$$K = \frac{V_o}{V_s} = 0.67$$

$$\rightarrow K = 0.67 = \frac{R_2}{R_1 + R_2} \rightarrow R_2 = K R_1 + R_2 K$$

$$R_2 - R_2 K = K R_1$$

$$R_2 = \frac{K R_1}{(1-K)}$$

tolerance of 5%


$$\rightarrow R_2 = 20 k\Omega$$

$$R_1 = 10 k\Omega$$

$$= 2 R_1$$

if 20% try $R_2 = 68 k\Omega, R_1 = 33 k\Omega$

Ex 3-12 p 102 7th ed

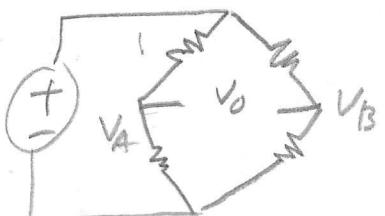

2 Voltage dividers

 $V_A - V_B$, fundamental property of node voltages

Unit output Method

$$Y = KX \quad (3-18)$$

Find K by assuming output of one unit and determine input required to produce that unit output.

1.) Unit output assumed $V_O = 1V$ or $C_O = 1A$

2.) The input required to produce that unit output is found by KCL, KVL, Ohms Law

3.)


$$K = \frac{\text{Output}}{\text{Input}} = \frac{1}{\text{Input for unit output}}$$

(30)

3-13 p103


Fig 3-21

use unit output to find

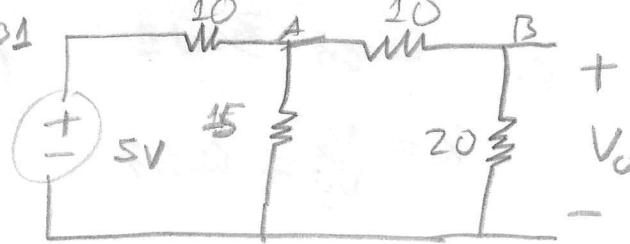 V_o so assume $V_o = 1$

$$\text{Then } i_0 = \frac{1}{20} = 0.05 \text{ A}$$

KCL at B →

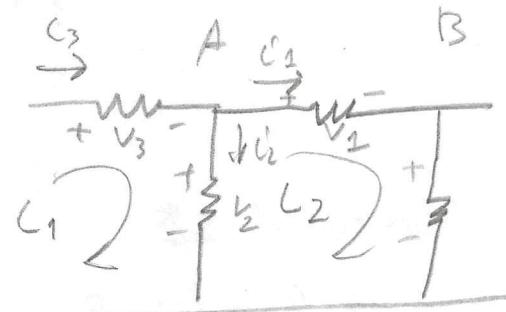

L2 KVL

$$V_1 + V_o - V_2 = 0 \rightarrow R_2 i_2 = V_1 + V_o$$

$$= 1.5 = V_2$$

$$i_2 = \frac{1.5}{20} = 0.075 \text{ A}$$

$$\therefore i_3 = i_2 + i_1 = 0.15 \text{ A}$$

$$V_3 = 1.5 \text{ V} \quad V_s = V_3 + V_2 = 3 \text{ V} \rightarrow k = \frac{1}{3}$$

p105 Additivity Property

any output current or voltage of a linear resistive circuit with multiple inputs can be expressed as a linear combination of the several inputs

$$(3-19) \quad y = k_1 x_1 + k_2 x_2 + k_3 x_3 \dots$$

(3-33)


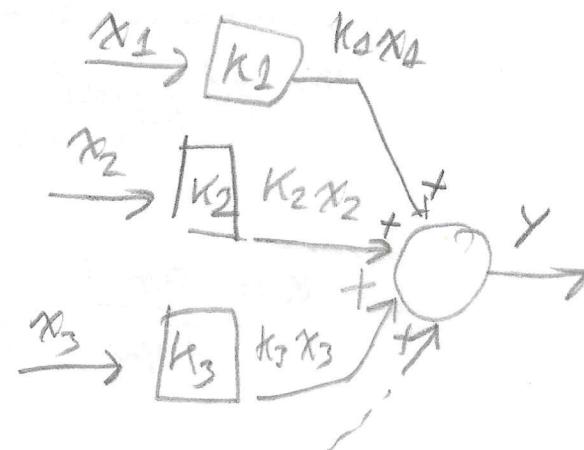


Figure 3-34

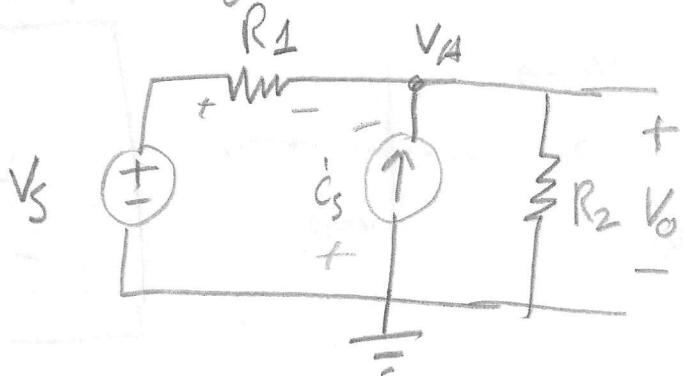

Superposition

Use Node Analysis \rightarrow KCL A

$$i_s + \frac{V_s - V_A}{R_1} - \frac{V_A}{R_2} = 0 \rightarrow i_s + \frac{V_s}{R_1} = V_A \left(\frac{1}{R_1} + \frac{1}{R_2} \right)$$

$$V_o = V_A \rightarrow V_o = \left(\frac{R_2}{R_1 + R_2} \right) V_s + \left(\frac{R_1 R_2}{R_1 + R_2} \right) i_s \quad (3-20)$$

Superposition Principle

From $y = k_1 x_1 + k_2 x_2 + k_3 x_3 \dots$

each input source is independent of all other input


\rightarrow so the output can be found by finding the contribution from each source acting alone, then adding the individual responses to obtain the total response

1) 'Turn off' all but one independent sources, find output of that source alone

2) Repeat for all sources till we have the output due to each source



3) Total output is all independent sources 'on'
is algebraic sum of individual outputs

(31)

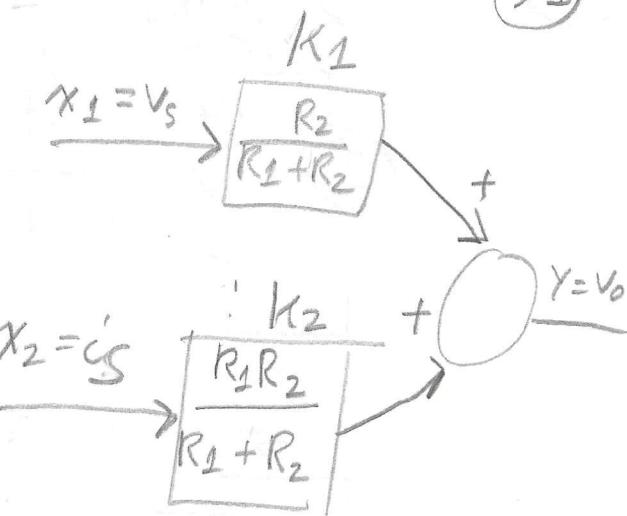


Block Diagram

(32) Turning of Sources

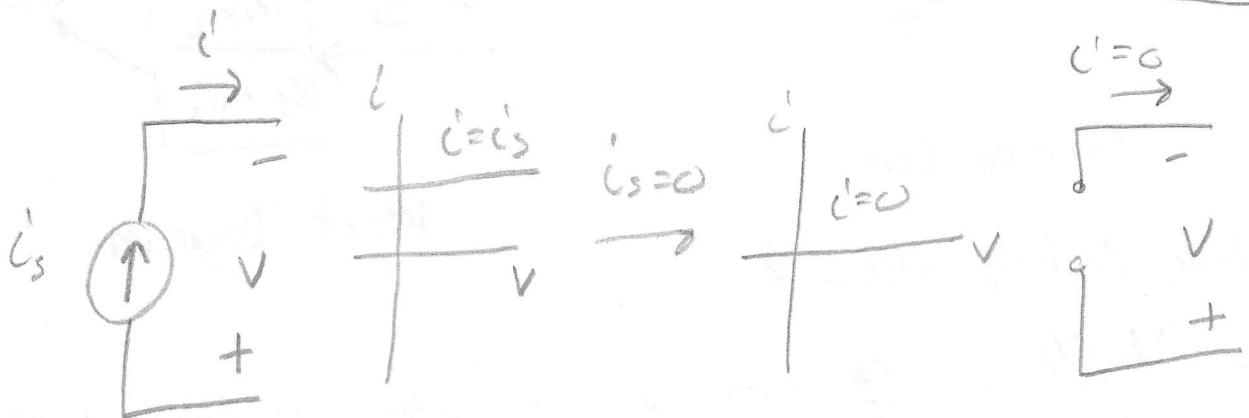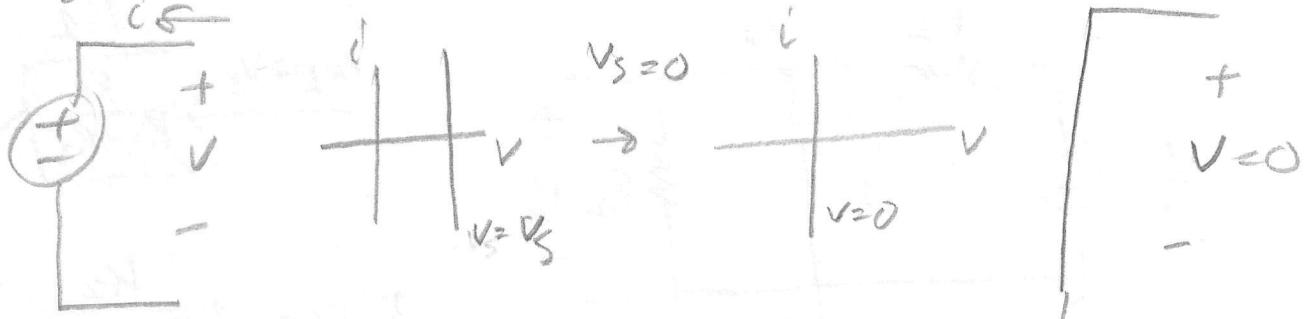

Ex 3-36

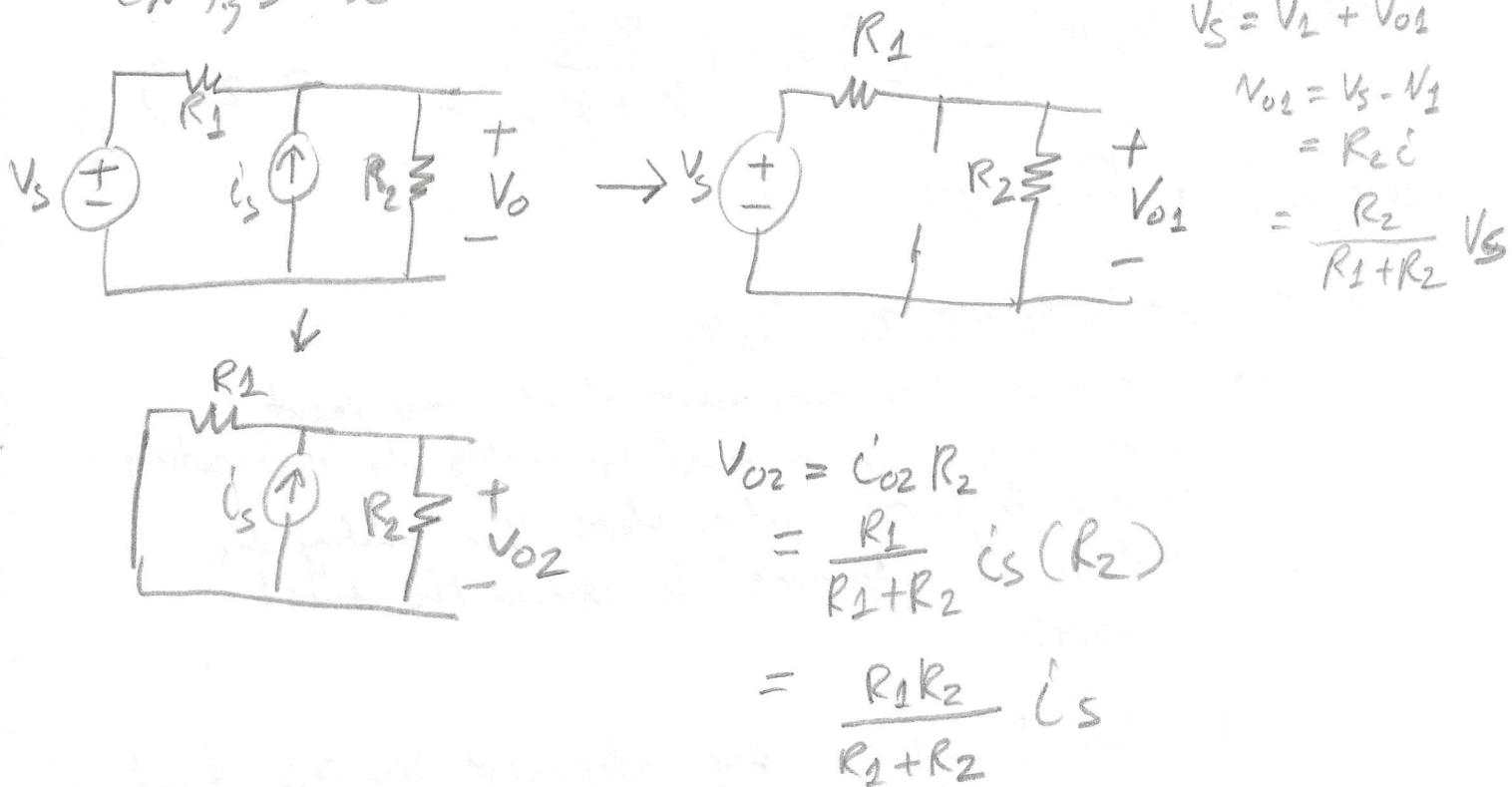

Superposition:

$$V_o = V_{o1} + V_{o2} = \frac{R_2}{R_1 + R_2} V_s + \frac{R_1 R_2}{R_1 + R_2} i_s$$

Ex 3-14 p 107

- Another voltage divider

PL09 Thevenin and Norton Equivalent Circuits


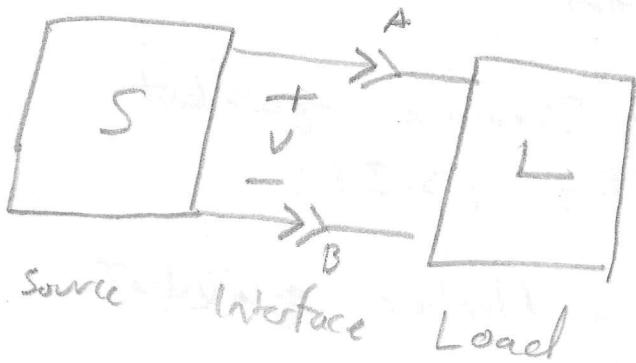


Fig 3-41, two terminal interface

Interface B = connection between circuits, they are frequent so we have special tools + analysis methods

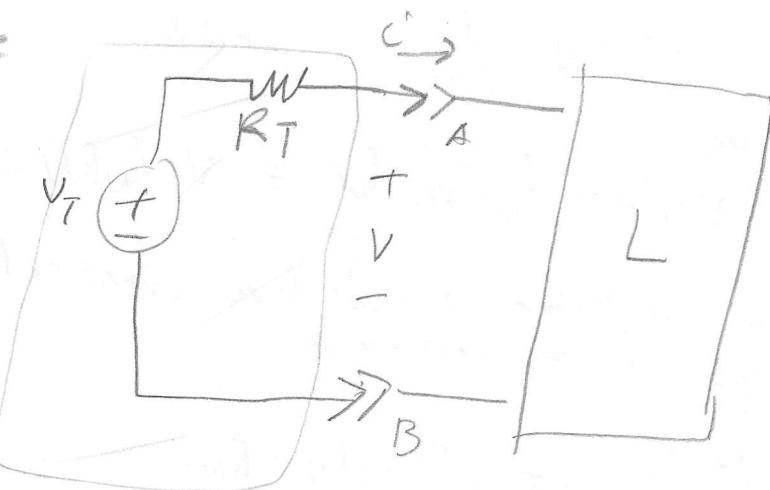signals from the source circuit delivered to the load circuit



Source Interface Load

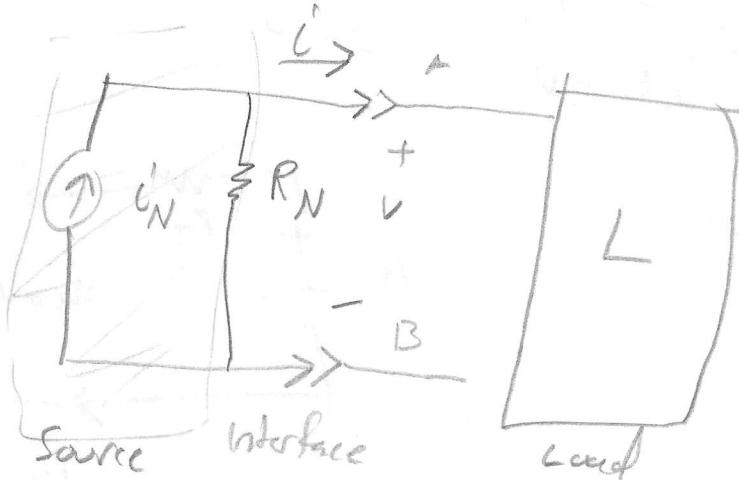


Fig 3-42

Thevenin and Norton equivalent circuits shown in (3-42) are valuable tools for dealing with circuit interfaces.

Condition for equivalent circuits exist:

If the source circuit in a 2 terminal interface is linear then the interface signals v and i do not change when the source circuit is replaced by its Thevenin or Norton equivalent

→ Load doesn't need to be linear

→ Loads can be linear storage elements called capacitors + inductors

(34) Thevenin and Norton are practical sources

i-v characteristics are same

You can interchange them

→ KVL + Ohm's Law to Thevenin equivalent

$$A-B \rightarrow V = V_T - i R_T \quad (3-21)$$

Next KCL, Ohm's Law to Norton equivalent

at A-B $i_N - \frac{V}{R_N} - i = 0$

$$i = i_N - \frac{V}{R_N} \quad (3-22)$$

So we have

$$V R_N i = i_N R_N V \rightarrow V = i_N R_N - R_N i \quad (3-23)$$




The Thevenin and Norton circuits have identical i-v relationships so we can write

$$V = V_T - i R_T, V = i_N R_N - R_N i$$


$$\Rightarrow R_N = R_T \quad (3-24)$$

$$i_N R_N = V_T$$

Fig 3-43

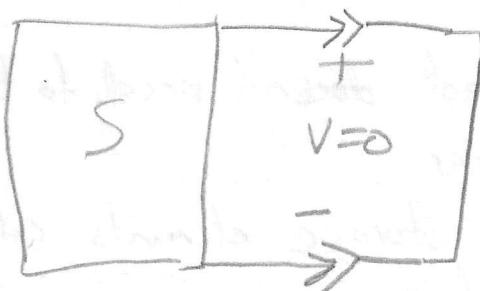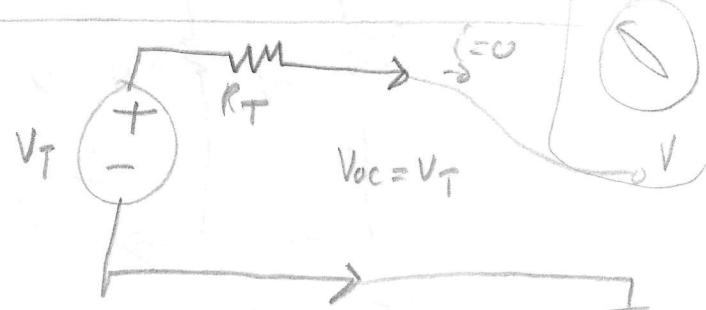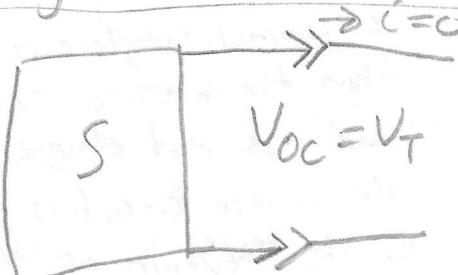

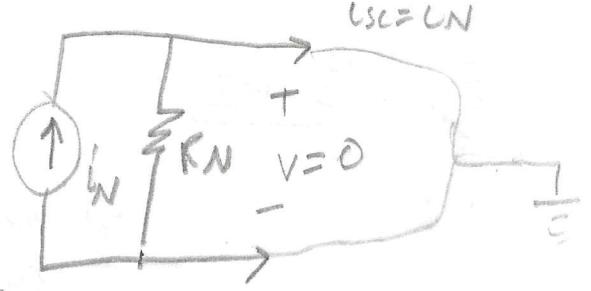$i_{sc} = i_N$
all i diverted
to short circuit



So

$$V_T = V_{OC}$$


$$i_N = i_{SC}$$

$$R_N = R_T = V_{OC}/i_{SC}$$

p 112 Applications of Thévenin and Norton Equivalent Circuits

→ replacing a complex circuit by its Thévenin or Norton equivalent can greatly simplify the analysis and design of interface circuits

Fig 3-44

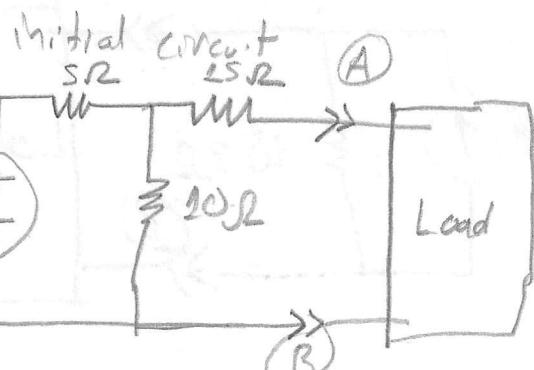

→ Select Load so the Source Circuit delivers 4V

We need the Thévenin or Norton equivalent

→ So we need V_{OC} , i_{SC}

as $i=0$ we get

$$V_T = V_{OC} = \frac{10}{10+5} \times 15 = 10V$$

→ we have Voltage Open circuit

to find i_{SC} (current short circuit)



$$i_X = \frac{15V}{R_{eq}} \quad R_{eq} = 5 + 25 \parallel 10 \Omega \\ = 11 \Omega$$

$$\rightarrow i_X = i_1 + i_{SC} \quad \rightarrow i_{SC} = \frac{V_1}{15} = \frac{i_X}{25(10+25)}$$

$$i_X = V_1(10^- + 25^-)$$

$$V_1 = \frac{i_X}{(10^- + 25^-)}$$

$$i_{SC} = \frac{10}{10+25} i_X$$

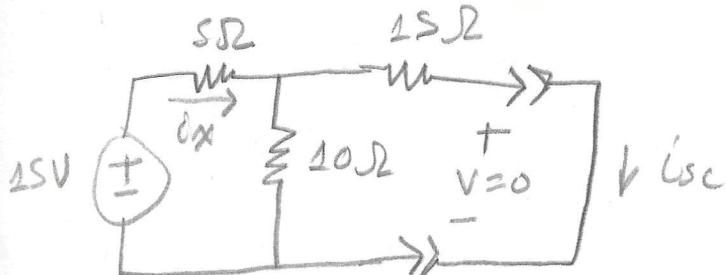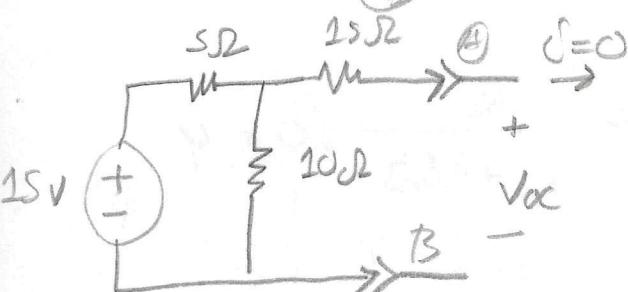

Current division

$$③ 6) \quad \text{So } i_{SC} = i_N \quad \text{So } i_{SC} = i_N = 0.545 \text{ A}$$

And $V_T = 10 \text{ V}$



$$\text{So } R_T = R_N = \frac{V_{OC}}{i_{SC}} = \frac{V_T}{i_N} = \frac{10}{0.545} = 18.3 \Omega$$

Recall (3-25)

$$V_T = V_{OC}$$

$$i_N = i_{SC}$$

$$R_N = R_T = \frac{V_{OC}}{i_{SC}}$$

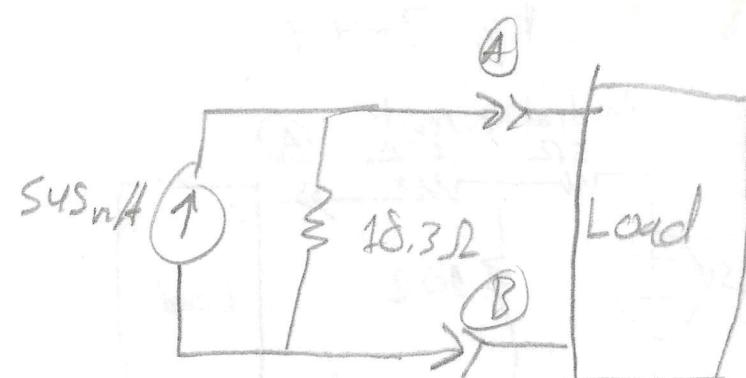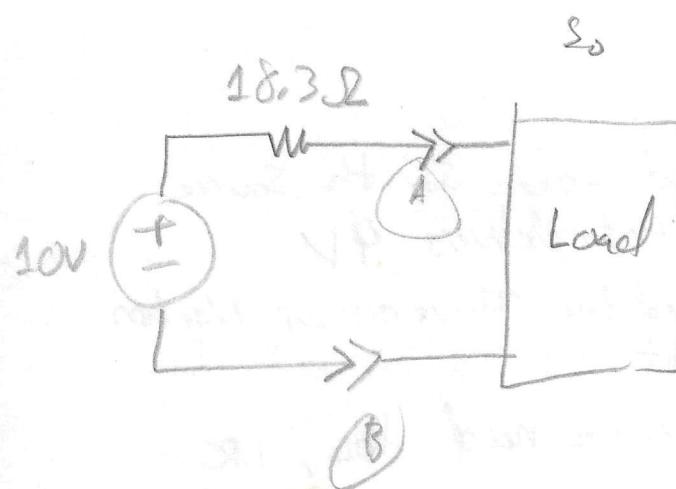

$$\text{So use } V_T, \quad \frac{R_L}{R_L + R_T} V_T \rightarrow \frac{R_L}{R_L + 18.3} 10 = 4$$

$$R_L = 12.2 \Omega$$