

Some chapter 4 Notes

Shoeberly

①

4-1 Linear Dependent Sources

Design of circuits containing devices like transistors or op amps (are active devices)

active device is a component that requires an external power supply to operate correctly.

active circuit; a circuit is one that contains one or more active devices.

Active circuits are capable of providing signal amplification

→ recall the proportionality property, Section 1.7:

$$Y = kX$$

Signal amplification means $k > 1$ when X and Y have the same dimensions

→ active circuits can deliver more signal

→ active devices operating in a linear mode are modeled using resistors and one or more dependent sources


Dependent sources: is a voltage or current source whose output is controlled by a voltage or current in a different part of the circuit

4 Types


- 1.) Current controlled Voltage source (CCVS)
- 2.) Voltage controlled Voltage source (VCVS)
- 3.) Current controlled Current source (CCCS)
- 4.) Voltage controlled Current source (VCCS)

(2)


Fig 4-1

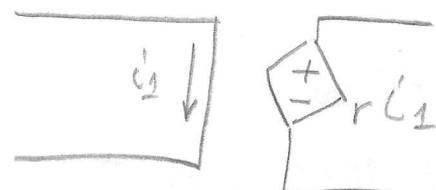


CCVS

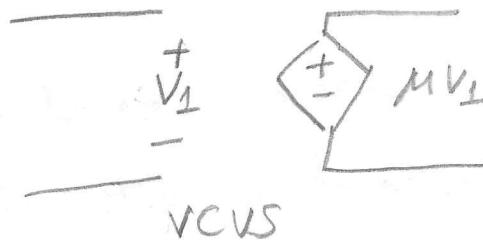

VCVS

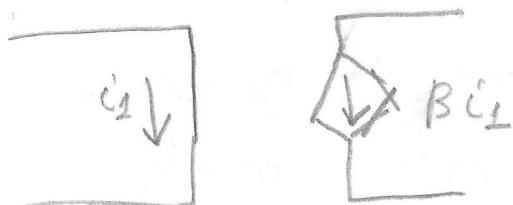

CCCS

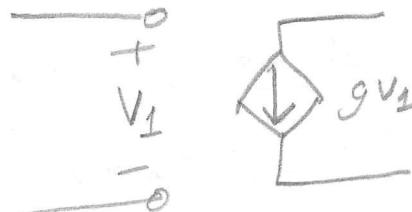

VCCS

Block Diagram of a
gain stage

Linear dependent source: output is proportional to the controlling voltage or current,

Proportionality factor: $\mu, \beta, r, g \rightarrow \text{gain}$

Voltage gain: μ

Current gain: β

trans-resistance: r_S

transconductance: g_S


Dependent sources aren't physical devices, they are used in combination with other circuit elements to create models of active devices.

(3)

Voltage source shorts when it turns off
 Current source open circut when its off

Dependent sources that turn off behave the same
 → They don't turn off individually
 → They depend on excitations supplied by
 independent sources

Fig 4-2

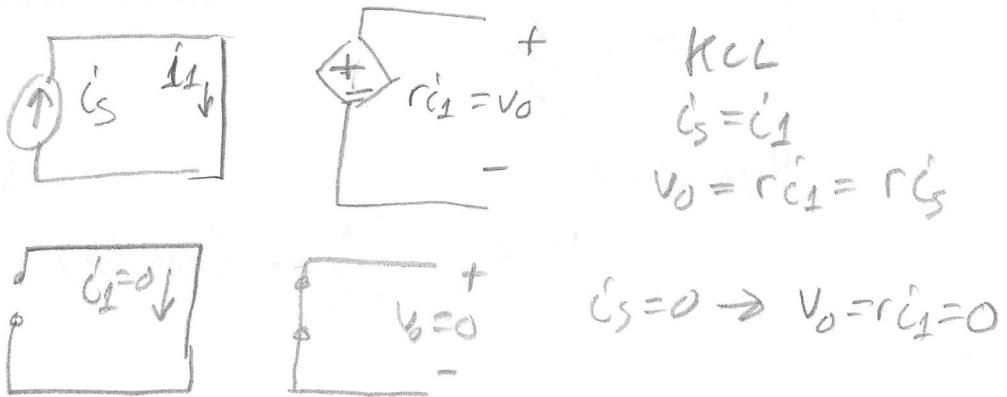

Because of this, be careful of superposition and Thevenin's theorem

Superposition / responses due to all independent sources acting simultaneously is equal to the sum of the responses due to each independent source acting at one time.

[Difference? Only at one time a signal!]

No half + half


$$f(x) + f(y+z) = f(x+y) + f(z) \quad \text{X for Dependent Sources}$$

p156 4-2 Analysis of Circuits with Dependent Sources

for dependent sources, we cannot lose the controlling signal in our analysis methods

→ we can do Source transformation on dependent sources

Fig 4-3

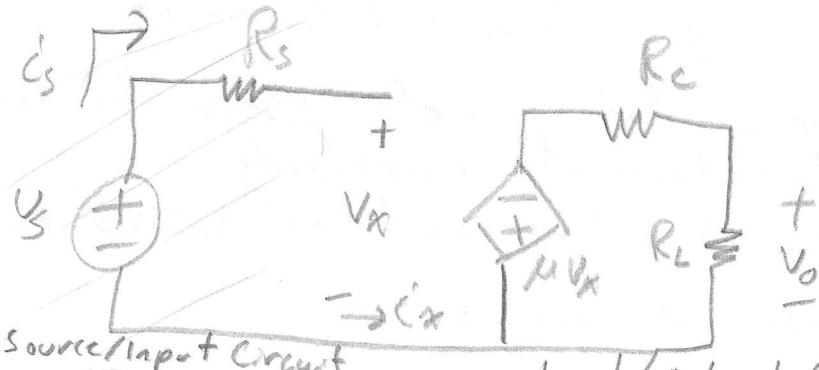

What's $K = \frac{V_o}{V_s}$

Voltage divider

What's the relationship
between V_x and V_s ?

$$V_o = \frac{R_L}{R_L + R_C} (-\mu V_x)$$

$$\text{KVL: } -V_s + I_s R_s + V_x = 0$$

open circuit, $I_s \rightarrow 0$

$$V_x = V_s$$

$$\therefore V_o = \frac{R_L}{R_L + R_C} (-\mu V_s) \quad \rightarrow K = \frac{V_o}{V_s} = \frac{R_L}{R_L + R_C} (-\mu)$$

Some Observations

$$R_s = R_C = R_L = 1 \text{ k}\Omega, \mu = 10^5$$

$$\text{So } K \rightarrow -50000, \text{ Big}$$

And $I_s = 0, I_x = 0 \rightarrow$ The source isn't supplying power
 \rightarrow The Dependent Source doesn't rely on
 the input for power output


(5)

Pg 157

Ex) 4-1

$\dot{C}_0?$ $V_o?$ $P_0?$ and $K = \frac{P_0}{P_S}$, Power Gain

Fig 4-4

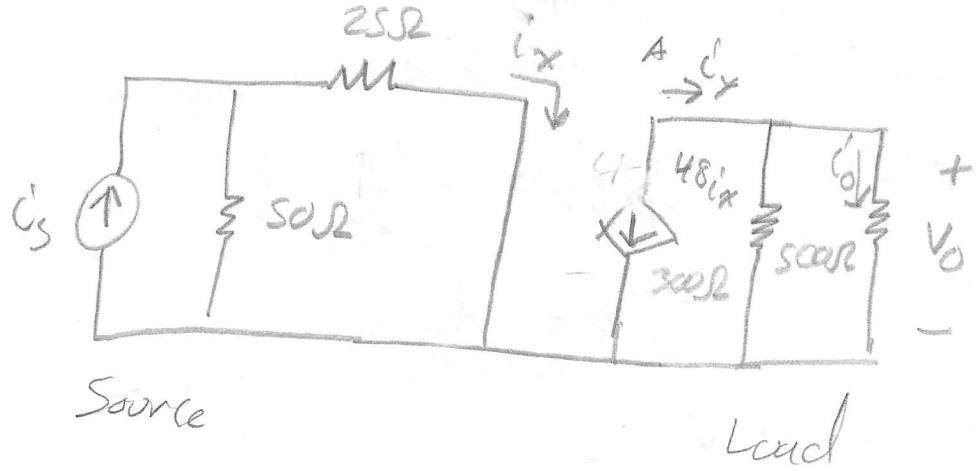

Current division: Load

$$\dot{C}_0 = \frac{300}{300+500} \dot{i}_x$$

$$\dot{i}_y = -48\dot{i}_x$$

Current division: Source

$$\dot{i}_x = \frac{50}{50+25} \dot{C}_S$$

So then, $\dot{C}_0 = \frac{300}{300+500} (-48) \frac{50}{50+25} \dot{C}_S$

$$\dot{C}_0 = -12 \dot{C}_S \quad V_o = 500 (\dot{C}_0) = -6000 \dot{C}_S \quad (4-3) \quad (4-4)$$


Often, active circuits produce negative K_S $K < 0$ → Signal Inversions

$$P_0 = \dot{C}_0 V_o = 72,000 \dot{C}_S^2 W$$

$$R_S = R_N \dot{C}_S^2 = (50/125) \dot{C}_S^2 W \quad K = \frac{72,000}{50/3}$$

⑥ exercise
4-1

Fig 4-5

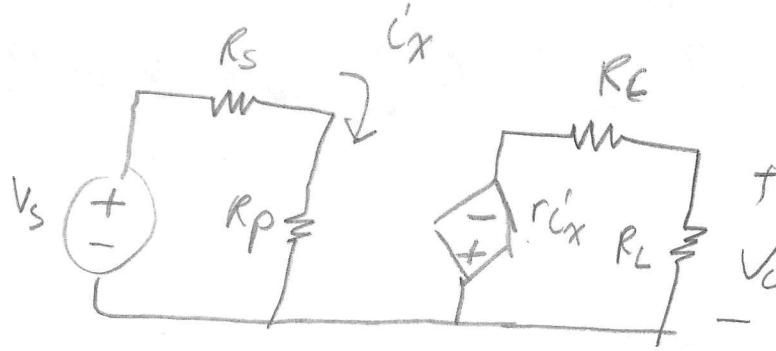

Voltage division! Load

$$V_o = \frac{R_L}{R_L + R_C} (-r_iX)$$

$$R_p iX = \frac{R_p}{R_s + R_p} V_s$$


$$iX = \frac{1}{R_s + R_p} V_s$$

$$\rightarrow V_o = \frac{-R_L r}{(R_L + R_C)(R_s + R_p)} V_s$$

Voltage division! Source

pl5g Node-Voltage Analysis w/ Dependent Sources

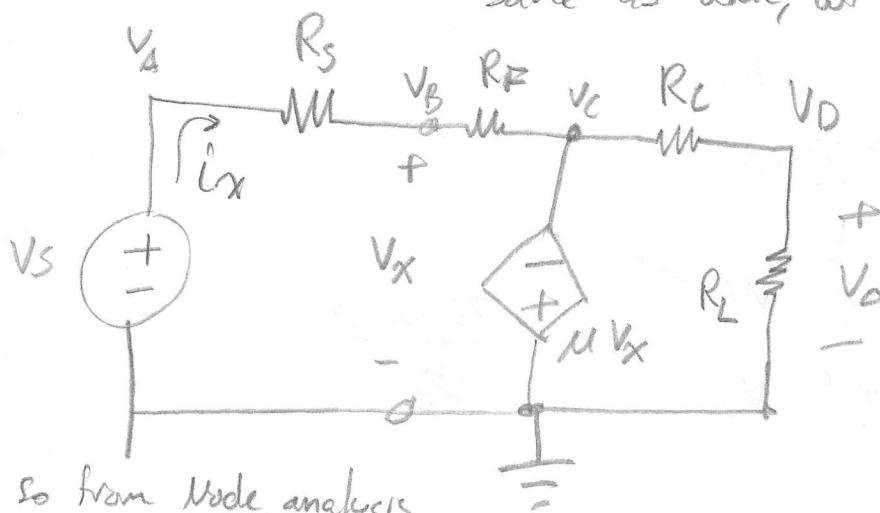Same as before, but we have another constraint



$$\text{ratio } k = V_o / V_s$$

Node Voltage KCL Node B

$$\rightarrow i_X = \frac{V_B - V_C}{R_F}$$

Remember
Passive
Sign Con.

$$\frac{V_A - V_B}{R_s} - \frac{V_B - V_C}{R_F} = 0$$

so from Node analysis

$$V_A = V_s, V_B = V_X, V_C = -\mu V_X, V_D = V_o$$

$$\frac{V_s - V_X}{R_s} - \frac{V_X - (-\mu V_X)}{R_F} = 0$$

Node D

$$\frac{V_C - V_D}{R_C} = \frac{V_D}{R_L}$$

$$-\frac{\mu V_X - V_o}{R_C} - \frac{V_o}{R_L} = 0$$

$$\frac{V_s}{R_s} - \frac{-\mu V_x}{R_F} = V_x(R_s + R_F) \Rightarrow V_x = \frac{V_s}{1 + \frac{(1+\mu)R_s}{R_F}}$$

for D

$$V_o(R_L + R_C) = \frac{-\mu V_x}{R_C} \rightarrow V_o = \frac{-\mu V_x R_L}{R_L + R_C}$$

$$\text{So we have } V_o = \frac{-\mu R_L}{R_L + R_C} \left[\frac{\frac{V_s}{1 + \frac{(1+\mu)R_s}{R_F}}}{R_L + R_C} \right]$$

$$\text{Then we have } K = \frac{V_o}{V_s} = \left[\frac{-\mu R_L}{R_L + R_C} \right] \left[\frac{1}{1 + \frac{(1+\mu)R_s}{R_F}} \right]$$


If we set value $R_F, R_F \rightarrow \infty$

$$\text{so now } K = \frac{-\mu R_L}{R_L + R_C}, \quad \text{if all } R_s = 1 \text{ k}\Omega \\ \mu = 10^5$$

$\frac{R_F}{\infty}$	K
∞	-50,000
$1.1M\Omega$	-495.05
$100k\Omega$	-49.9
$10k\Omega$	-4.99

R_F = Feedback Resistor
but $C_F \neq 0$

⑧ Example 4-2 p160

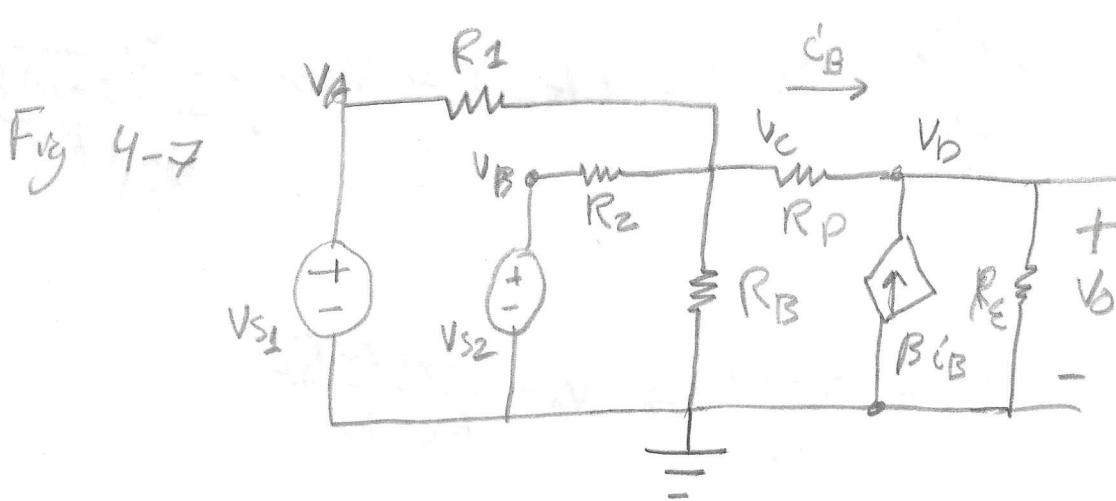

From inspection, Node C

$$V_C(R_P + R_B + R_E + R_I) - V_A R_I - V_B R_2 - V_D R_P = 0$$

Node D

$$V_D(R_P + R_E) - V_C R_P - \beta i_B = 0$$

Note! KCL at D!

$$\frac{V_C - V_D}{R_P} + \beta i_B - \frac{V_D}{R_E} = 0$$

$$\frac{V_C}{R_P} + \beta i_B = V_D(R_E + R_P)$$

recall, we subtract incoming currents, add outgoing currents when doing inspection

$$\text{we can write } i_B = \frac{1}{R_P} (V_C - V_D)$$


→ To write node-voltage equations for circuits with dependent sources, use the inspection method like normal, we get a system of equations that's not symmetrical, then express the dependent source in terms of the unknown node voltages, then those terms are now arranged in the matrix → No longer symmetrical, but we have a system

pL67 Mesh - Current Analysis w/ Dependent Sources

Same for Node-Voltage analysis

Just do mesh analysis, and then deal with the Dependent constraint, matrix won't be symmetrical after this

Fig 4-14

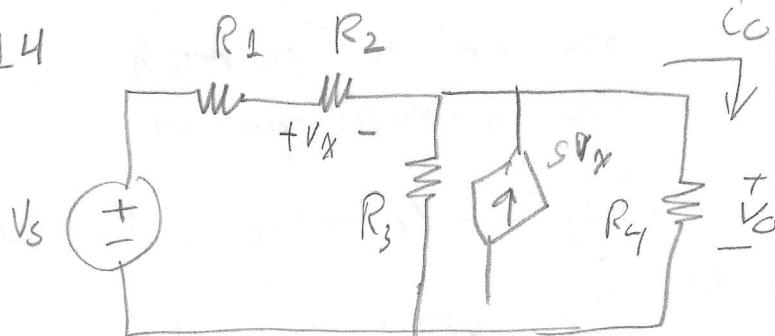

for $v_x? R_{IN}?$


$$R_1 = 50\Omega$$

$$R_2 = 1k\Omega$$

$$R_3 = 100\Omega$$

$$R_4 = 5k\Omega$$

$$S = 100 \text{ mS}$$

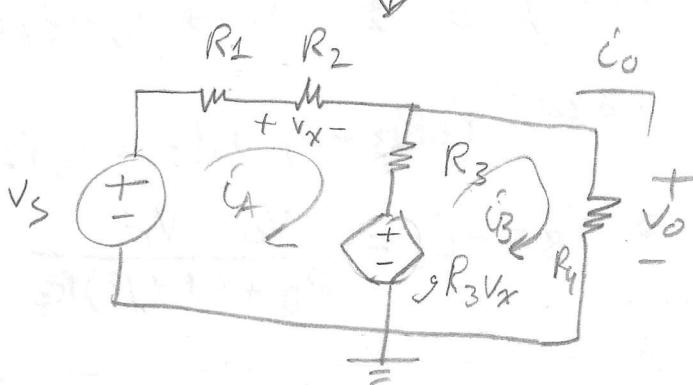

$$A: -V_s + R_1 i_A + R_2 i_B = 0$$

$$B: +R_3 i_A - R_3 i_B + R_4 i_B - S R_3 V_x = 0$$

$$-R_3 (i_A - i_B) + i_B R_4 - S R_3 V_x = 0$$

$$\text{Ohm's Law} \rightarrow i_A R_2 = V_x$$

So now we have

$$(R_1 + R_2 + R_3 + S R_2 R_3) i_A - R_3 i_B = V_s$$

$$-(R_3 + S R_2 R_3) i_A + (R_3 + R_4) i_B = 0$$

$$\rightarrow (2.115 \times 10^4) i_A - (10^2) i_B = V_s$$

$$-1.01 \times 10^4 i_A + (5.1 \times 10^3) i_B = 0$$

Cramer's rule

$$i_A = \frac{\begin{vmatrix} V_s & -10^2 \\ 0 & 5.1 \times 10^3 \end{vmatrix}}{\det} \quad i_B = \frac{\begin{vmatrix} 2.115 \times 10^4 & V_s \\ -1.01 \times 10^4 & 0 \end{vmatrix}}{\det}$$


⑩

$$V_O = i_B R_4 \quad R_{IN} = \frac{V_S}{i_A} = 10.95 k\Omega$$

$$= 0.904 V_S$$

p169 4-7, bipolar junction transistor operating in the active mode

Fig 4-15 Find transistor base current i_B

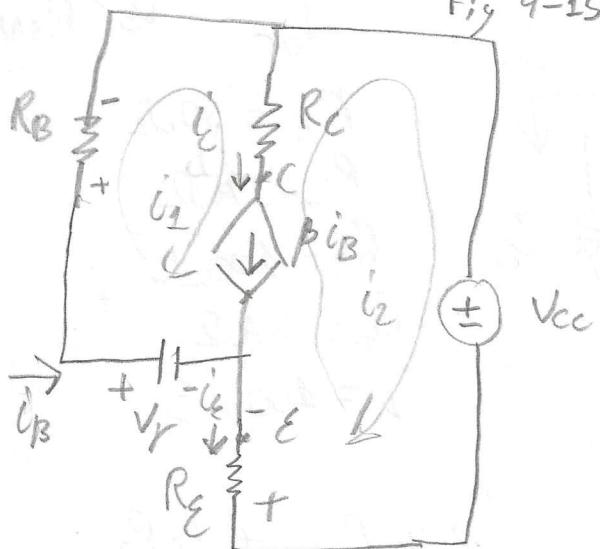

→ we need a supermesh

KVL supermesh equation

$$+i_1 R_B - V_r + V_{cc} + i_2 R_E = 0$$

$$\text{From KCL: } \beta i_B = i_1 - i_2$$

$$\text{And } i_B = -i_1 \rightarrow i_2 = i_1(1 + \beta)$$

$$\text{So now: } i_1 R_B - V_r + V_{cc} + i_1(1 + \beta) R_E = 0$$

$$i_1 = \frac{V_r - V_{cc}}{R_B + (1 + \beta) R_E} \rightarrow i_B = -i_1 = \frac{V_{cc} - V_r}{R_B + (1 + \beta) R_E}$$


p171 Thévenin Equivalent Circuit w/ Dependent Sources

To find the Thévenin equivalent of an active circuit, we must leave the independent sources on or else supply excitation from an external source. So the Thévenin resistance cannot be found by the Look back method (all independent sources must be turned off).

→ Turning off independent sources turns off dependent sources which changes the characteristics of input/output

p172 Example 4-9 what's the input R?

(11)

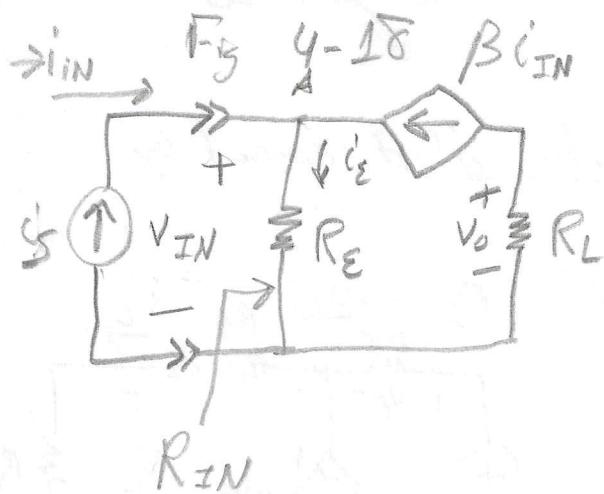

For $i_{IN} = 0$, $\beta i_{IN} = 0$

$$\therefore R_{IN} = R_E$$

KCL at Node A

$$\begin{aligned} i_E &= i_{IN} + \beta i_{IN} \\ &= (1+\beta) i_{IN} \end{aligned}$$

$$\text{Ohm's Law, } \rightarrow V_{IN} = i_E R_E = R_E (1+\beta) i_{IN}$$

$$\text{So we have } R_{IN} = \frac{V_{IN}}{i_{IN}} = R_E (1+\beta)$$


Notes:

4-18 models a transistor circuit in which the gain parameter β typically lies between $50 \sim 250$.

The input resistance w/ external excitation is $(\beta+1)R_E$, which is significantly higher than R_E alone,

Bigger R_{IN} helps reduce the effects of loading on the input source

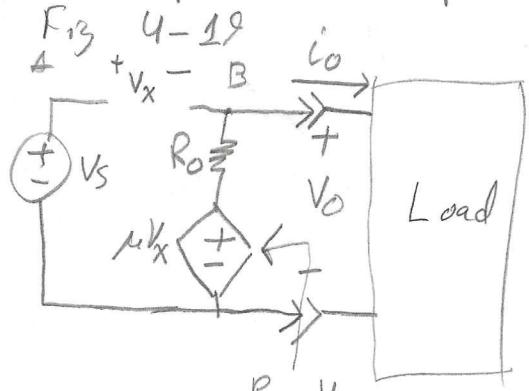Example 4-10 p 172 What's the Thevenin Equivalent?



KVL

$$V_X + V_O - V_S = 0 \rightarrow V_X = V_S - V_O$$

Load back resistance would be R_O

KCL at B

$$\frac{M V_X - V_O}{R_O} = i_O \rightarrow \frac{M V_S - M V_B - V_O}{R_O} = i_O$$

$$\frac{-V_O(M+1)}{R_O} = i_O - \frac{M V_S}{R_O} \rightarrow V_O = \frac{i_O R_O}{M+1} + \frac{M V_S}{M+1}$$

So RVL of a Thevenin circuit

$$\begin{aligned} \text{I-V relationship is } & i R_T + V_o - V_T = 0 \\ \rightarrow V_o &= V_T - i R_T \end{aligned}$$

$$\text{Therefore } V_o = \frac{M V_S}{M+1} - \frac{i_O R_O}{M+1}$$

$$V_T = \frac{M V_S}{M+1} \quad R_T = \frac{R_O}{M+1}$$

(12) This is a model of an op-amp circuit called Voltage Follower

$R_o = 100\Omega$ for general purpose OPAMP as $\mu = 10^5$

So active resistance is $2m\Omega$

Low output resistance reduces the loading effect caused by connecting a load to the output

Exercise 4-12 R_{IN} ? V_T ? R_T ?

$$i_{IN} = \frac{V_s - \mu V_F}{R_F} \quad V_{IN} = \mu V_F$$

kV_L

$$V_F + \mu V_F = V_s \rightarrow V_s = V_F(1 + \mu)$$

$$\text{so } V_{IN} = \frac{\mu V_s}{1 + \mu} \quad i_{IN} = \frac{1}{R_F} \left[V_s - \frac{\mu V_s}{1 + \mu} \right]$$


$$i_{IN} = \frac{V_s}{R_F} \left[\frac{1 + \mu - 1}{1 + \mu} \right] = \frac{V_s}{R_F(1 + \mu)}$$

$$R_{IN} = \frac{V_{IN}}{i_{IN}} = R_F(1 + \mu) \text{ if } V_{IN} = V_s$$

$$V_T = \mu V_F$$

$$R_T = \frac{\mu V_F}{\mu V_F} R_o = R_o$$

$$V_T = \frac{\mu V_s}{1 + \mu}$$

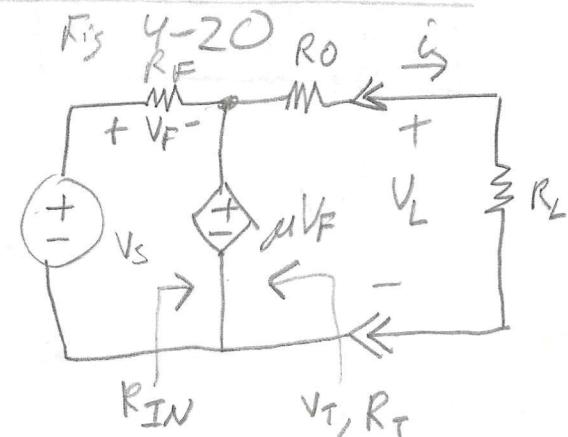

$$i_{IN} = \frac{\mu V_F}{R_o} \quad \text{Source transformation}$$

$$V_T = i_{IN} R_T = \frac{i_{IN} R_o}{1 + \mu}$$

$$= \frac{1 + \mu}{R_o} V_s - V_o$$

Example 4-11, Notes on BJTs

(13)

→ dependent sources are used to model semiconductor devices like transistors and OP Amps


The model describes Voltages + currents at exit terminals

Bipolar junction transistor (BJT)

Field Effect transistor (FET)

→ They have operating modes with different i-V characteristics

BJT

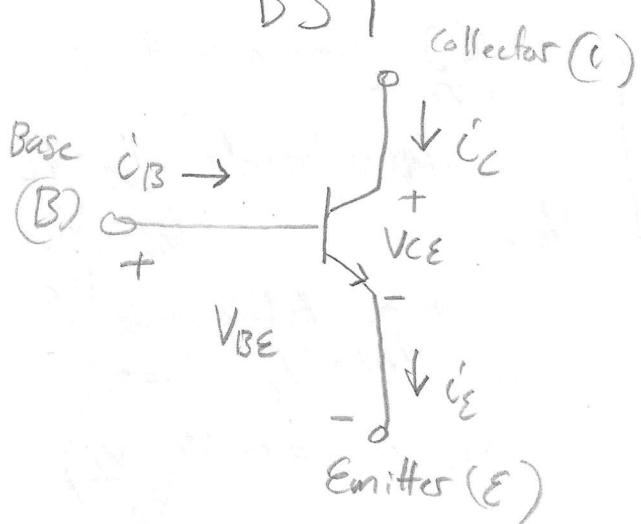

These can change

V_{BE} : Base-Emitter Voltage

V_{CE} : Collector-emitter Voltage

$$\text{KCL: } i_E = i_B + i_C$$

i_B, V_{BE} This model can't have
 i_C, V_{CE} these variables be negative

Active Mode: i_C is controlled by i_B , V_{BE} is constant



$$i_C = \beta i_B, V_{BE} = V_T$$

Proportionality factor $\beta \sim$ forward gain $50 \sim 300$


$V_T \sim$ threshold Voltage $V_T < 1 \text{ V}$

active mode

saturation mode

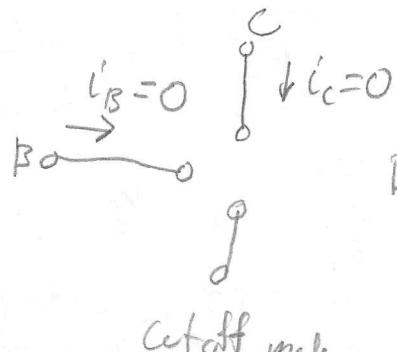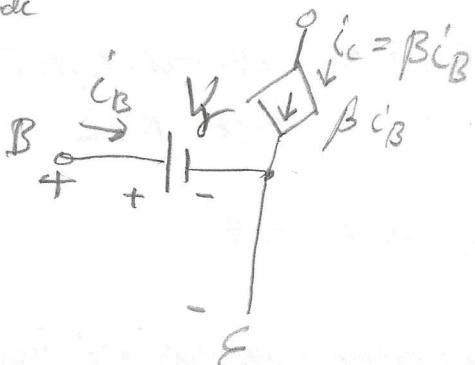

cutoff mode

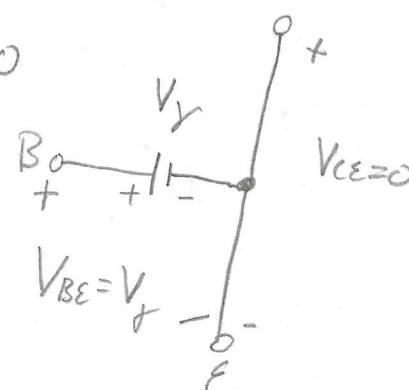

(14) In saturation mode, $i_c = \text{short-circuit current from external circuit}$

BJT output variables

Cutoff bounds Saturation bounds

$V_{OC} = \text{open circuit voltage}$

$$0 \leq i_c \leq i_{SC}$$


$$V_{OC} \geq V_{CE} \geq 0$$

Assume

1) i_c, V_{CE} cannot be ' $-$ '

2) V_{OC}, i_{SC} depend on the rest of the circuit

Fig 4-23

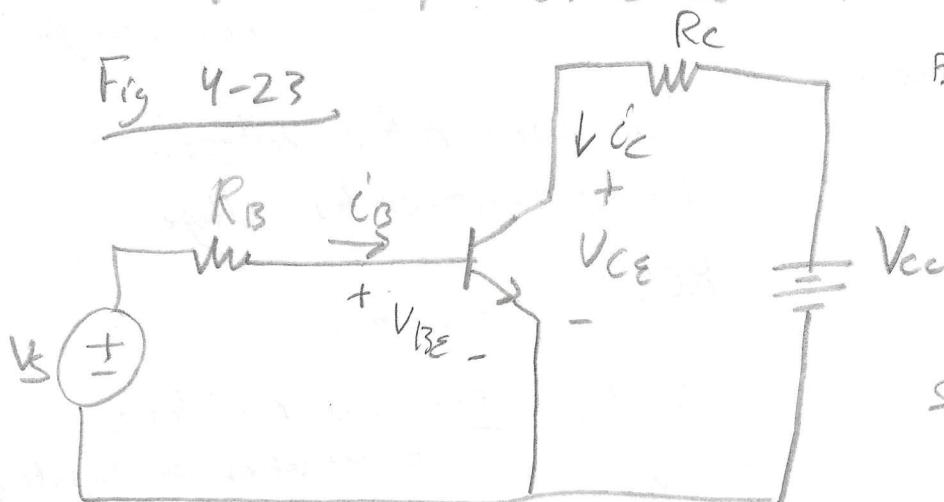

BJT common emitter circuit

$$\text{upper bounds } V_{OC} = V_{CC}$$

$$i_{SC} = \frac{V_{CC}}{R_C}$$

$$\begin{aligned} &\text{Assume Active mode} \\ &V_{BE} = V_r, i_c = \beta i_B \\ &i_c = \beta i_B = \beta \left(\frac{V_s - V_r}{R_B} \right) \end{aligned} \quad (4-11)$$

For $V_s > V_r$, then $i_c > 0$

If $V_s < V_r$, $i_c < 0 \rightarrow \text{BJT is in cutoff mode}$

Cutoff bounds

$$i_c = 0, V_{CE} = V_{OC} = V_{CC}$$

When $V_s > V_r$, $i_c = \beta \left(\frac{V_s - V_r}{R_B} \right)$ predicts positive collector current that increases linearly with V_s . To get collector-emitter voltage, KVL


$$V_{CE} = V_{CC} - i_c R_C \quad (4-12)$$

$\therefore V_{CE} > 0$ for $i_c < \frac{V_{CC}}{R_C}$, we $\frac{V_{CC}}{R_C} \equiv i_{SC}$ (short circuit)

Thus $V_s > V_r, i_c < i_{SC} \rightarrow \text{BJT is active}$

if (4-11) predicts $i_c > i_{SC}$ then $V_{CE} < 0 \rightarrow \text{saturation conditions violated}$

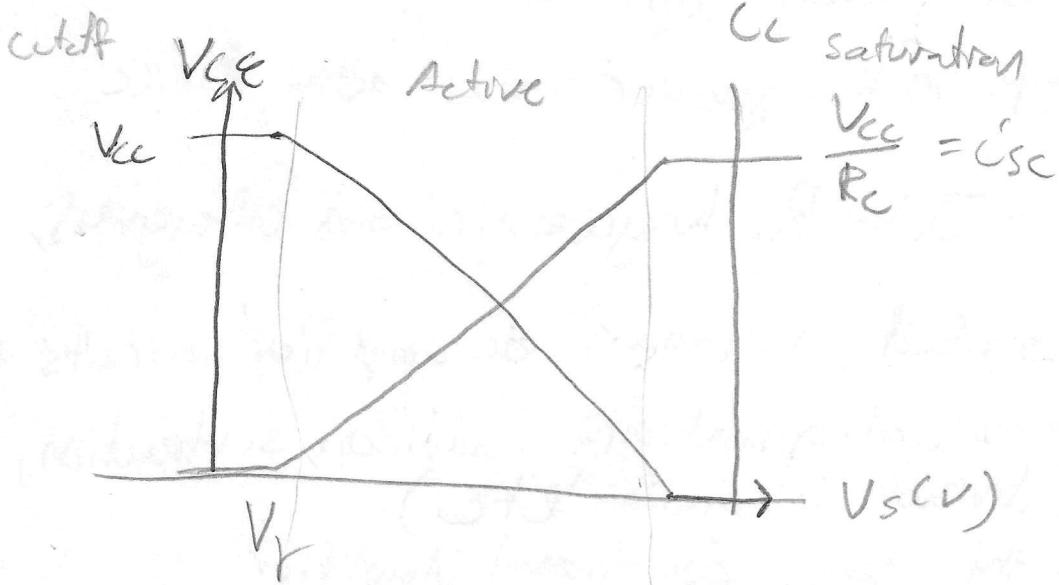But we are still saturated $i_c = i_{SC} = V_{CC}/R_C$ and $V_{CE} = 0$



When $V_S < V_f$, cutoff

$$I_C = 0 \quad V_{CE} = V_{OC} = V_C$$

for $V_S > V_f$

$$I_C = \beta I_B = \beta \left(\frac{V_S - V_f}{R_B} \right)$$

$$V_{CE} = V_C - I_C R_C$$

as V_S increases,
 I_C increases
 V_{CE} decreases

I_C increases until it reaches saturation

$$I_C = I_{SC}$$

transistor reaches saturation

and the constant value,

$$I_C = I_{SC} = \frac{V_C}{R_C}$$

$$V_{CE} = 0$$

→ Supply V_2 , gamma cutters fall

Note: In digital applications, the input voltage drives the transistor between the cutoff and saturation modes passing through the active mode as quickly as possible.

In analog application, the transistor remains in the active mode where the slope of the transistor characteristic provides voltage amplification.

46

4-3 The Operational Amplifier

IC OPAMP is the premier linear active device

1947 - John R. Ragazzini and colleagues,

paper described high-gain dc amplifier circuits that perform mathematical operations (addition, subtraction, multiplication, division, integration etc)

hence the name operational Amplifier


general- and special-purpose analog computers using vacuum tubes

The Device itself is a complex array of transistors, resistors, diodes, and capacitors, all fabricated and interconnected on a tiny silicon chip.

The device can be modeled by I-V characteristic


- ICs

OP AMP Notation

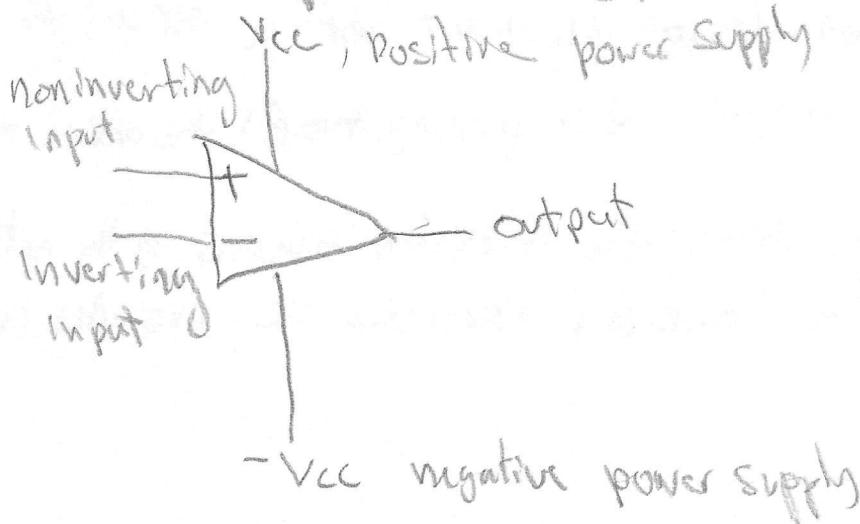

power supply may not be seen, but they are there


17

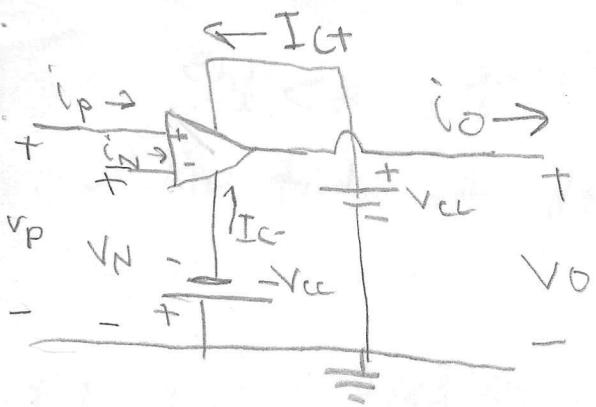

all voltages are defined to a common reference node

Note the direction of currents

$$i_p + i_N + I_{C+} + I_{C-} = i_O$$

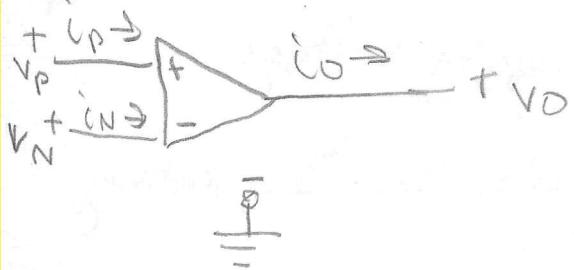


\Rightarrow Shorthand Notation

$$i_O = i_N + i_p$$

This is very wrong, The output current does not come from the input current. Input currents are very small
Output current comes from the supply voltages

Transfer characteristic

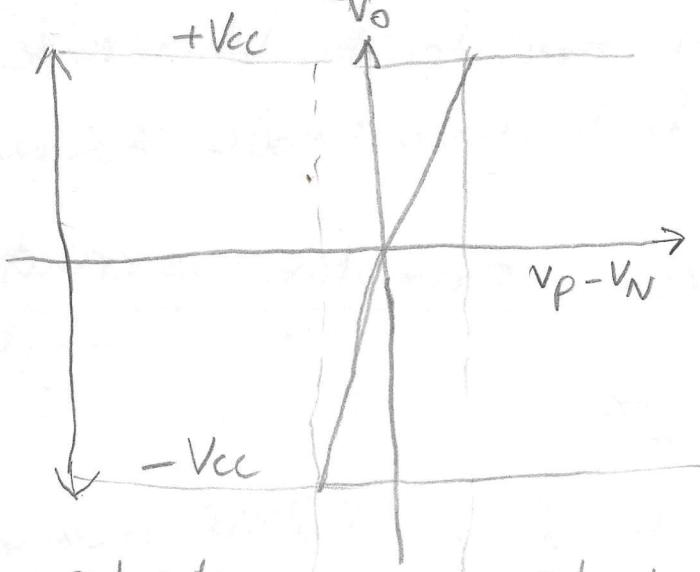

this characteristic provides the relationship between

non inverting input: v_p

inverting input: v_N

and the output voltage v_o

3 regions

+Saturation

-Saturation

linear

-Saturation Linear +Saturation

In the Linear Region, the OP AMP is a differential amplifier

output is proportional to the difference of the inputs

$$v_o = A(v_p - v_N) \quad (4-15)$$

Slope is the Voltage Gain

⑧ The voltage gain is very large, $A > 10^5$

as long as $(V_p - V_N)$ is very small, the output will be proportional to the input

when $A(V_p - V_N) > V_{CC}$, OPAMP is saturated

→ output voltage is limited by supply voltage

Like the transistor, the OPAMP also has 3 operating modes

1.) +Saturation $A(V_p - V_N) > V_{CC}$; $v_o = +V_{CC}$

2.) -Saturation $A(V_p - V_N) < -V_{CC}$; $v_o = -V_{CC}$

3.) Linear mode $|A(V_p - V_N)| < V_{CC}$; $v_o = A(V_p - V_N)$


Usually, OPAMP circuits use the model for the Linear mode

If the op-amp is not specified to be linear mode, Assume it is,

and if $-V_{CC} < v_o < V_{CC}$, assumption was correct

Ideal OPAMP Model p178

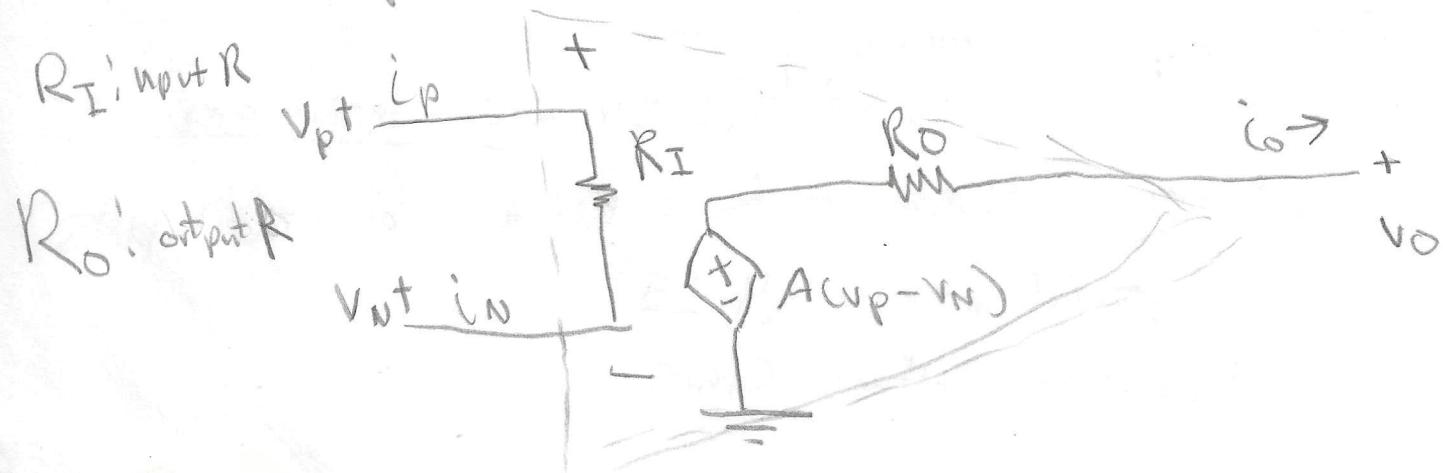Dependent-Source Model of an OPAMP in Linear Mode



(19)

typically

$$10^6 < R_I < 10^{12} \Omega \quad \text{High } R_I$$

$$10 < R_O < 100 \Omega \quad \text{Low } R_O$$

$$10^5 < A < 10^8 \quad \text{High } A$$


↑

Key attributes to OP AMPS

Typically $V_{CC} \approx 15V$, A is very large $\approx 10^5$

$$\text{we can write } -V_{CC} \leq V_o \leq +V_{CC} \quad , V_o = A(V_p - V_N)$$


$$-\frac{V_{CC}}{A} \leq (V_p - V_N) \leq +\frac{V_{CC}}{A}$$

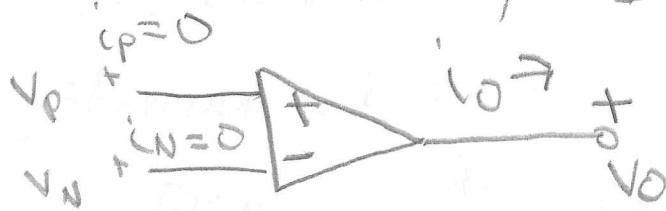i.e. $V_{CC} \approx 15V$, $A \approx 10^5$, It comes to be $V_p \approx V_N$ This is a practical op-amp model
for Ideal OP-AMP $A \rightarrow \infty$ and thus, $V_p = V_N$, $R_I \rightarrow \infty$, so $i_p = 0, i_N = 0$ It's necessary to have a feedback path from the output to the input (one or both) to ensure $V_p \approx V_N$

With proper feedback we can get an Ideal Model

20

Noninverting OP AMP p180

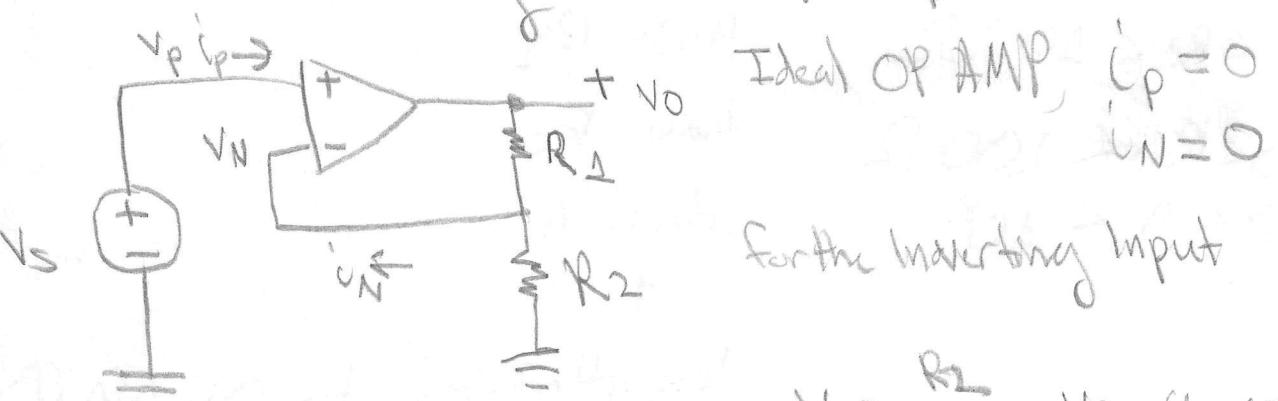

for the inverting input (Voltage Division)

$$V_N = \frac{R_2}{R_1 + R_2} V_O \quad (4-17)$$



Fig 4-32

Ideal OP AMP constraints demand

$$V_P = V_N, \text{ so } V_N = V_S \rightarrow V_S = \frac{R_2}{R_1 + R_2} V_O \rightarrow V_O = \frac{R_1 + R_2}{R_2} V_S$$

Strategy:

- 1) Use circuit analysis methods to express the OP AMP input voltages V_P and V_N in terms of circuit parameters,
- 2) Use ideal OP AMP constraint $V_P = V_N$ to solve input-output relationship

Input-output relationship for noninverting amplifier

$$V_O = K V_S, \quad K = \frac{R_1 + R_2}{R_2} \quad (4-20)$$

K is a proportionality constant and closed loop gain K

It defines input-output relationship when the feedback loop is connected (closed)

for Op AMPs we have two types of Gains


(21)

- 1.) the Large open-loop gain from the Op Amp itself
- 2.) the closed-loop voltage gain of the Op Amp circuit with a negative feedback path.
[Not by the Op AMP Gain]

This gain is determined by the resistors

K is smaller than A , but defined and useable

Fig 4-33

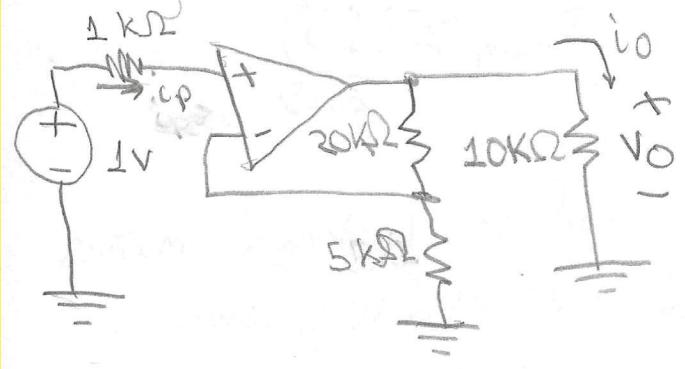

Q181 What's V_o ? i_o ? K ? P_o ? P_x ?

Voltage gain
Power gain

We know $K = \frac{R_1 + R_2}{R_2} = \frac{20k + 5k}{5k} = 5$

But there's now a $1k\Omega$ Resistor
KVL: $-V_s + (1k\Omega)i_p + V_N = 0$

But recall for an Ideal Op AMP, $i_p = 0$, so there's no voltage drop across the resistor.

$$\text{So } V_o = \frac{R_1 + R_2}{R_2} V_s \rightarrow V_o = 5V', K = 5'$$

$$i_o = \frac{5V}{10k\Omega} = 500\mu A, P_o = i_o V_o = 2.5mW$$

There's no power gain, $i_p = 0$, source doesn't supply power.

Design an amplifier with a gain, $K=10$

for $R_2 = 10\text{ k}\Omega$, then $R_1 = 90\text{ k}\Omega$ (These resistors normally have low tolerances $\pm 1\%$)

We usually limit ourselves to the range $1\text{ k}\Omega$ to $1\text{ M}\Omega$, we need to think about the power dissipation in the resistors. We usually use resistors with $\frac{1}{4}\text{ W}$ rating. We remember the maximum voltage is 15 V

$$\text{So the smallest } \frac{1}{4}\text{ W R is } R_{\min} \geq \frac{(15)^2}{0.25}$$

$$R_{\min} \geq 900\Omega$$

~~For~~ $1\text{ M}\Omega$ is chosen because surface leakage makes it difficult to maintain the tolerance in a high-value resistance. High valued R_s are noisy

Effects of finite OP AMP Gain

Ideal OP AMP has infinite gain, but we have models for finite gain

$$R_I \approx 10^6\Omega \approx 10^{12}\Omega$$


so we can treat it as an open circuit

non-inverting (V_p) determined by source

Inverting can be found by circuit division

remember Voltage division
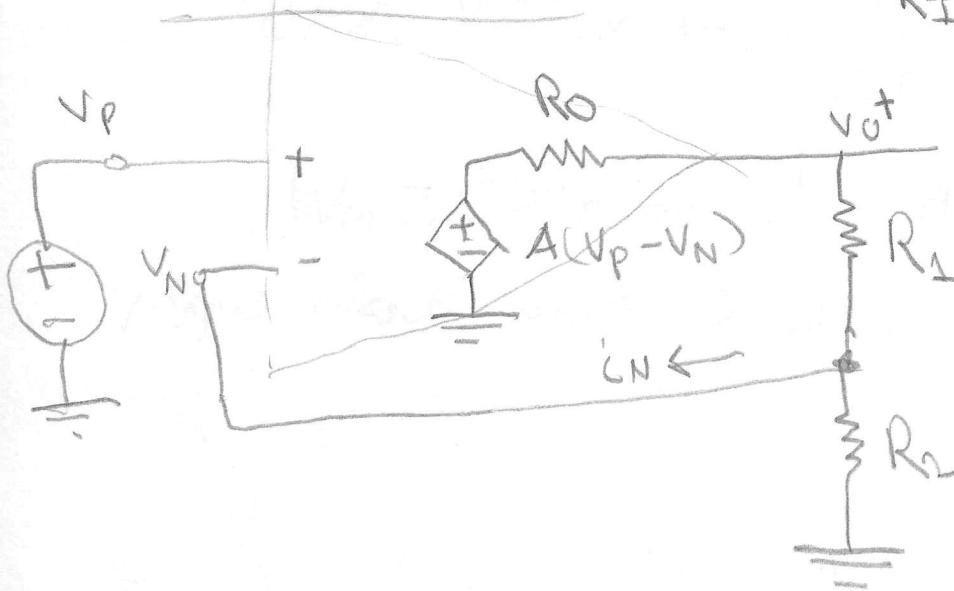
$$V_o = \frac{(R_1 + R_2)}{R_o + (R_1 + R_2)} A(V_p - V_N)$$



recall from Non Invertig OP AMP

(23)

$$V_N = \frac{R_2}{R_1 + R_2} V_O, \quad V_P = V_S$$

$$V_O = \left[\frac{(R_1 + R_2)}{R_0 + (R_1 + R_2)} \right] A \left[V_S - \frac{R_2}{R_1 + R_2} V_O \right] \quad [4-21]$$

from this relationship, we can see that the output V_O depends on the output V_O , so feedback is present

we now have

$$V_O = \frac{A(R_1 + R_2)}{R_0 + R_1 + R_2(1+A)} V_S \quad (4-22)$$

$$\lim_{A \rightarrow \infty} V_O = \lim_{A \rightarrow \infty} \frac{A(R_1 + R_2)}{R_0 + R_1 + R_2(1+A)} V_S$$

$$\begin{aligned} & \text{if } \lim_{A \rightarrow \infty} \frac{A(R_1 + R_2)}{R_2(A)} V_S \text{ as } A \text{ is very large} \\ &= \frac{R_1 + R_2}{R_2} V_S \end{aligned}$$

so we have

$$V_O = \frac{R_1 + R_2}{R_2} V_S = K V_S$$

K is the closed loop gain from the ideal OPAMP model
for finite A , we ignore R_0 as its small compared to R_1, R_2

$$\text{eventually we get } V_O = \frac{K}{1 + (K/A)} V_S$$

so we get good approximation to Ideal OPAMP

as long as $K \ll A$

rule of thumb, $K < \frac{A}{100}$

Closed loop gain
 K must be less than 1% of OPAMP Gain A

2H

Feed back Path also Affects^{out} Resistance
To find the Thévenin circuit

$$\text{open-circuit voltage, } V_O = V_{TH} = \frac{K}{1+(KA)} V_S$$

$$\text{short-circuit current, } I_{SC} = I_N = \frac{A(V_S)}{R_O} = \frac{AV_S}{R_O}$$

(No current goes thru R_1, R_2)

So $R_{\text{Thévenin}}$

$$R_T = \frac{V_O}{I_{SC}} = \frac{V_{TH}}{I_N} = \frac{K}{1+(KA)} \left(\frac{R_O}{A} \right) = \frac{(K/A)}{1+(K/A)} R_O$$

$$\text{when } K \ll A, R_T = \frac{K}{A} R_O \approx 0 \Omega$$

~~With~~ with feedback, $R_T \rightarrow 0$, or very small compared to R_T without feedback

$$\text{Typically, } R_O < 100 \Omega, A > 10^5$$

So typically in this course, we are dealing with ideal OP AMP I-V characteristics (as long as conditions are met)

→ OP AMP circuits have essentially zero R_T

so then → output voltage does not change with different loads

Thevenin output resistance of an OP AMP w/ feed back is essentially zero

4-4 OP AMP Circuit Analysis

p 184

(25)


This is useful for analog signal-processing systems
noninverting amplifier

plus: voltage follower, the inverting amplifier, the summer,
and the subtractor

→ recognize the feedback pattern,

→ isolate the basic circuit as a building block

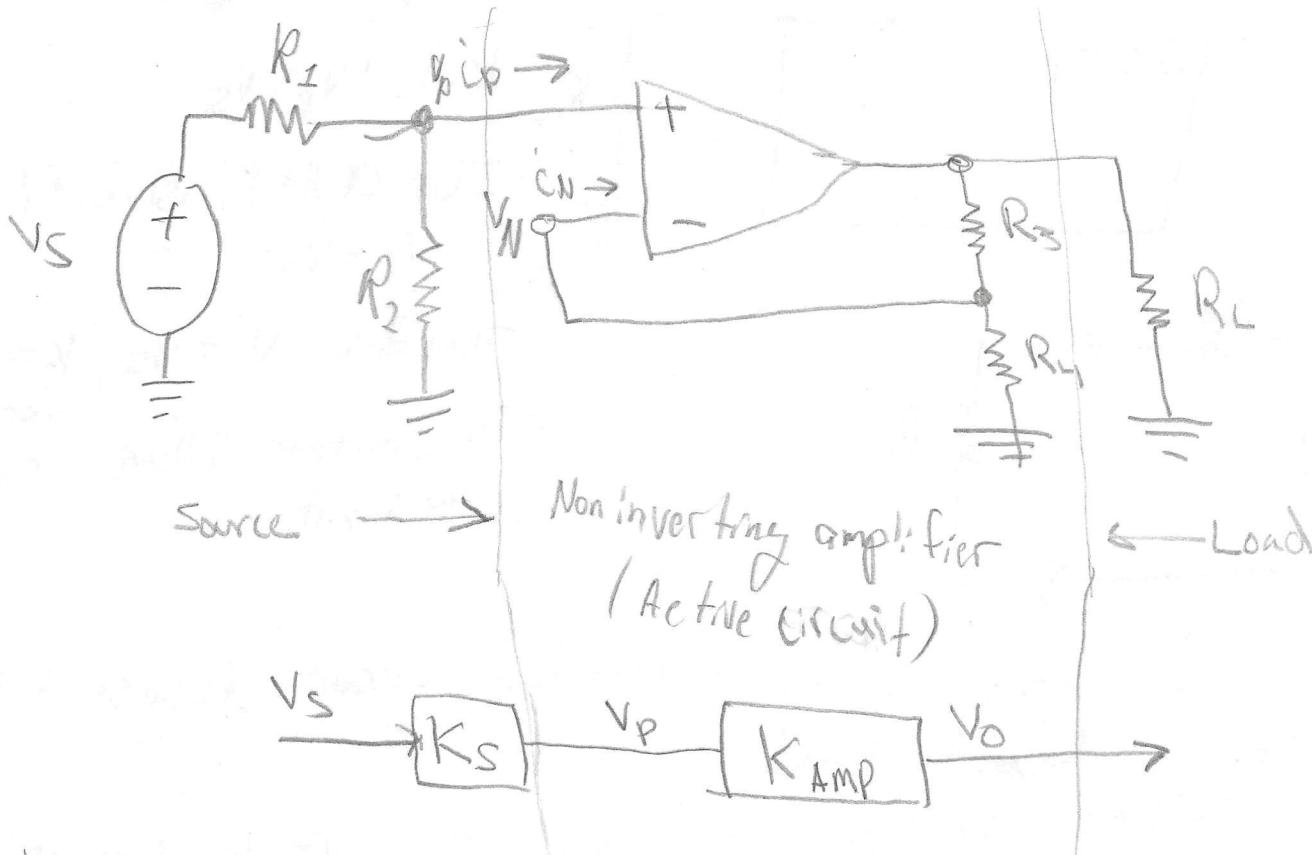Example 4-13, find the input-output relationship of the circuit



We have 2 building block gains

(1) K_s , the proportionality constant of the source circuit

(2) K_{Amp} , gain of the noninverting amp

$$as i_p = 0, so V_p = \frac{R_2}{R_1 + R_2} V_s, K_s = \frac{V_p}{V_s} = \frac{R_2}{R_1 + R_2}$$

Ideal OP AMP


$$\text{constraints: } V_p = V_N = \frac{R_4}{R_3 + R_4} V_o \rightarrow V_o = \frac{R_3 + R_4}{R_4} V_p \quad K_{Amp} = \frac{V_o}{V_p} = \frac{R_3 + R_4}{R_4}$$

26 The overall gain of the circuit

$$K_{\text{circuit}} = K_S K_{\text{AMP}} = \left(\frac{V_p}{V_S} \right) \left(\frac{V_O}{V_p} \right) = \frac{V_O}{V_S} = \left(\frac{R_2}{R_1 + R_2} \right) \left(\frac{R_3 + R_4}{R_4} \right)$$

We can do this because $\phi = 0$ and Ideal OP AMP non-inverting constraints

Voltage Follower

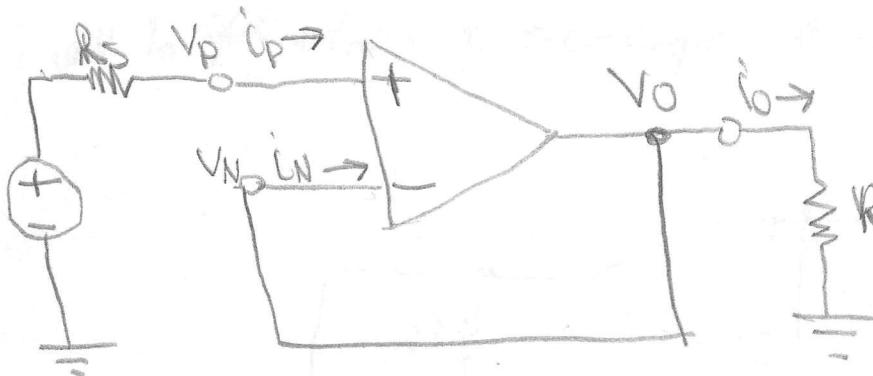


This forces $V_N = V_O$, they're connected

as $i_p = 0$, $V_{RS} = 0$

KVL: $V_p = V_S$

Ideal OP AMP constraint:
 $V_p = V_N$

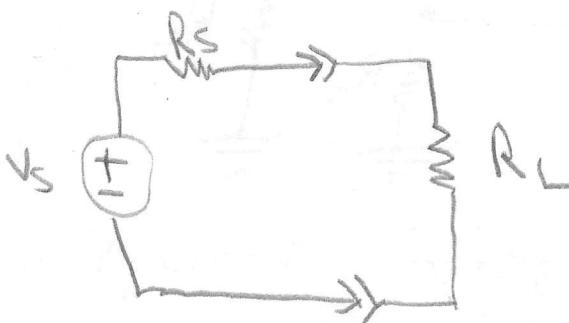Therefore $V_O = V_S$, $K = 1$
also from inspection



The voltage follower is used in interface circuits because it isolates the source from the load

→ Note! The input-output relationship $V_O = V_S$ does not depend on R_S or R_L (source or load resistance)

→ The second circuit is a voltage divider depending on R_S and R_L → This limits the signals that can be transferred across the interface

→ When a voltage follower is being used between source and load, the signal levels are limited by the OP AMP


So the current delivered to the Load, $i_L = \frac{V_0}{R_L}$

$$\text{as } V_0 = V_S, i_L = \frac{V_S}{R_L}$$

but what about $i_P = 0$? V_S isn't 0

→ Supply terminals, output current comes from the power supply
Don't Do KCL at ground p. 186

The Inverting Amplifier

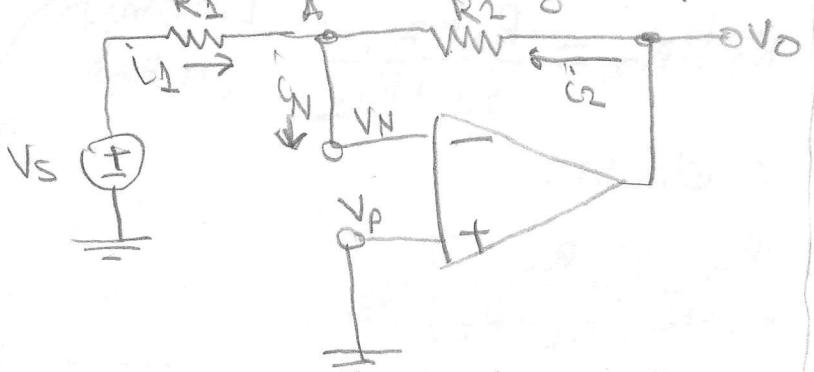

The input signal and the feedback are both applied at the inverting input
noninverting input is grounded
so $V_p = 0$

KCL Node Analysis at A

$$\frac{V_s - V_N}{R_1} + \frac{V_O - V_N}{R_2} - i_N = 0$$

(4-24)

4-39 the inverting
amplifier circuit

OP AMP Constraints: $V_p = V_N, i_p = 0 = i_N$
as $V_p = 0, V_N = 0$

$$\text{so } \frac{V_s - 0}{R_1} + \frac{V_O - 0}{R_2} - 0 = 0 \rightarrow V_O = -\frac{R_2}{R_1} V_s \quad (4-25)$$

We have $V_O = K V_S, K = -\frac{R_2}{R_1}$ the closed-loop gain, it's negative
hence inverting amplifier.



this block diagram indicates inverting or non inverting OP AMP configuration

28

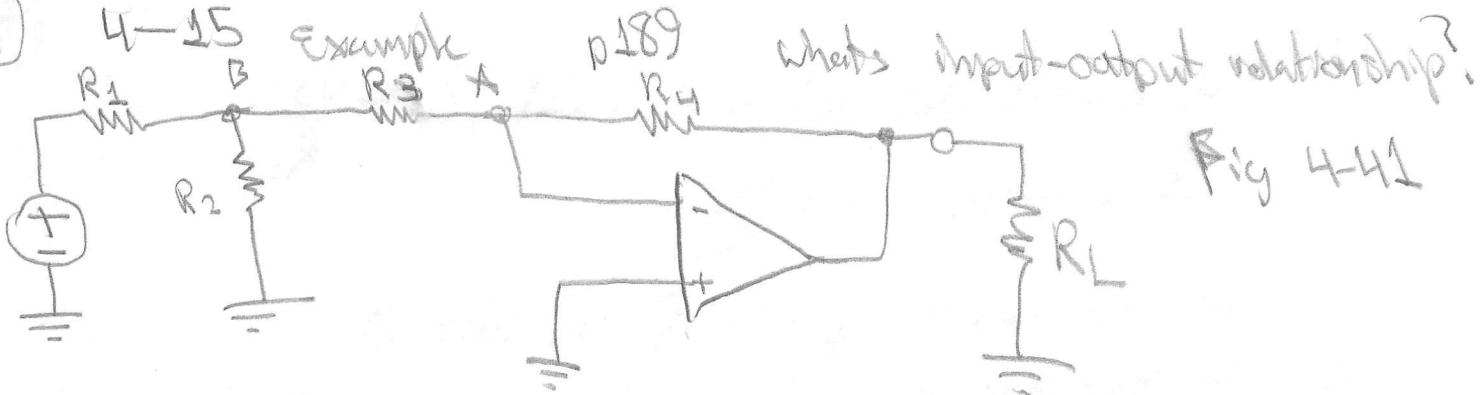


Fig 4-41


The input resistance is affected by the Source circuit, find the Thvenin equivalent

$$V_T = \frac{R_2}{R_1 + R_2} V_s \quad R_T = R_2 // R_1 = \frac{R_1 R_2}{R_1 + R_2} \quad (\text{Look back method})$$

KCL at A and Ideal OP AMP constraints

$$V_O = -\frac{R_4}{R_3 + R_T} V_T = -\frac{R_4}{R_3 + R_T} \left[\frac{R_2}{R_1 + R_2} V_s \right]$$

The Summing Amplifier (adder circuit)

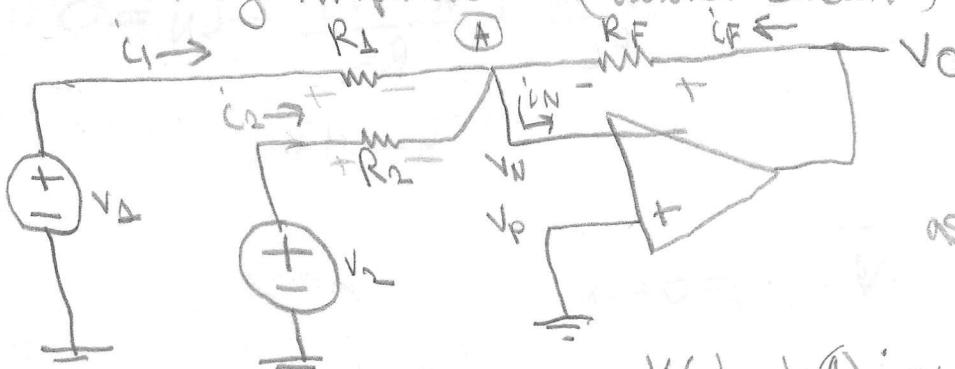

2 inputs connected to Node A, A is the summing point

as $V_p=0$, similar to inverting amplifier

$$\text{KCL at } A: \frac{V_1 - V_N}{R_1} + \frac{V_2 - V_N}{R_2} + \frac{V_O - V_N}{R_F} = 0$$

As $V_p=0, V_N=0, i_N=0$

$$\rightarrow \frac{V_1}{R_1} + \frac{V_2}{R_2} + \frac{V_O}{R_F} = 0$$

$$\rightarrow V_O = -\frac{R_F}{R_1} V_1 - \frac{R_F}{R_2} V_2 \quad (4-28)$$

Fig

4-43

$$K_1 = -\frac{R_F}{R_1} \quad K_2 = -\frac{R_F}{R_2} \quad \text{These are the gains}$$

If $R_1 = R_2 = R$

$$V_o = -\frac{R_F}{R} (V_1 + V_2)$$

Summing Amplifier

Inverting Summer


for n inputs,

$$V_o = \left(-\frac{R_F}{R_1}\right)V_1 + \left(-\frac{R_F}{R_2}\right)V_2 + \dots + \left(-\frac{R_F}{R_n}\right)V_n \quad (4-29)$$

$$= K_1 V_1 + K_2 V_2 + \dots + K_n V_n$$

Note for Non-inverting summer; $V_p \neq 0$ so the K 's at the summing point are influenced by the R 's associated for each input. The example on p162 shows that getting good K 's can be tricky, easier to keep R 's the same

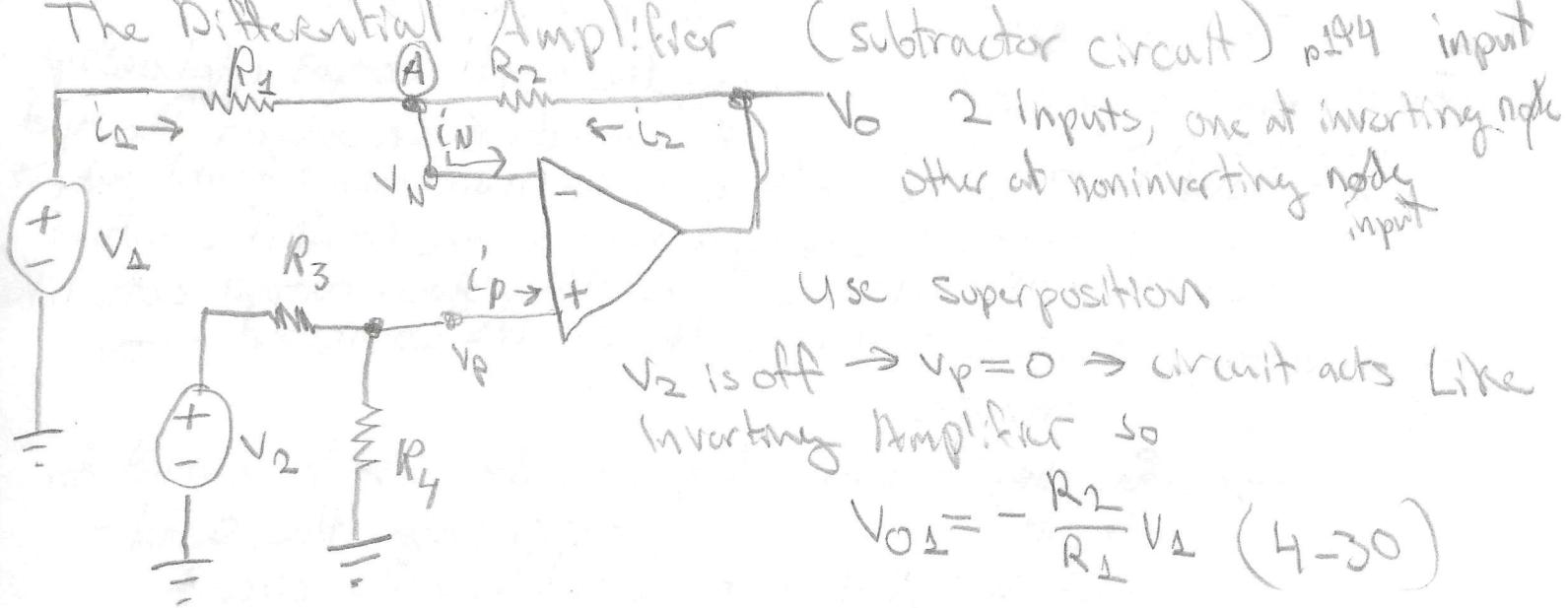The Differential Amplifier (subtractor circuit)




V_2 is off (V_2 on) \rightarrow noninverting amp w/
Voltage divider input so write

$$V_{o2} = \left[\frac{R_L + R_2}{R_L} \right] \left[\frac{R_4}{R_3 + R_4} \right] V_2 \quad (4-31)$$

Superposition: $V_o = V_{o1} + V_{o2} = \left(-\frac{R_2}{R_1}\right)V_1 + \left(\frac{R_L + R_2}{R_L} \frac{R_4}{R_3 + R_4}\right)V_2$

$$V_o = [-K_1] V_1 + [K_2] V_2$$

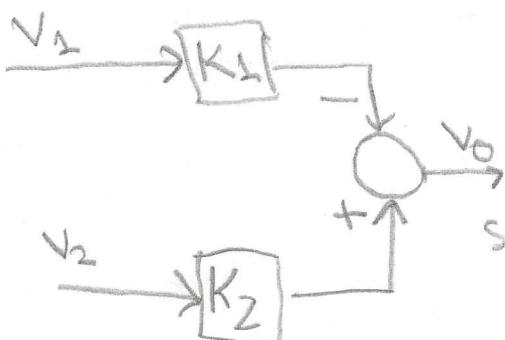for $(R_3/R_2) = (R_4/R_2) \rightarrow V_o = \frac{R_2}{R_1} (V_2 - V_1)$



30 Fig 4-48, Summary of Basic OP AMP signal-processing circuits p 195

Basic OP AMP Building Blocks


The noninverting and inverting amplifiers are represented as gain blocks.

The Summer Amp and differential amp require a gain block and the summer point symbol.

Be careful when going from circuit to block diagram and block diagram to circuit. → Some gain blocks involve negative gains - Gains of inverting summer are negative. The required minus sign is sometimes moved to the summer point and the value of X in the gain block is changed to a positive number. There isn't a standard

The OP AMP circuits defined in 4-48 can be interconnected without changing the input-output relationship of each circuit (as long as the connections are between the input and output). These feedback circuits have insignificant output resistances and can drive any load within the OP AMP's output current capacity. OP AMP circuit building block output acts like ideal voltage sources just like the sources connected to the OP AMP circuit inputs.

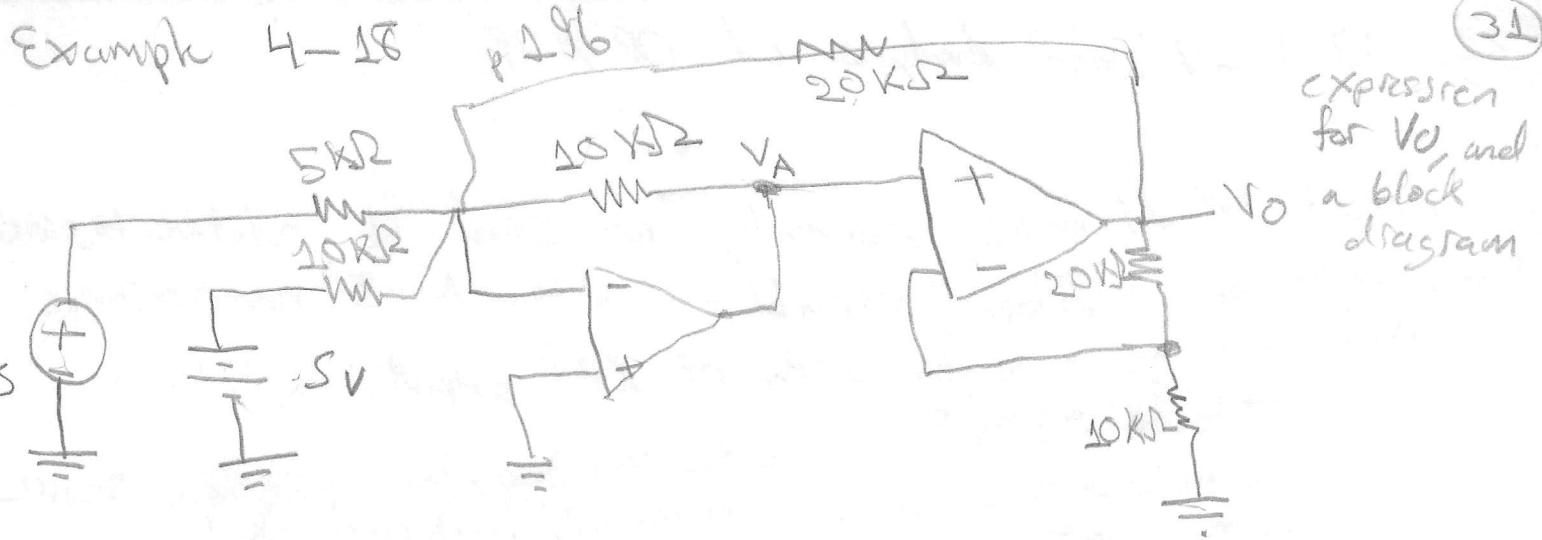→ Connecting the output of one building block circuit to an input of another does not change the signal-processing function performed by either circuit




Solution: we have a 3 input summer, and a non-inverting amplifier, V_A is the output of the summer.

Summer K: $K_n = -\frac{R_F}{R_n} \rightarrow V_A = -5 - 2V_s - \frac{1}{2}V_O$

noninverting k: $k = \frac{R_1 + R_2}{R_2} \rightarrow V_O = 3V_A$


Block Diagram

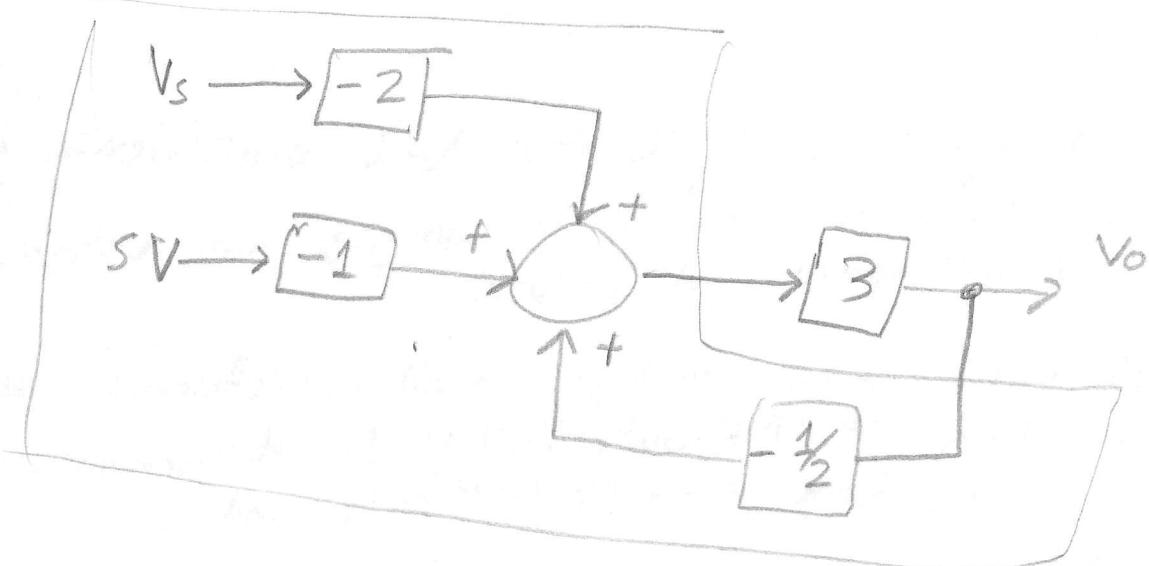

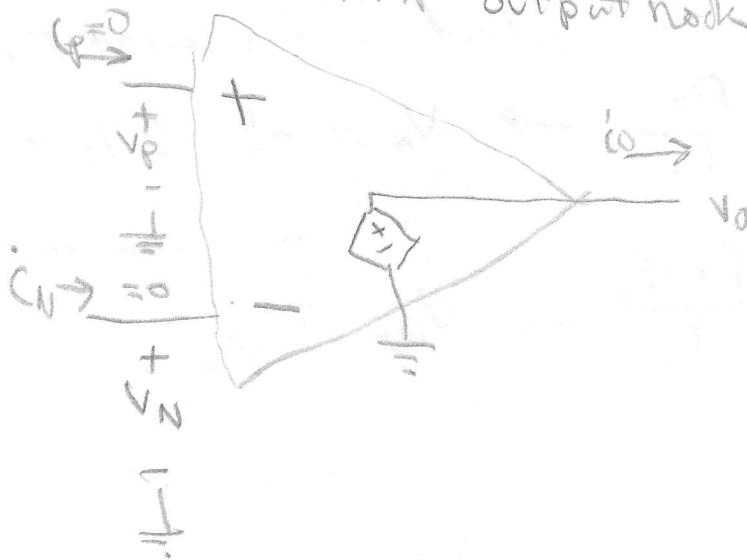(32) Node-Voltage Analysis w/ OP AMPS

circuit w/ N nodes, normally we find V_o relative to ground.
 Now, assign node voltage variables to the $N-1$ nonreference nodes, including a variable at the OP AMP output.

- Ideal OP AMP acts like a dependent voltage source between the output terminal and ground
- The OP AMP Node is determined by the other node voltages so we don't write a node equation at the OP AMP output node




Formulate node equations at the other $N-2$ nonreference in the usual way. But there are $N-1$ node voltages, more unknowns than equations. Recall $V_p = V_N$ and $i_p = i_N = 0$

Steps

- 1) Identify a node voltage at all nonreference nodes, including OP AMP outputs, but do not formulate node equations at the OP AMP output nodes.
- 2) Formulate node equations at the remaining nonreference nodes and then use the ideal OP AMP voltage constraint $V_p = V_N$ to reduce the number of unknowns

Example 4-20

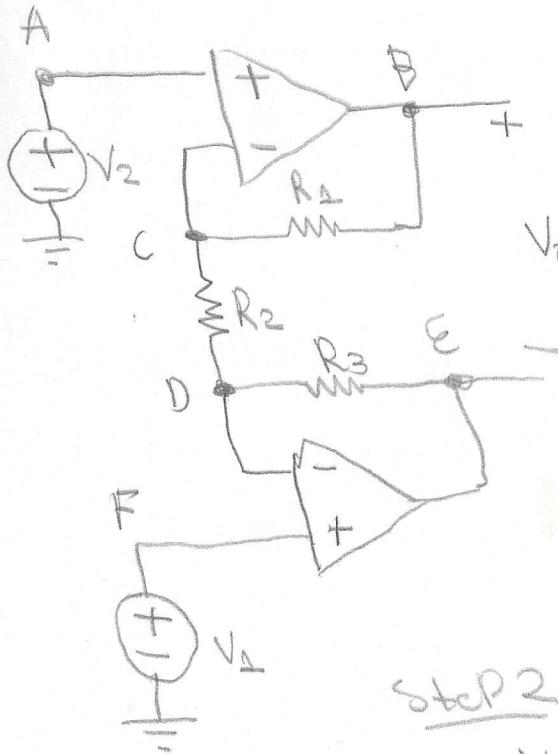

Derive an expression for V_0 in terms of V_1 and V_2

This circuit is not an interconnection of OP AMP circuits (R_2 is connected between two inputs)

Step 1: 6 non reference nodes, B, E are output nodes. A, F are known. so C, and D

$$C: -\frac{V_C - V_B}{R_2} + \frac{V_D - V_C}{R_2} = 0$$

$$D: \frac{V_C - V_D}{R_2} - \frac{V_D - V_E}{R_3} = 0$$

Step 2: recall $V_p = V_N$ for ideal OP AMP constraints
 $V_D = V_A$, $V_C = V_2$

$$\rightarrow C: -\frac{V_2 - V_B}{R_2} + \frac{V_1 - V_B}{R_2} = 0 \quad \text{find expression in terms of } V_B$$

$$D: \frac{V_2 - V_A}{R_2} - \frac{V_A - V_E}{R_3} = 0 \quad " \text{ for } V_E$$

$$\rightarrow V_B = \frac{R_1}{R_2}(V_2 - V_1) + V_2, \quad V_E = \frac{R_3}{R_2}(V_1 - V_2) + V_1$$

$$\text{So we have } V_0 = V_B - V_E = \left(\frac{R_1 + R_3}{R_2} \right) (V_2 - V_1)$$

These are 2 noninverting amplifiers

I didn't take notes for 4-5 OP AMP Circuit Design

4-6 OP AMP Circuit Applications.